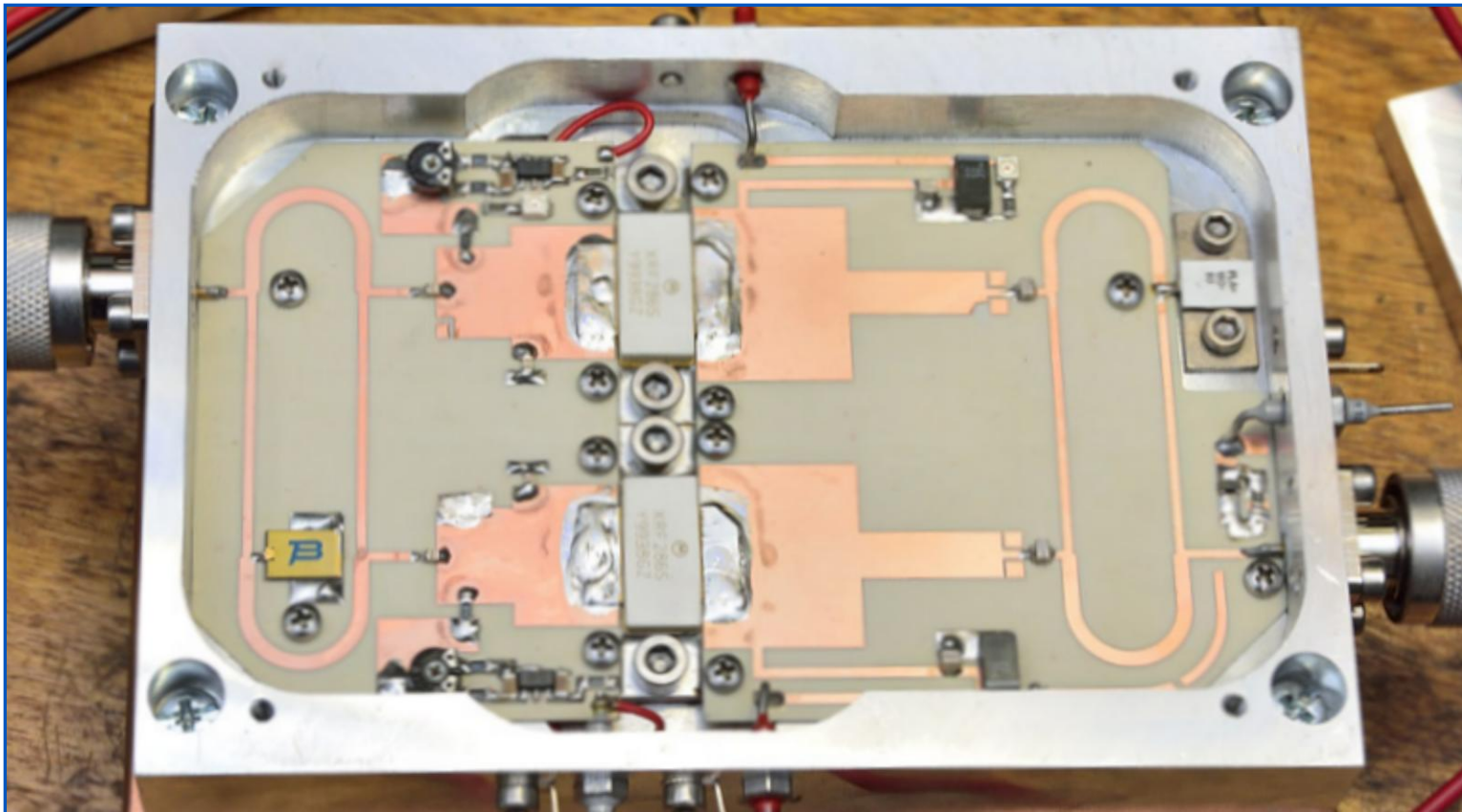


# QUADRATURE (90°) HYBRIDS



**K5TRA**

## BENEFITS FROM QUADRATURE HYBRIDS


- Quadrature split to identical loads has 1:1 input VSWR *regardless of the mismatch of those loads*
- Matched variable attenuators, variable phase shifters and negative resistance amplifiers can be realized
- Load sensitivity of combined amplifiers is reduced
- Reverse IMD performance is improved over individual amplifiers

# TYPES of QUADRATURE HYBRIDS

- Coupled transmission lines (directional couplers)
- Branch-line coupler (non-coupled lines)
- Lumped 'equivalent' representations of coupled-line and branch-line couplers
- All have common properties:
  - Input signal is split between two output ports (-3 dB each)
  - Phase difference between output ports is  $90^\circ$
  - A fourth port is provided for coupling to opposite  $90^\circ$  rotation. This is the hybrid isolate port.
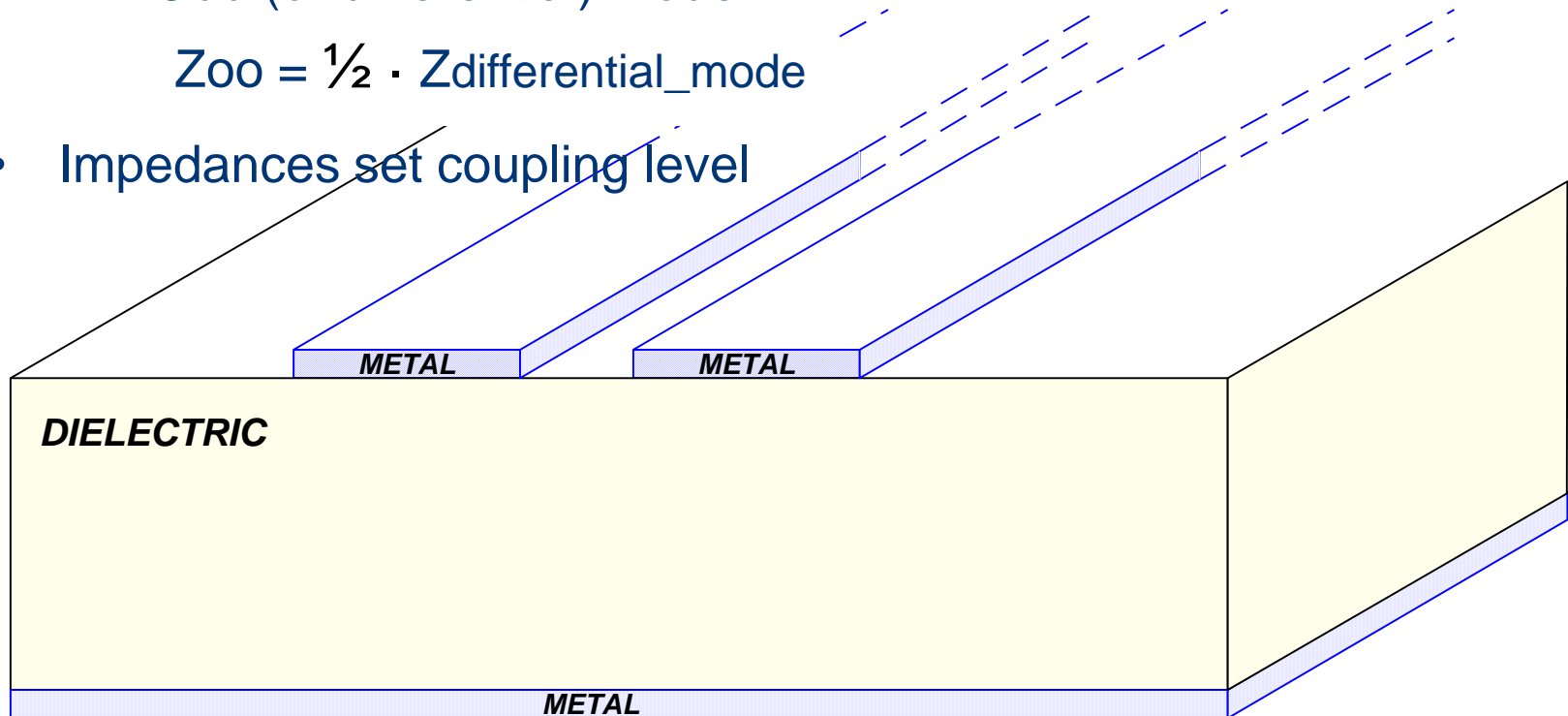
# COUPLED LINES - SYMMETRIC

- Two transmission-line modes:
  - Even (or common) mode  
 $Z_{oe} = 2 \cdot Z_{\text{common\_mode}}$
  - Odd (or differential) mode  
 $Z_{oo} = \frac{1}{2} \cdot Z_{\text{differential\_mode}}$
- Impedances set coupling level



# COUPLING COEFFICIENT $k$

$$C_{dB} = -20 \log(k)$$

$$k = 10^{\left(\frac{-C}{20}\right)}$$

$$k = \frac{\frac{Z_{oe}}{Z_{oo}} - 1}{\frac{Z_{oe}}{Z_{oo}} + 1}$$


$$Z_{oe} = \sqrt{\frac{1+k}{1-k}}$$

$$Z_{oo} = \sqrt{\frac{1-k}{1+k}}$$


$$Z_o = \sqrt{Z_{oe} Z_{oo}}$$

- 3 dB coupler:  $k = 0.707$
- Slight over coupling improves BW
- 50  $\Omega$  3 dB coupler impedances:  
 $Z_{oe} = 120.7 \Omega$   
 $Z_{oo} = 20.7 \Omega$


# Zoe/Zoo vs COUPLING (dB)

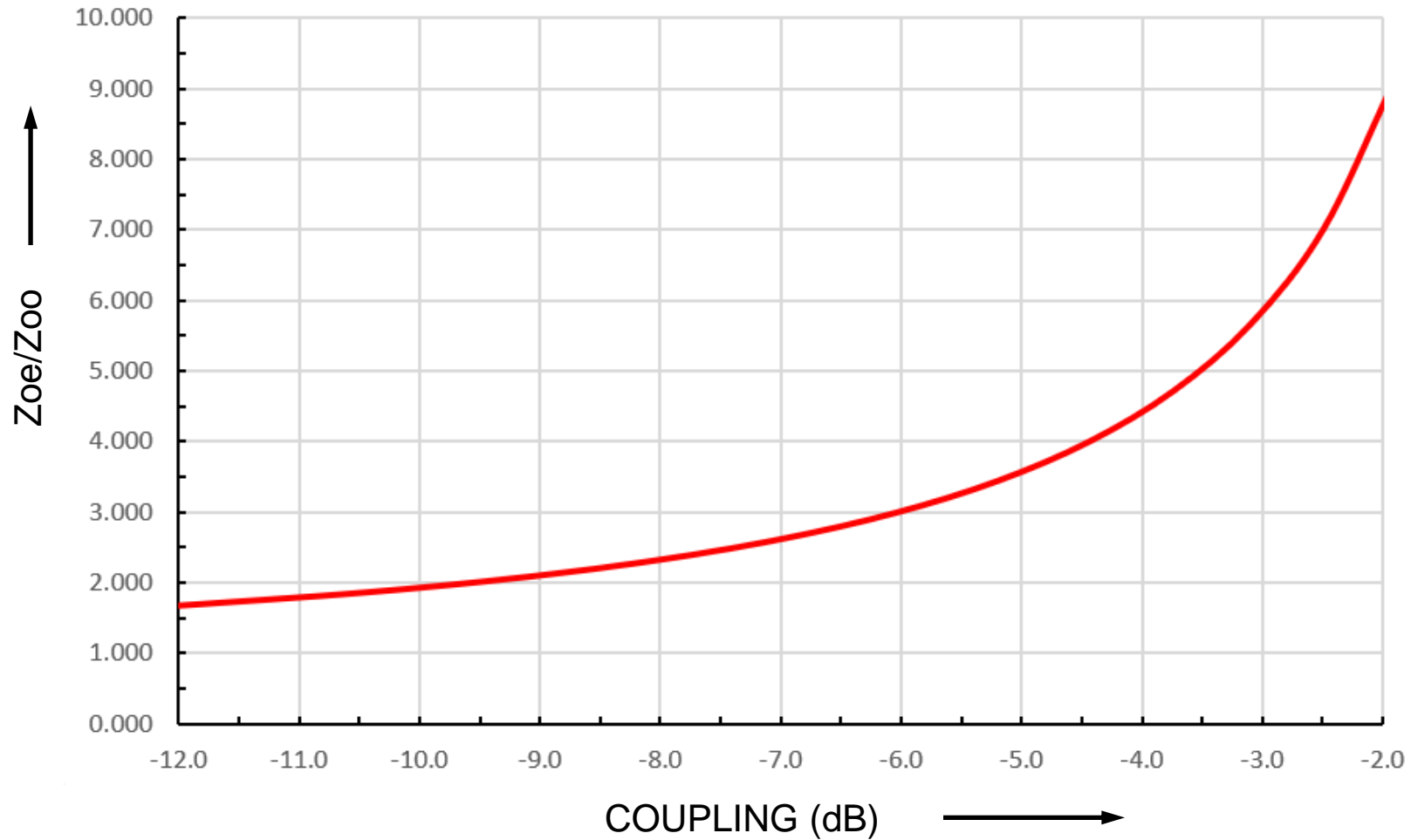

# POWER COMBINING LOSS DUE TO ERROR

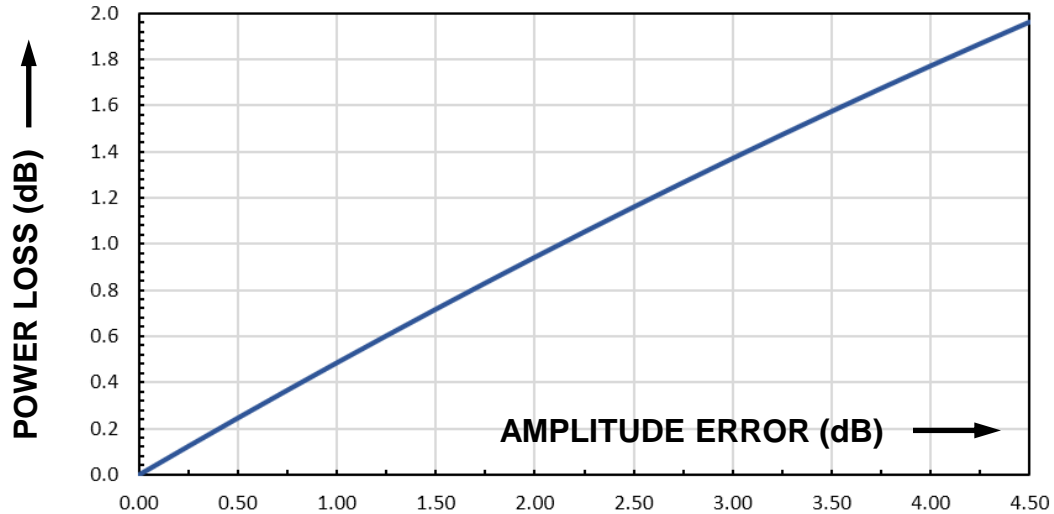


# BASIC DIRECTIONAL COUPLER

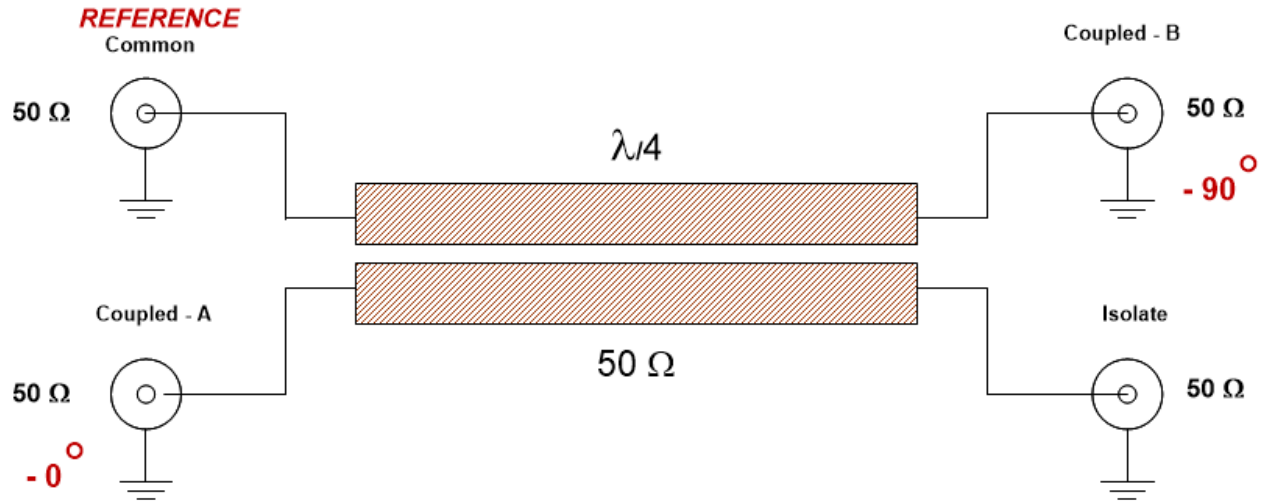

- Port phase relationships are independent of coupling level
- Coupled port (A) level is set by coupling
- Coupled port (B) level (the through line) receives the remainder of input signal that is not coupled to port (B)




# FOLDED COUPLER SYMBOL

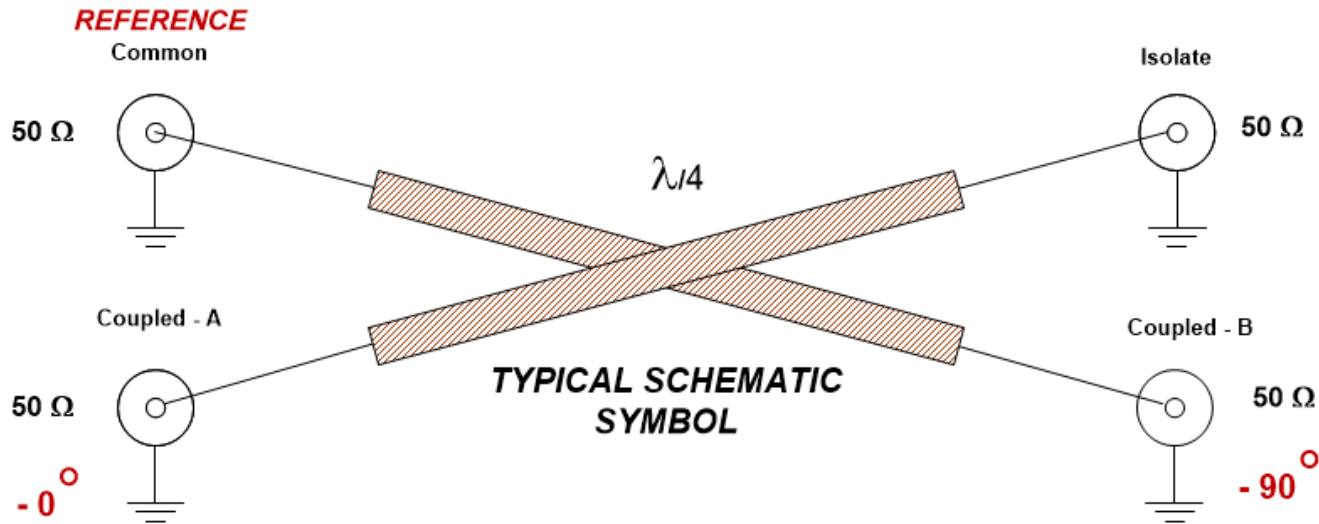


- Convenient schematic representation for 3 dB hybrids
- Both coupled ports are drawn on same side of coupler
- Often used schematically for any of the coupled line structures

# LANGE COUPLER

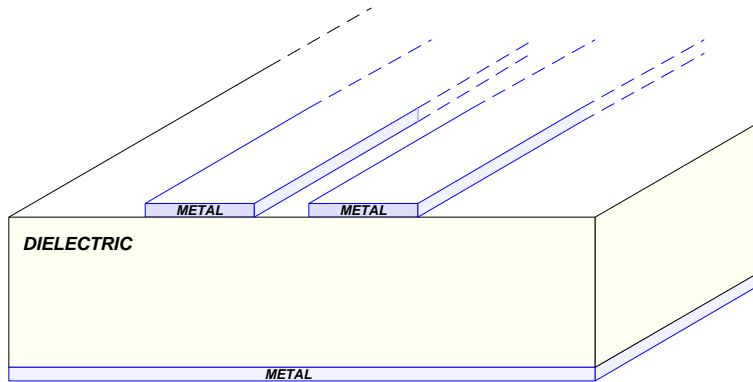


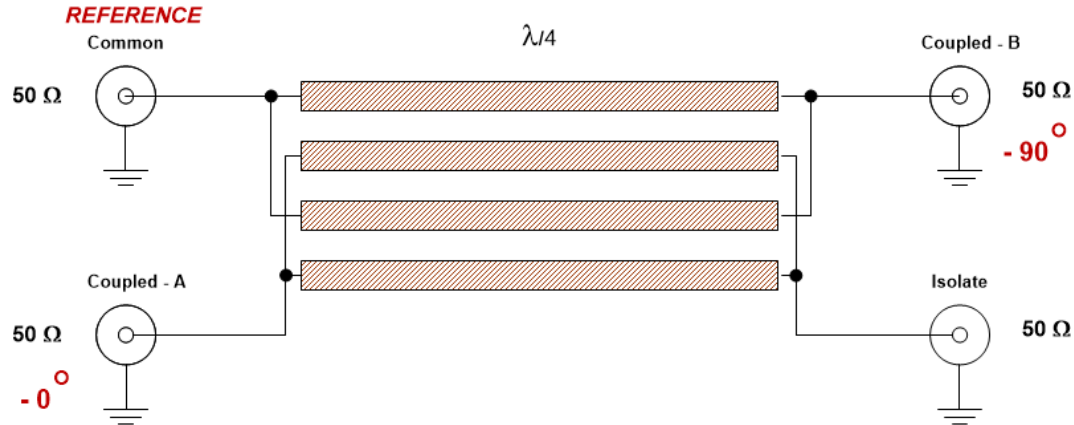- Coupled microstrip couplers are practically limited by dimensions to around -10 dB coupling
- We need at least -3dB coupling







- If the lines are split and interdigitated, greater coupling can be achieved
- This is the basic Lange coupler

# FOLDED LANGE COUPLER


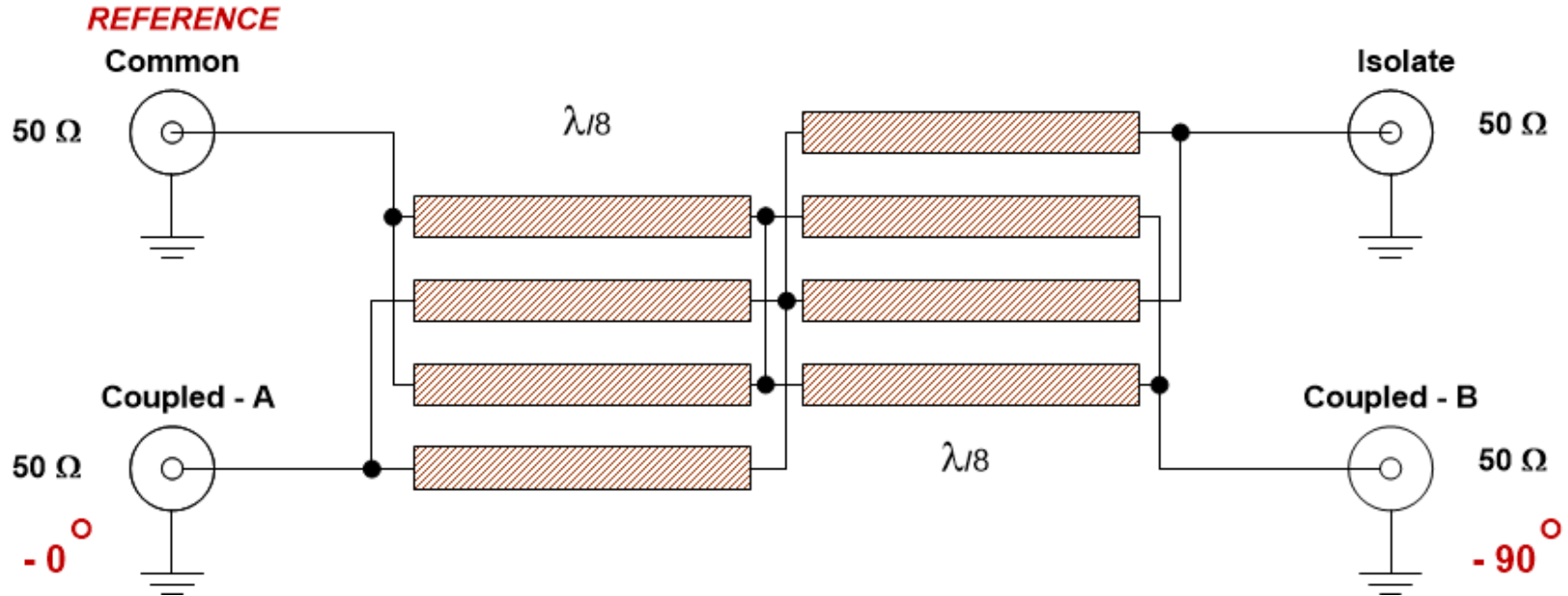


- Folded Lange coupler has both coupled ports on the same side
- This is the most commonly used form


# FOLDED LANGE COUPLER - RESPONSE

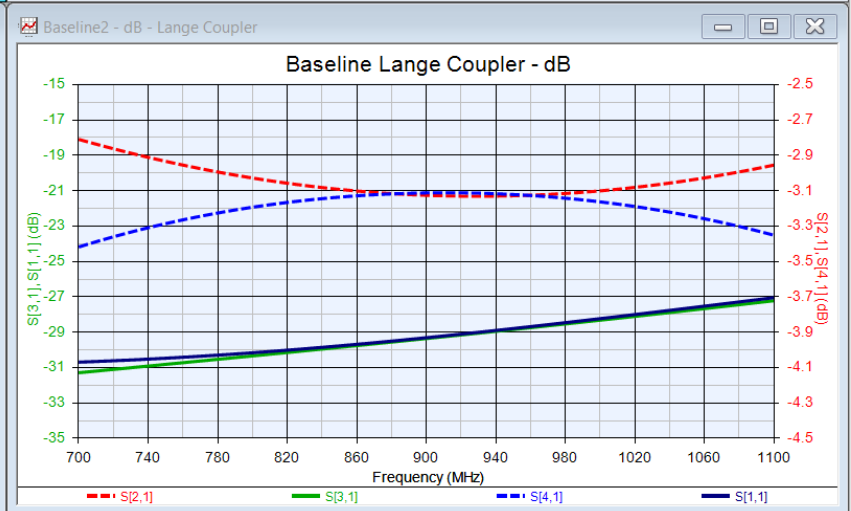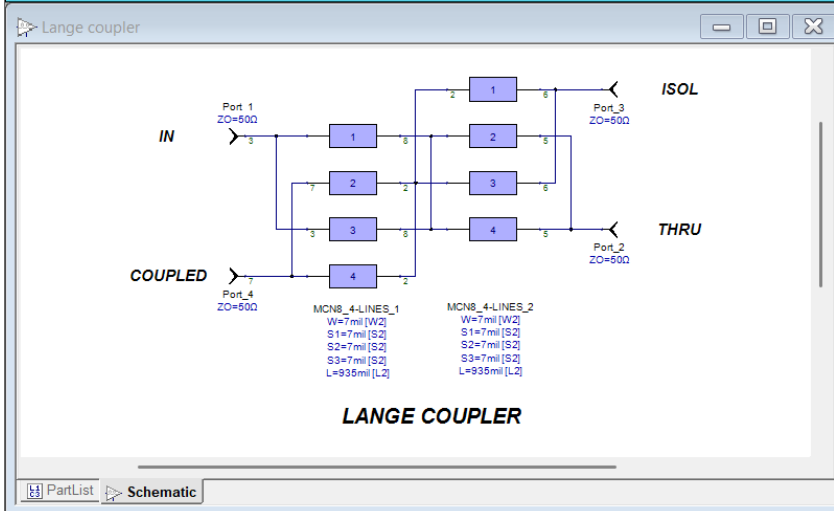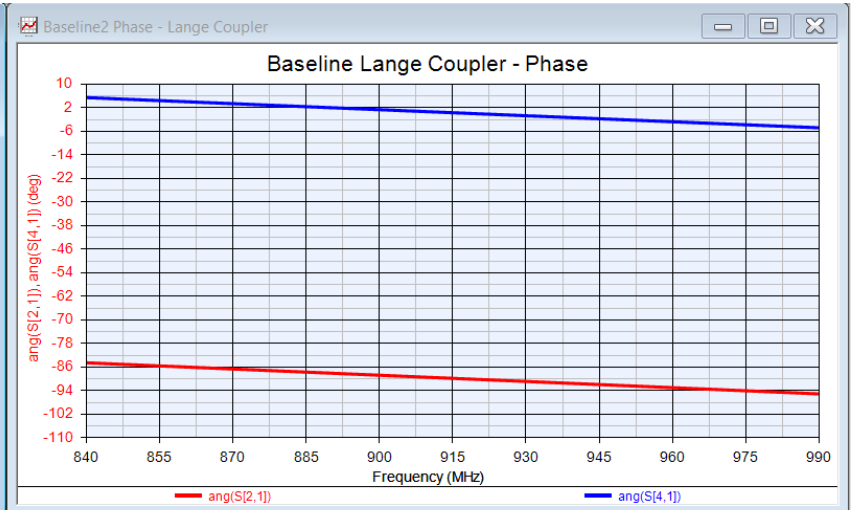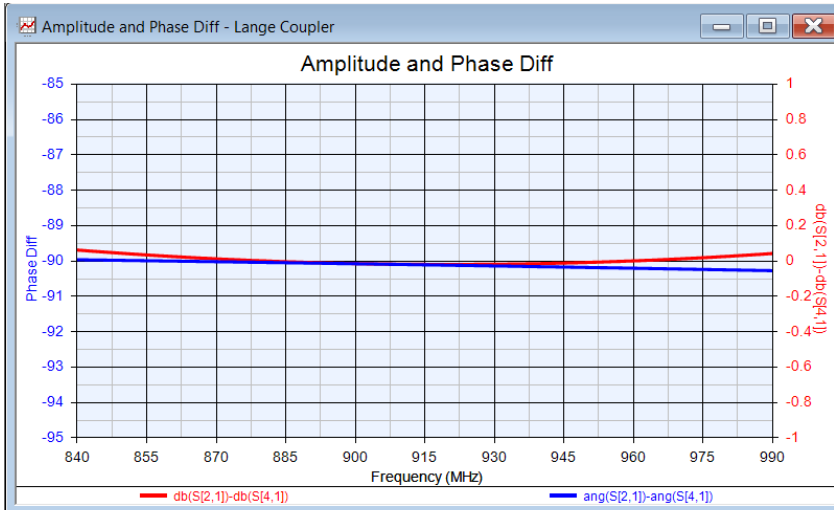

# LANGE COUPLER PHOTOS



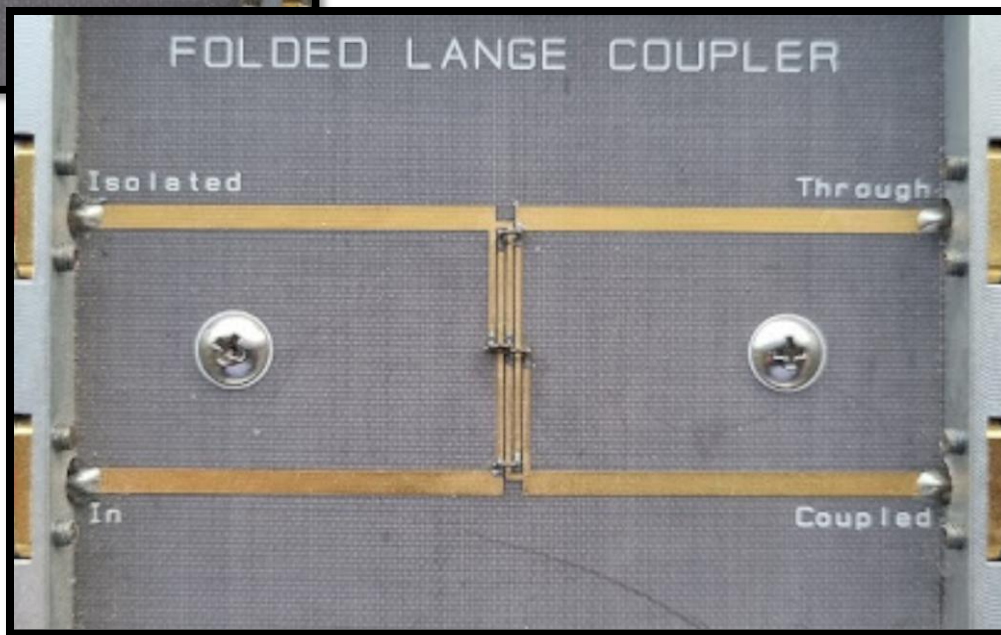
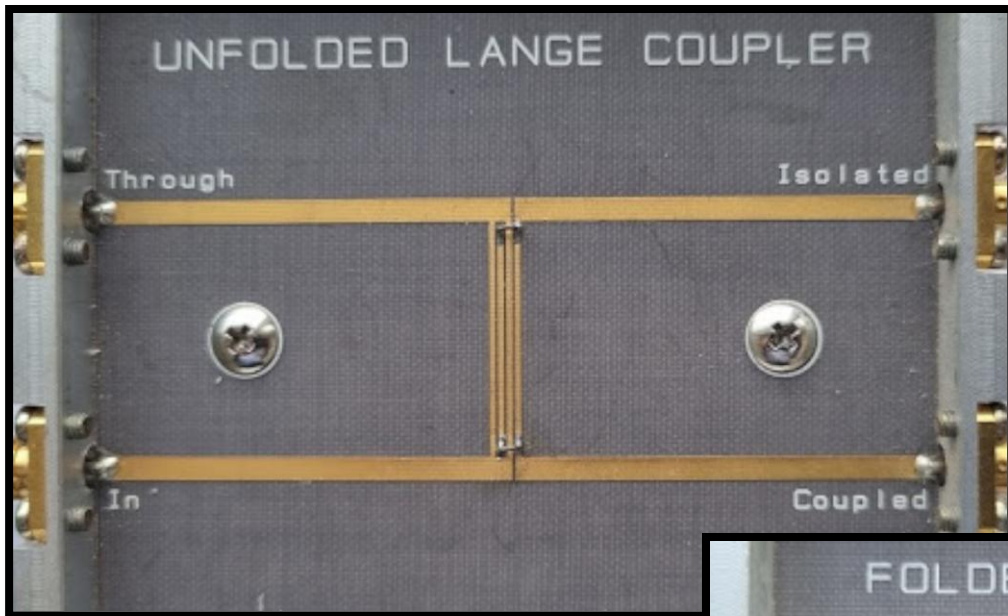


# BRANCHLINE HYBRID

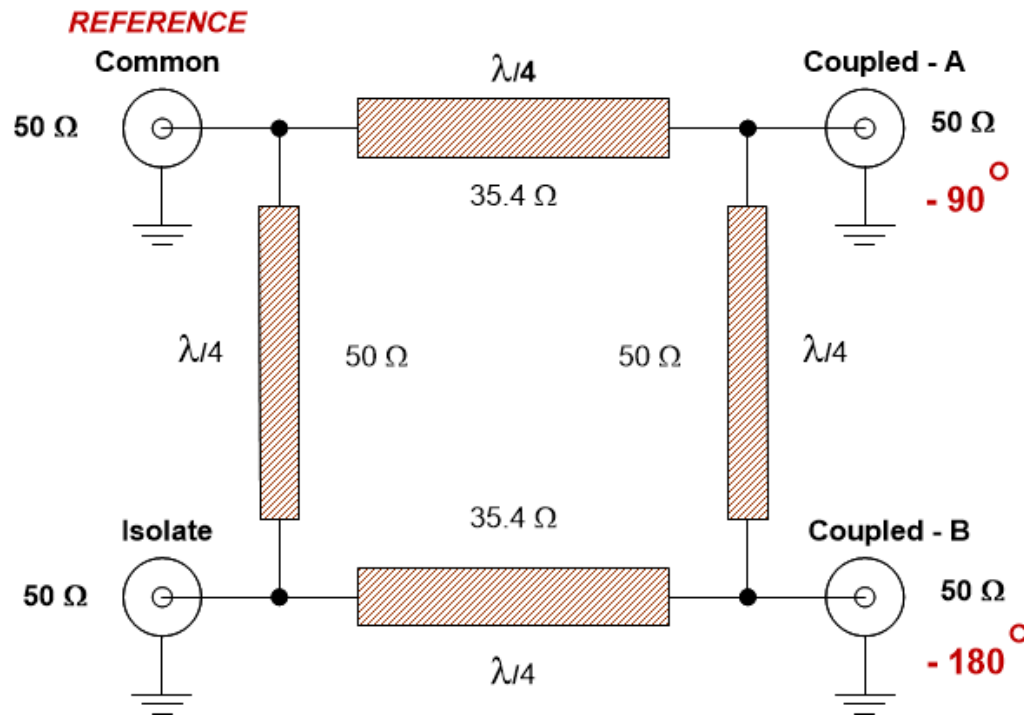


- The branchline hybrid does not use coupled lines
- Amplitude match of coupled ports isn't as good as the Lange coupler
- Power handling of a branchline hybrid is better


# BRANCHLINE HYBRID - RESPONSE

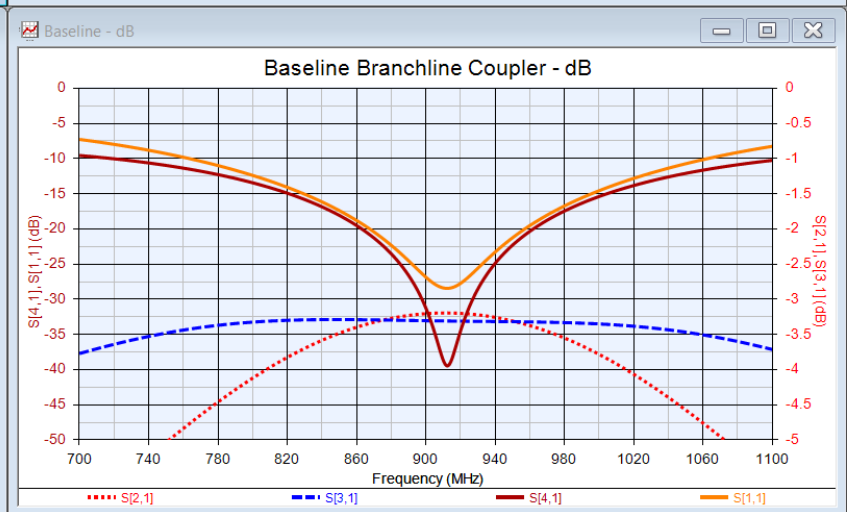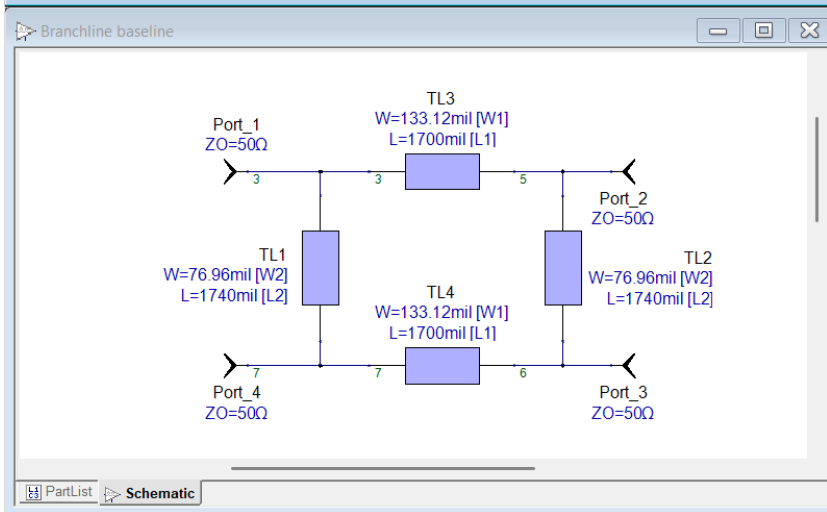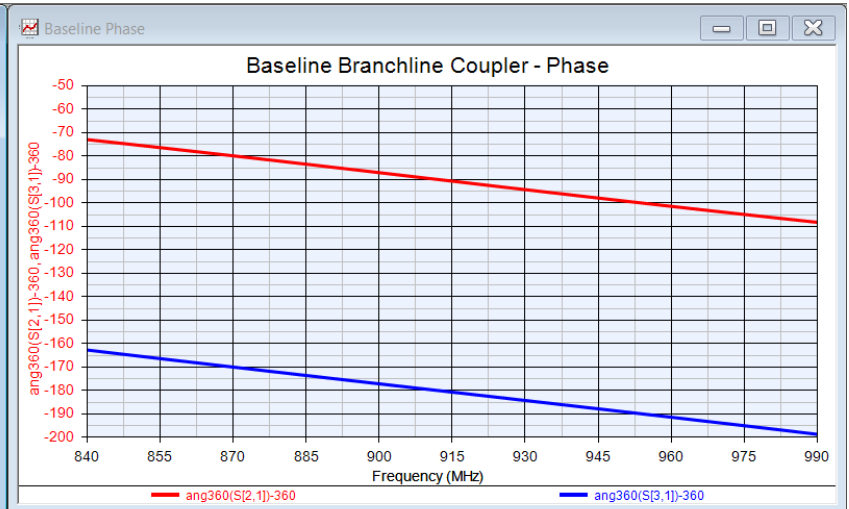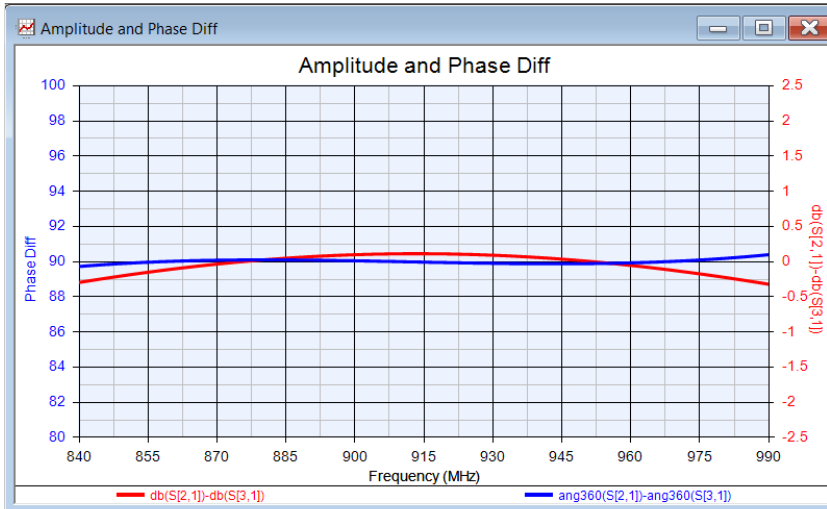

# LUMPED BRANCHLINE HYBRID




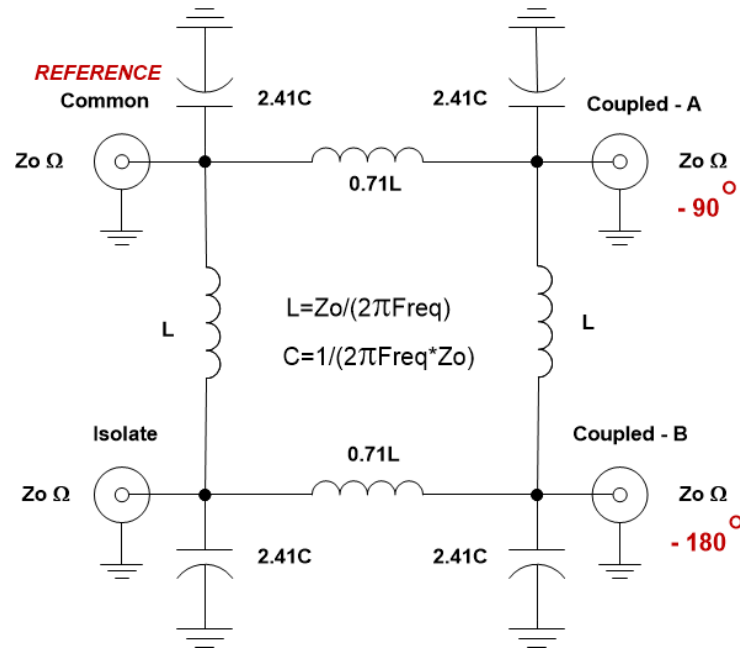


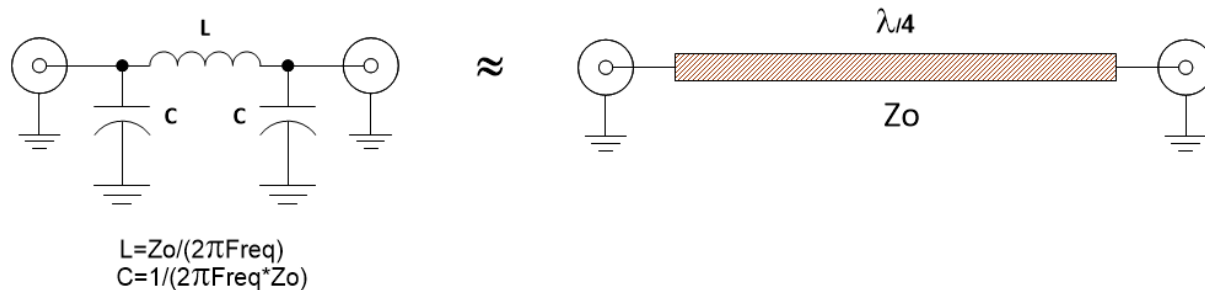- A lumped branchline hybrid uses an LC approximation of the branchline quarter-wave lines:






# LUMPED BRANCHLINE HYBRID - RESPONSE

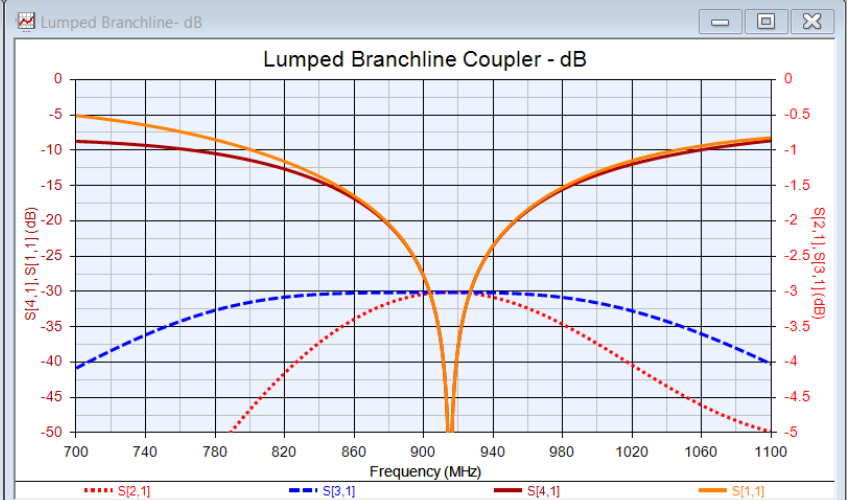
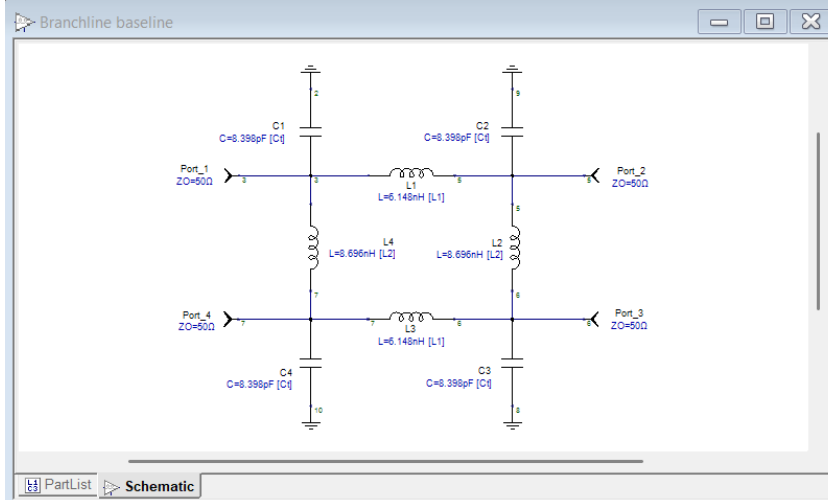
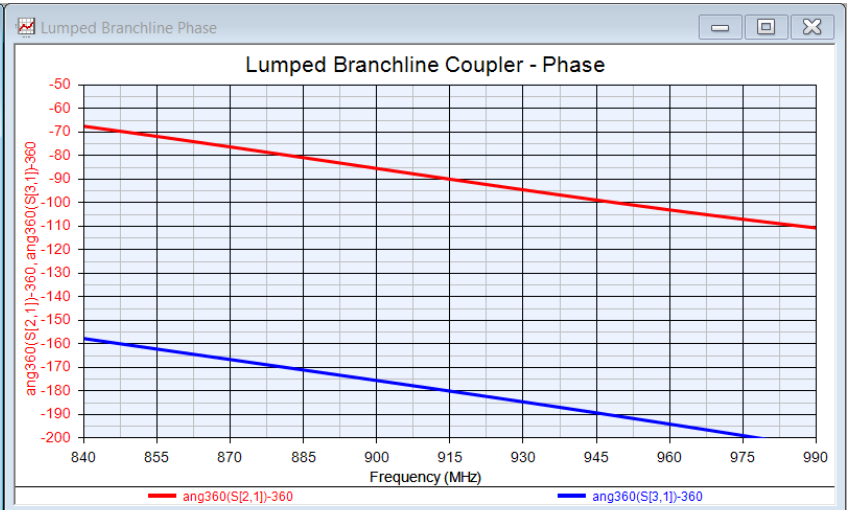
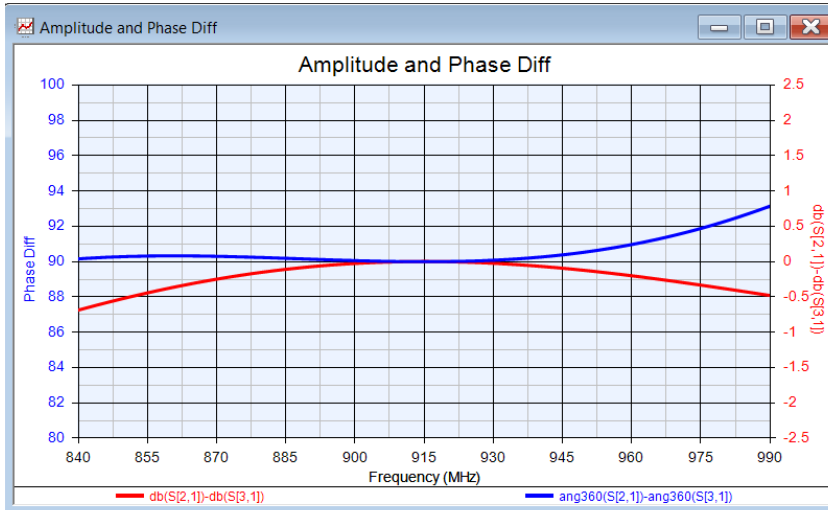


# LUMPED COUPLED-LINE HYBRID


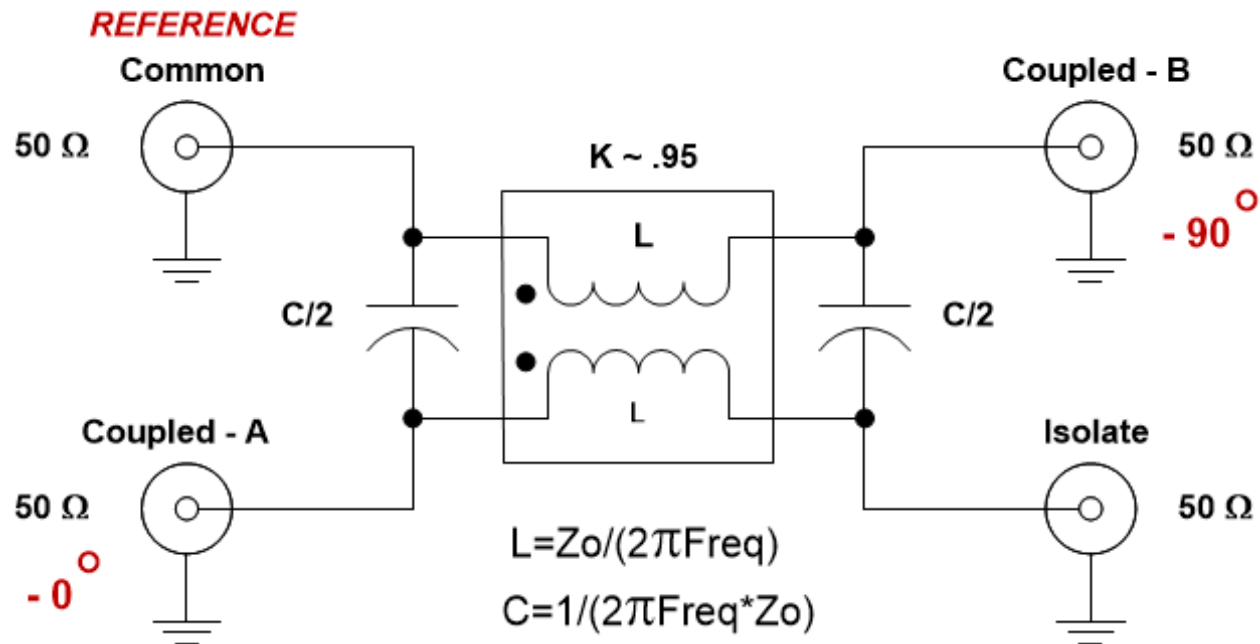


- A lumped coupled-line hybrid uses a tightly coupled pair of inductors
- Amplitude response is very narrow-band

# LUMPED COUPLED-LINE HYBRID - RESPONSE

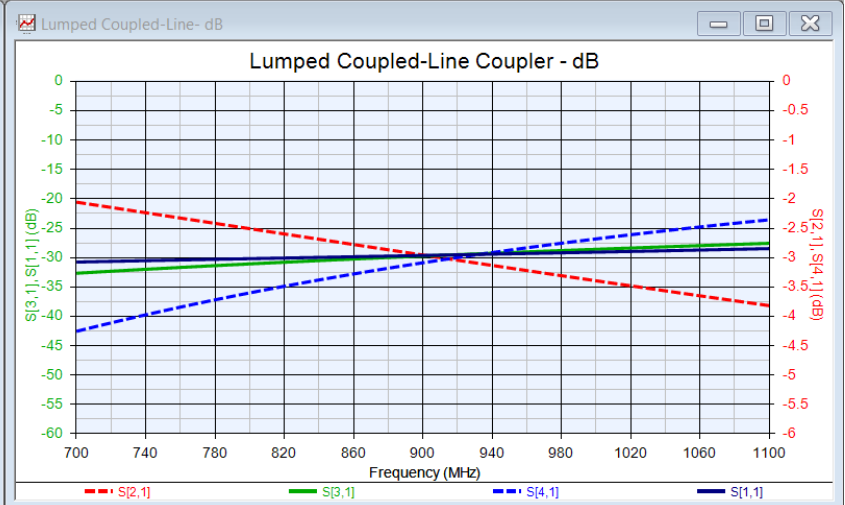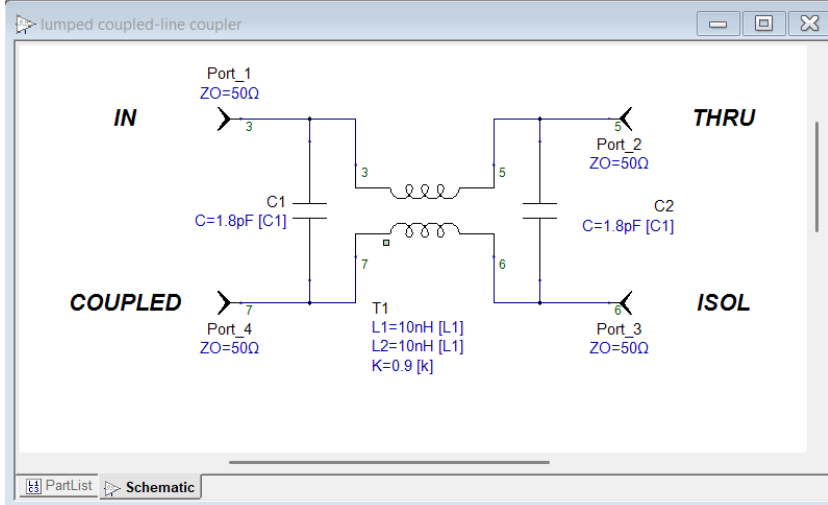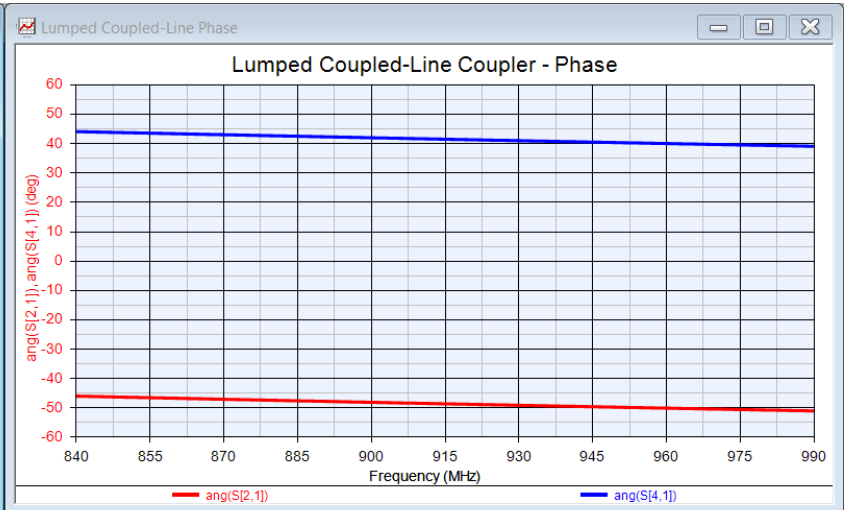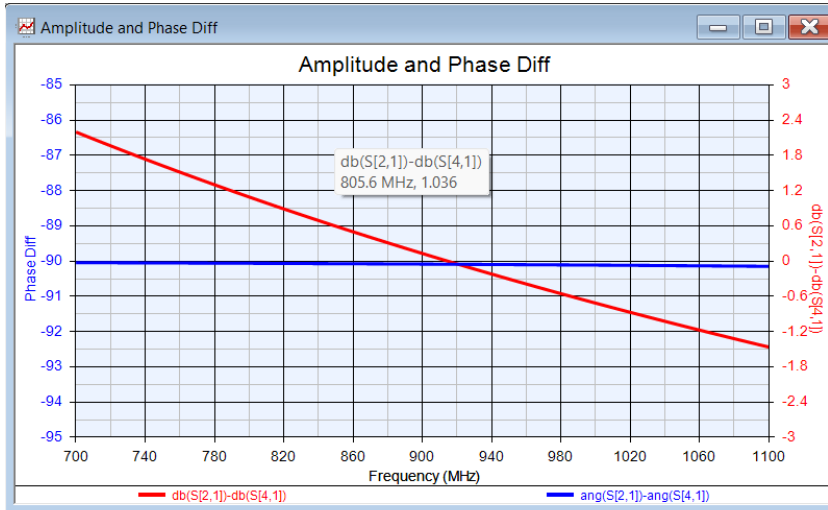


# WIRELINE COUPLED LINE HYBRIDS

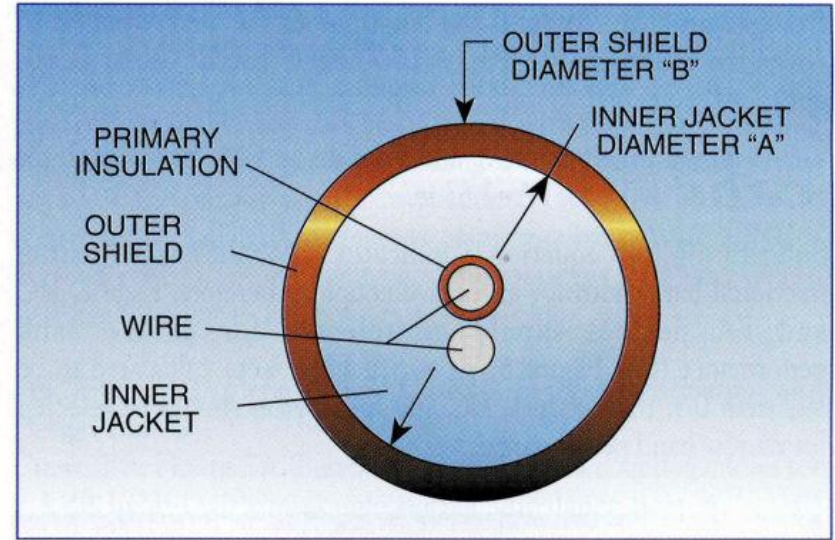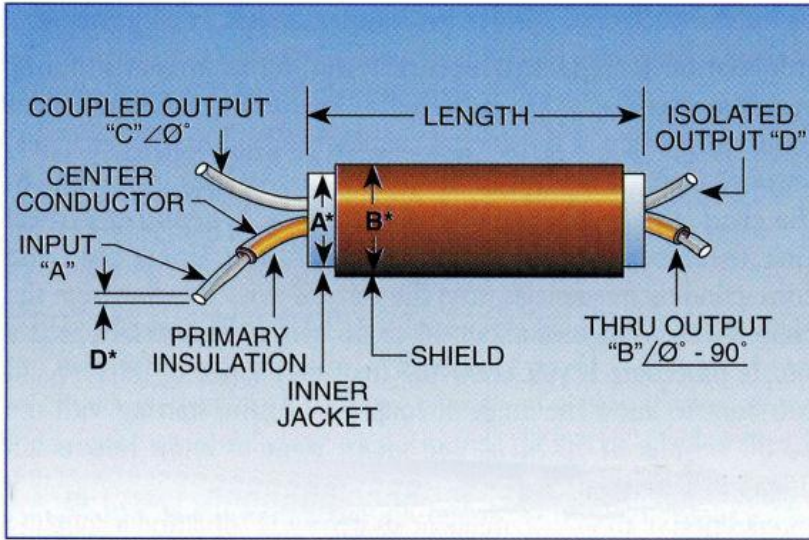


- A shielded pair of lines can provide a directional coupler
- 3 dB couplers of this form were first sold by Sage Labs (now API)

# SPECIAL REFLECTION CHARACTERISTICS

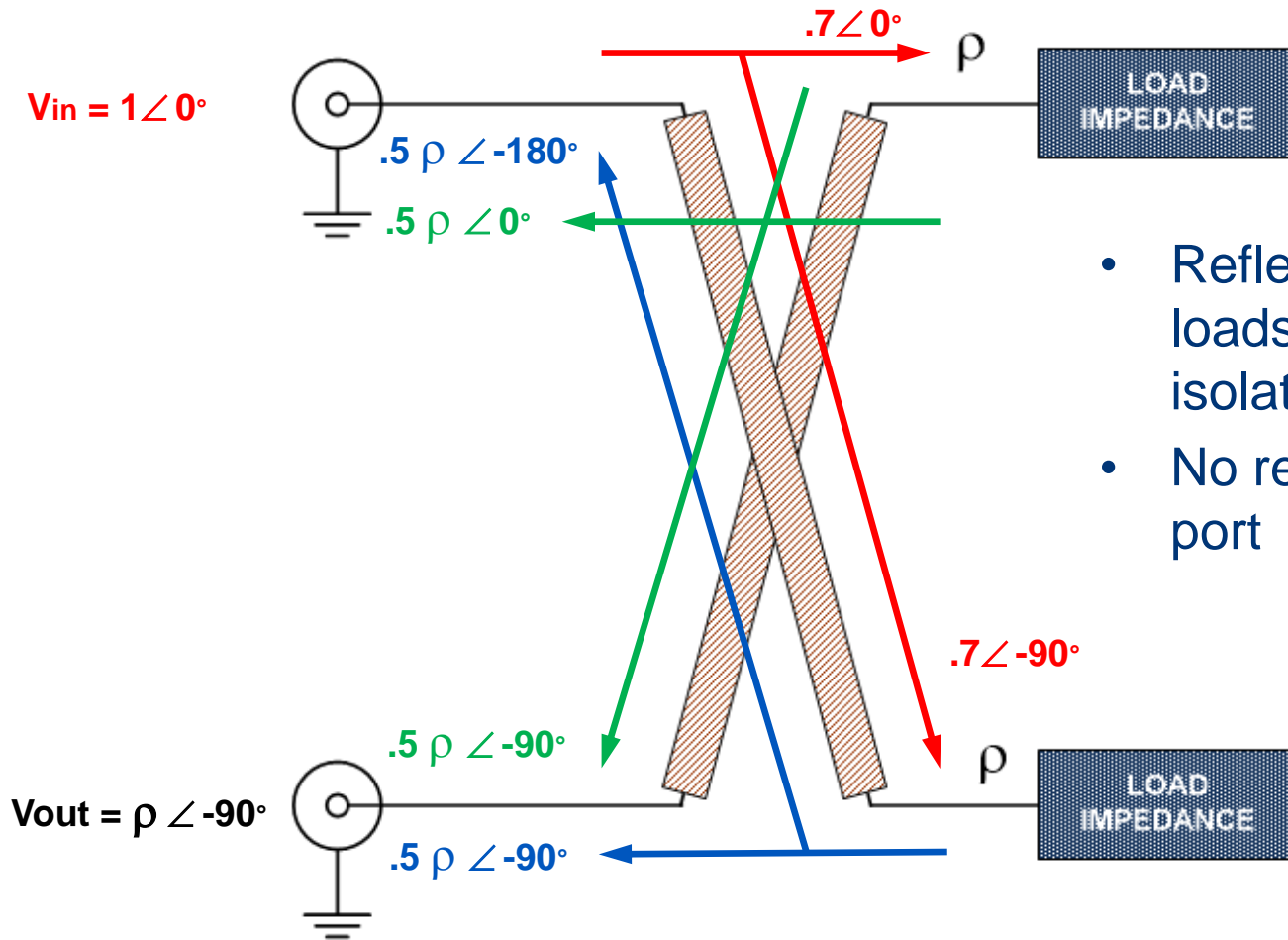


- Reflection from equal loads combine to the isolate port ( $V_{out}$ )
- No reflection to input port

# APPLICATIONS – DIODE CIRCUITS

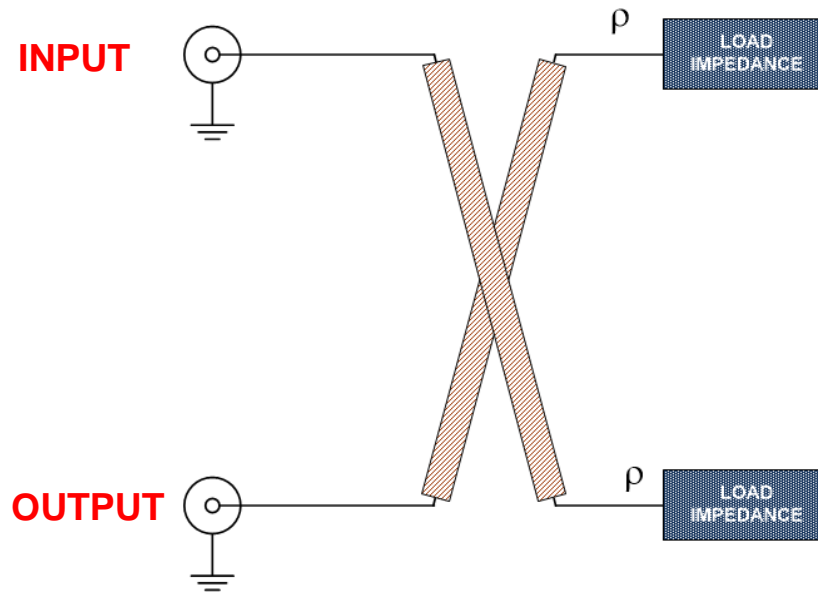


- Amplifier from negative resistance diodes: Impatt, Gunn or Tunnel
- Variable phase shifter from varactor diodes
- Variable attenuator from PIN diodes

# APPLICATIONS – AMPLIFIER COMBINING

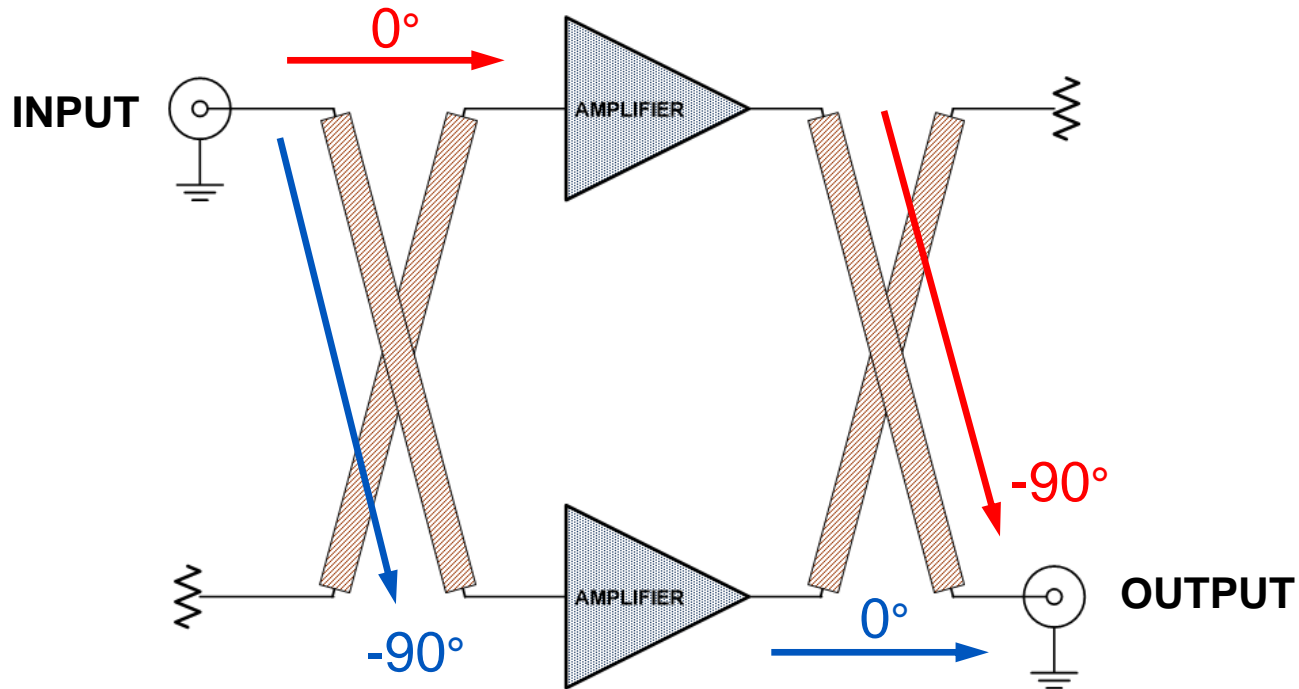

- ① The total phase shift through hybrids is  $-90^\circ$  for each amplifier path to the output port. Both amplifier signals arrive in-phase at the output port.


# APPLICATIONS – AMPLIFIER COMBINING

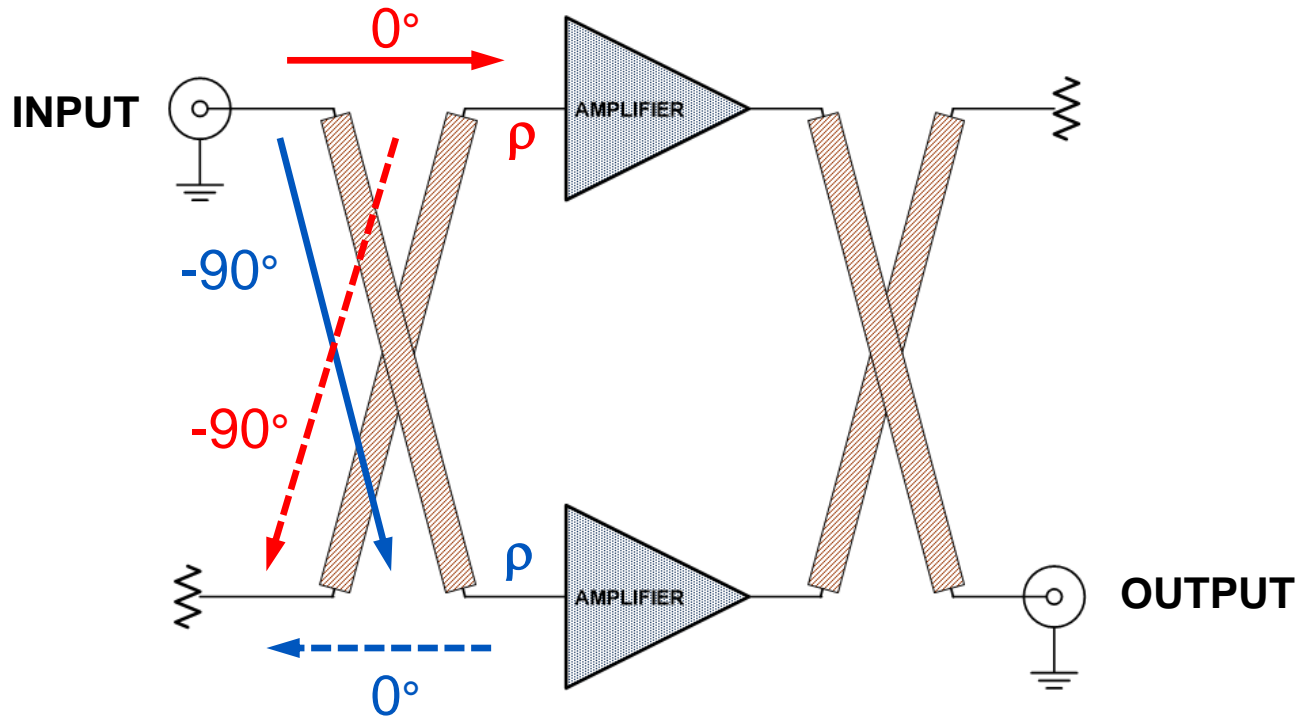

- ② Input from each amplifier is sent to the isolate termination. The path phase shift for each amplifier to the isolate termination is:  $\angle\rho - 90^\circ$ . Input VSWR of the pair is 1:1.




# APPLICATIONS – AMPLIFIER COMBINING

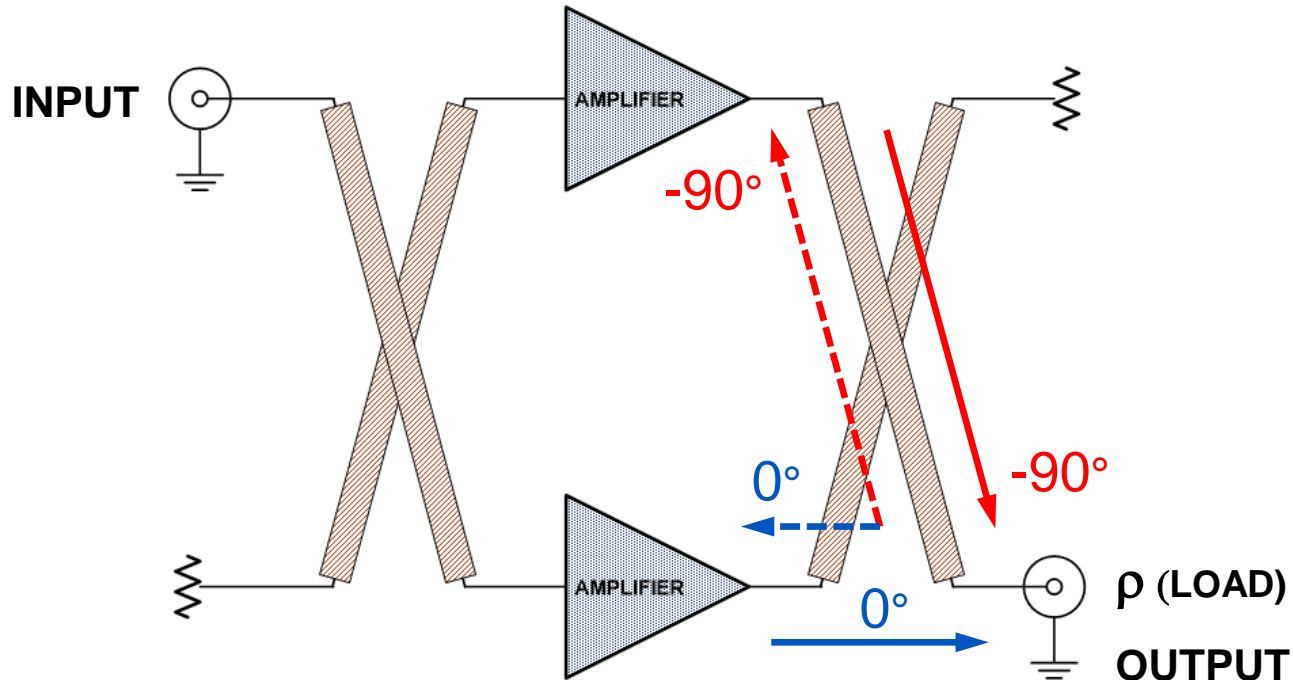


③ Load mismatch is applied differently. Upper amplifier sees the load reflection shifted by  $-180^\circ$  more than the lower amplifier. This desensitizes the pair. If one amplifier is more heavily loaded, the other is more lightly loaded. The total supply current is more constant. Note: Both amplifiers do see a mismatched load.

# APPLICATIONS – AMPLIFIER COMBINING

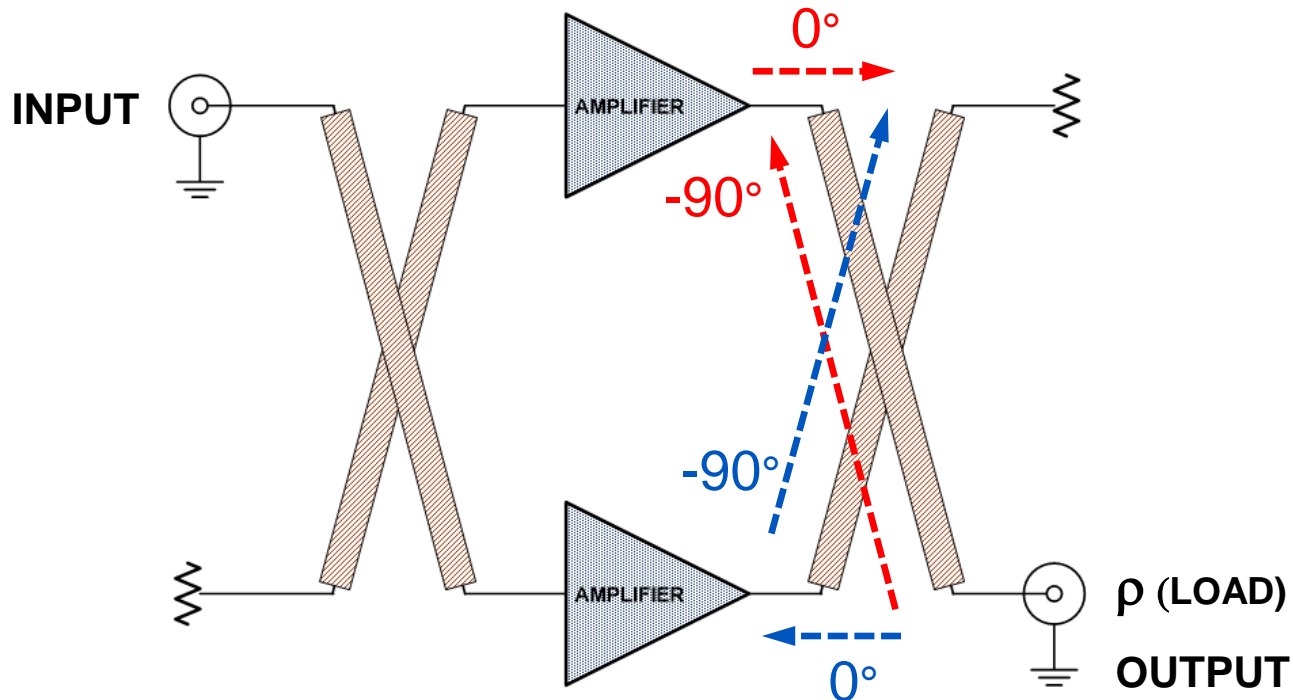

④ Power amplifier output match is for power not reflection; so, a single amplifier operating into a mismatch experiences multiple reflections due to mismatched source and load. This problem is mitigated in quad-combined amplifiers. Any reflected signal from the amplifier output is combined at the isolate termination.

# APPLICATIONS – AMPLIFIER COMBINING

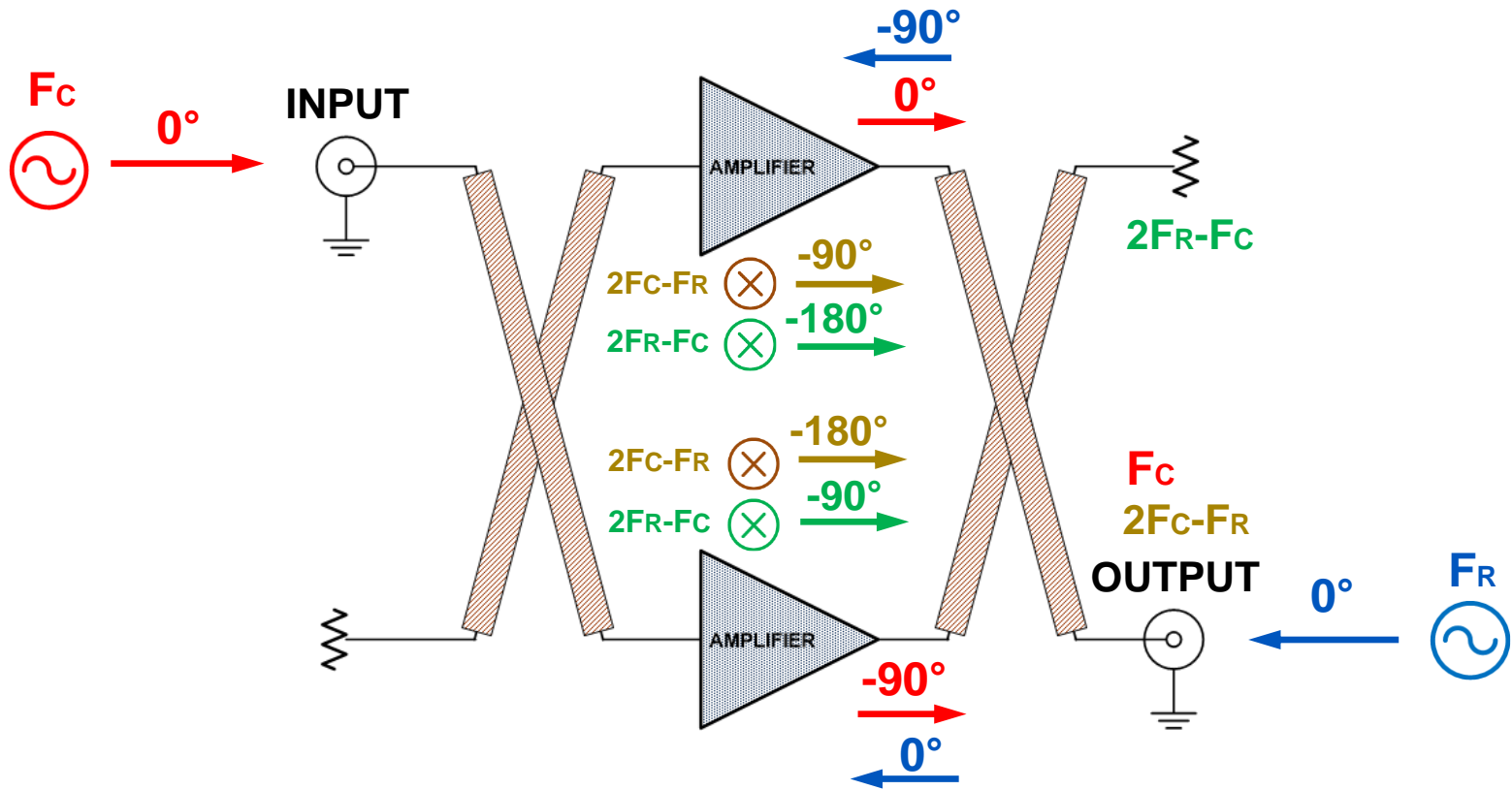

⑤ Reverse IMD:  $2F_R - F_c$  is sent to the output isolate termination. Reverse IMD:  $2F_c - F_R$  is sent to the output Port. Conclusion: some reverse IMD is suppressed.

## APPLICATIONS – AMPLIFIER COMBINING

- Both amplifier total phase shift is through hybrids is  $-90^\circ$ .
- Input and output reflection from each amplifier is sent to the isolate termination: VSWR of the pair is 1:1.
- Load mismatch is applied differently (by  $180^\circ$ ) to the amplifiers. This desensitizes the pair.
- Multiple reflections due to amplifier output mismatch are terminated in the isolate load.
- Reverse IMD performance is improved.

# SUMMARY

- Quadrature hybrids offer many advantages
- They are realized with -3 dB directional couplers or with branch-line structures.
- Lange couplers provides superior performance in microstrip media
- Applications include one port devices circuits (negative resistance amplifiers, phase shifters, and attenuators) and two port amplifiers.

# Questo E' Tutto

