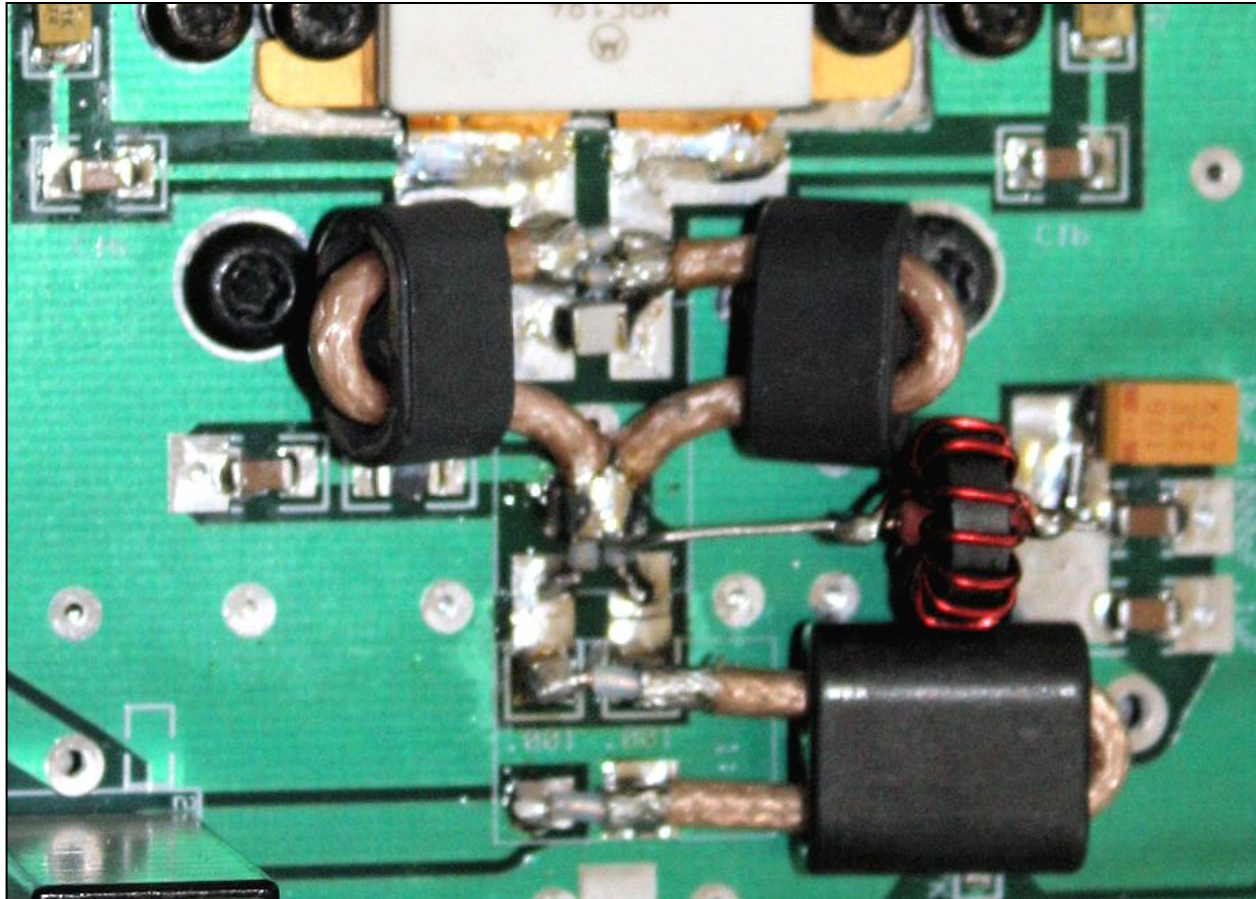


# Transmission-Line Transformers




**K5TRA**

# Categories of Transmission-Line Transformers


- Single  $\lambda/4$  lines and cascades of  $\lambda/4$  lines
- Distributed element approximations of lumped element (LC) designs
- Short, highly coupled unit element structures
  - Ruthroff
  - Guanella
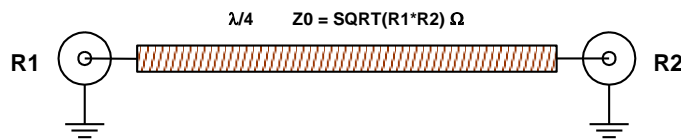
# $\frac{1}{4} \lambda$ and Stepped $\frac{1}{4} \lambda$ Transformers



- Half octave performance from single quarter-wave line transformer
- Nearly 2-octave performance from 3 stepped quarter-wave lines
- Comparison for  $50\Omega$  to  $100\Omega$  transformation (BW also depends on this)




$\frac{1}{4} \lambda$  Z INVERTER

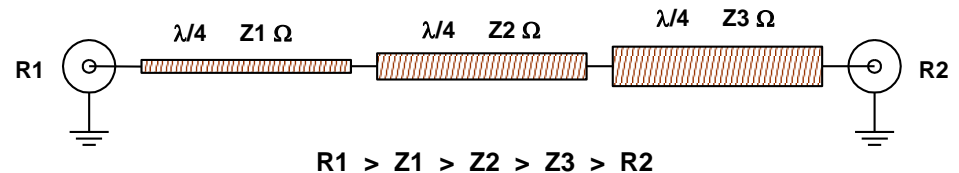

STEPPED Z TRANSFORMER

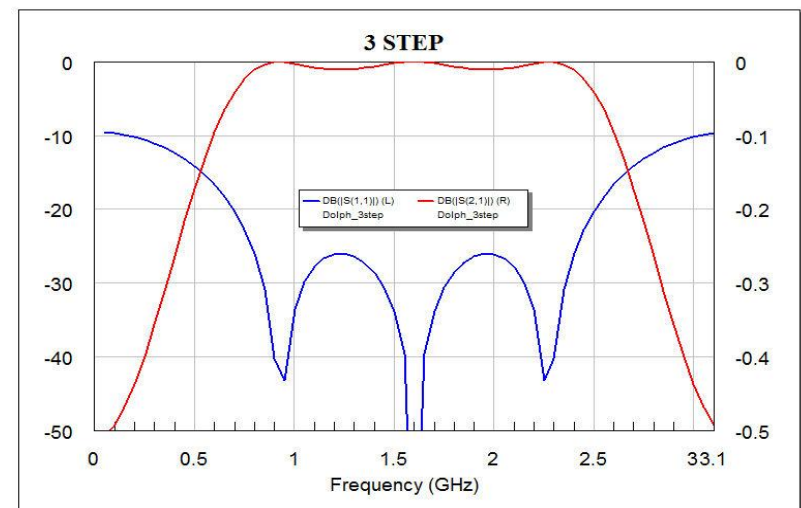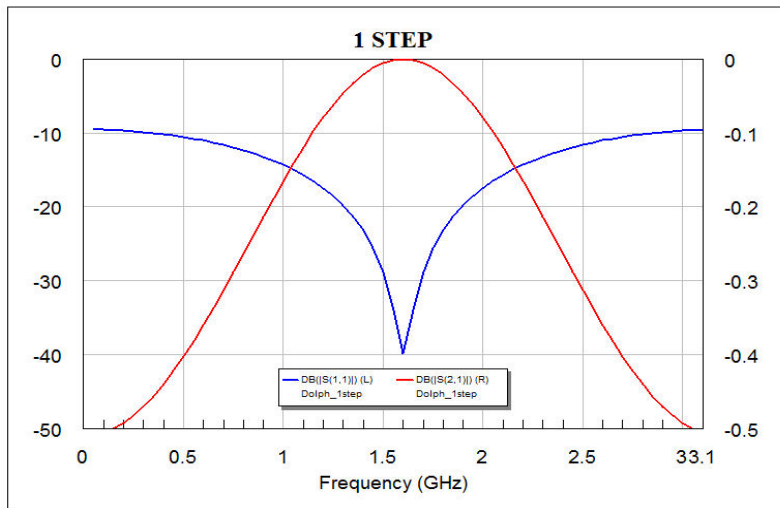
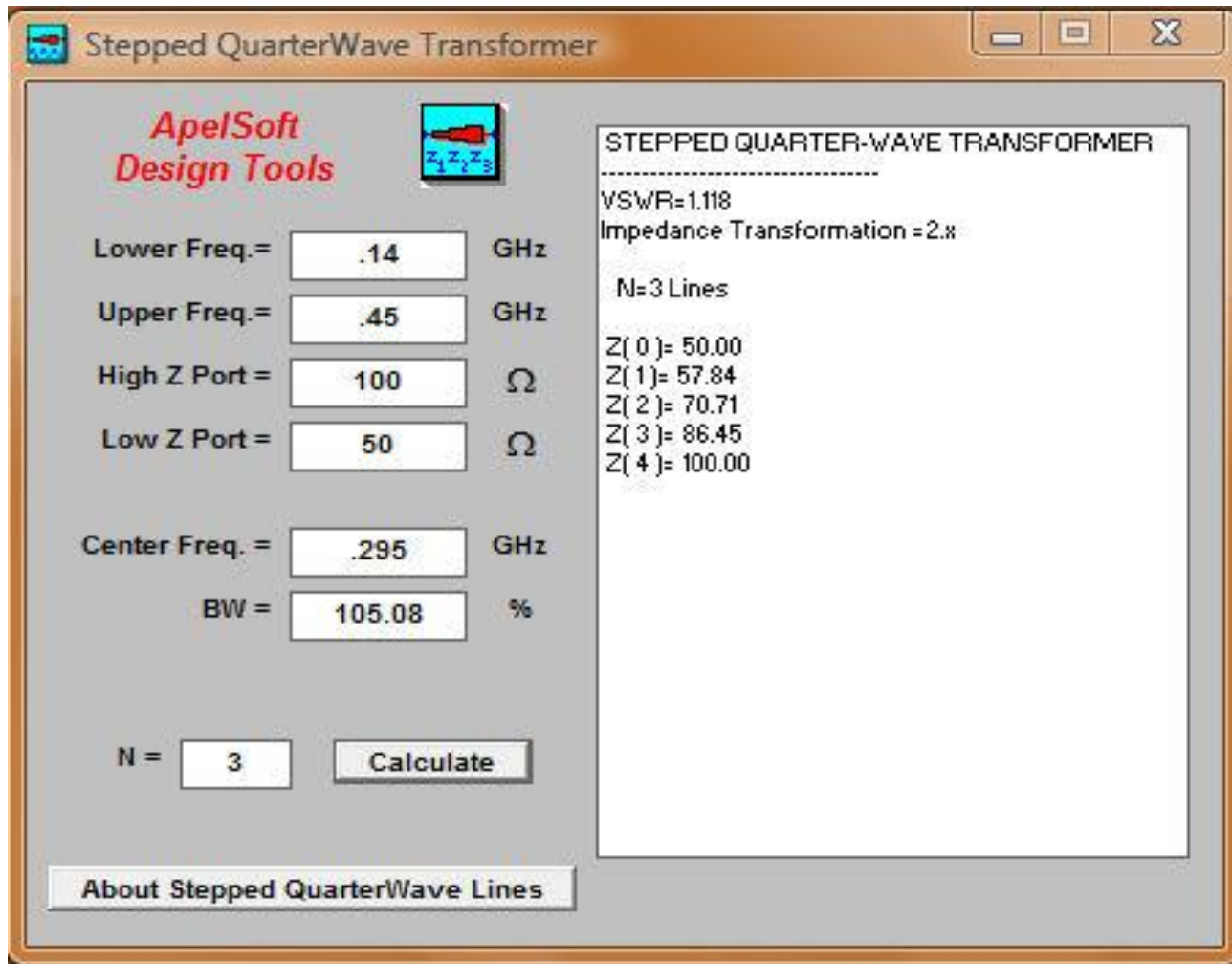
# Stepped $\frac{1}{4} \lambda$ Transformer Calculation



**ApelSoft  
Design Tools**

Lower Freq. =  GHz

Upper Freq. =  GHz

High Z Port =   $\Omega$

Low Z Port =   $\Omega$

Center Freq. =  GHz

BW =  %

N =

[About Stepped QuarterWave Lines](#)


```
STEPPED QUARTER-WAVE TRANSFORMER
-----
VSWR=1.118
Impedance Transformation = 2.x

N=3 Lines

Z( 0 )= 50.00
Z( 1 )= 57.84
Z( 2 )= 70.71
Z( 3 )= 86.45
Z( 4 )= 100.00
```


DOWNLOAD FROM: <http://k5tra.net/>
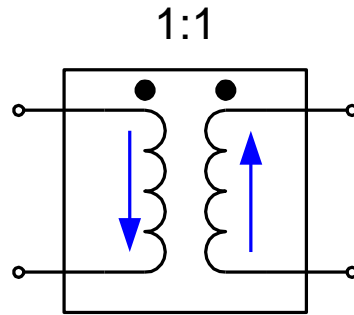
# Transmission-Line Transformer – Elements




CONVENTIONAL  
TRANSFORMER

=

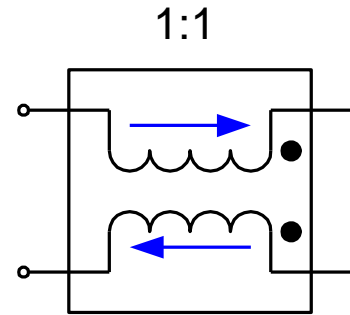


TRANSMISSION-LINE  
TRANSFORMER

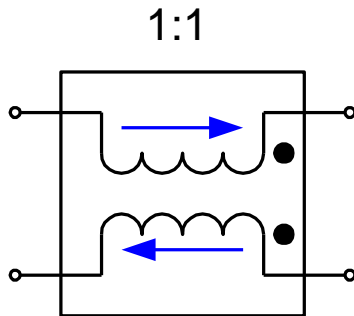

SYMBOLIC


=

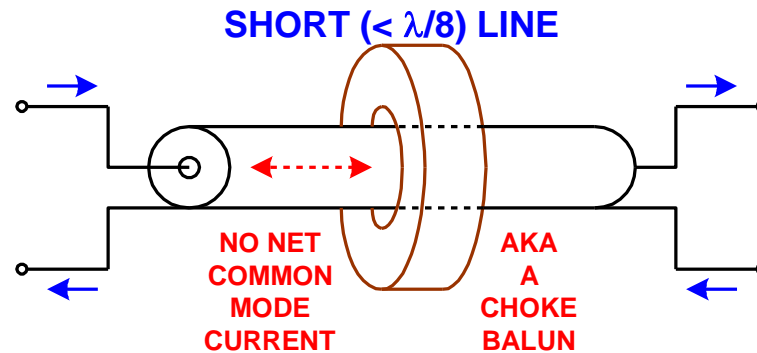

PHYSICAL

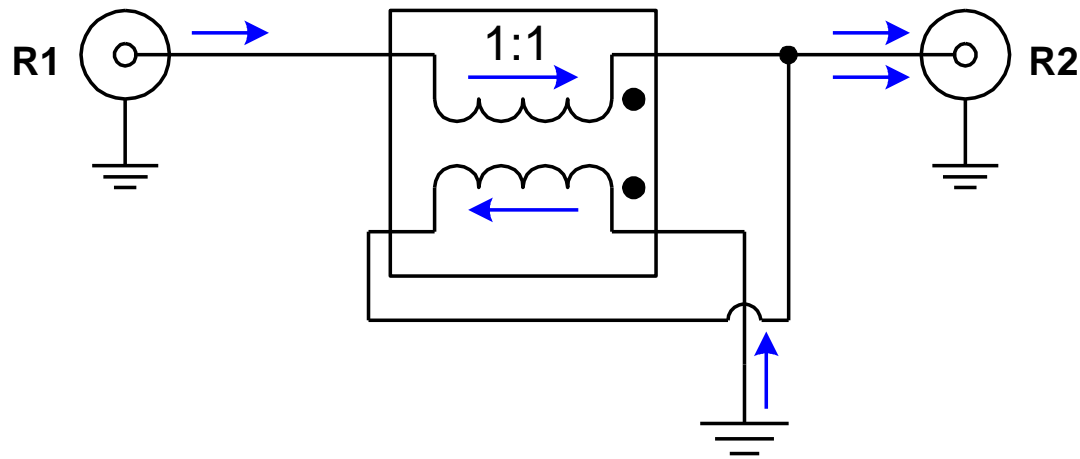
# Ruthroff Transformers

- Transmission line 'unit' element
- Physically short lines (length  $< \lambda / 8$ )
- Analysis based on currents
- $R_1 / R_2 = (I_2 / I_1)^2 = 4$
- Ferrite loading extends bandwidth (low end)



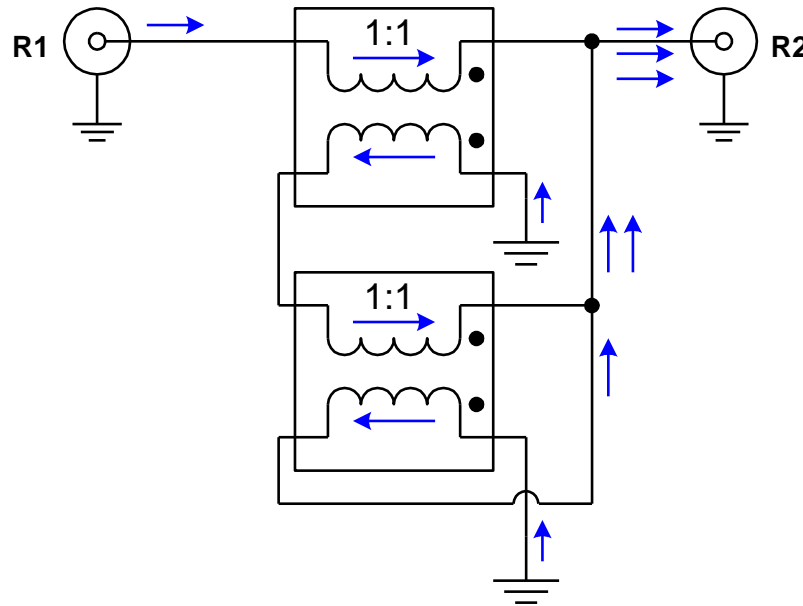
# Ruthroff Type 9:1 Transformer

- Transmission line 'unit' elements
- Physically short lines (length  $< \lambda / 8$ )
- Analysis based on currents
- $R_1 / R_2 = (I_2 / I_1)^2 = 9$
- Ferrite loading extends bandwidth (low end)


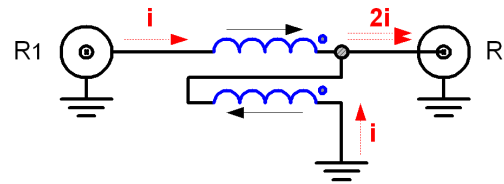
# Various Unbalanced Transformers


- Transmission line unit element building blocks
- Parasitic even mode characteristic impedance should be large ( $k \rightarrow 1$ )
- Z ratio available as squares of integer ratios
- First order analysis on basis of port current ratio
- Multiple line structures must have at least one shared current path
- DC path is present



$$i^2 R_1 = (2i)^2 R_2$$

$$R_1 = 4 R_2$$


**4:1 Transformer**

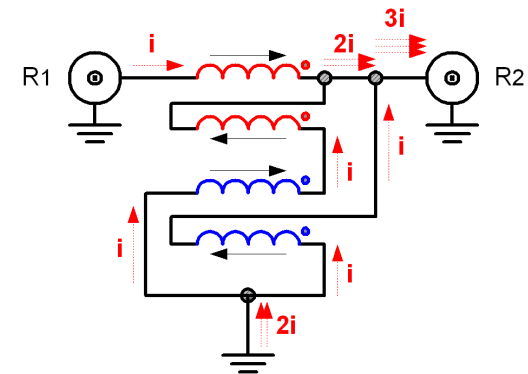

$$i^2 R_1 = (3i)^2 R_2$$

$$R_1 = 9 R_2$$


**9:1 Transformer  
version - A**

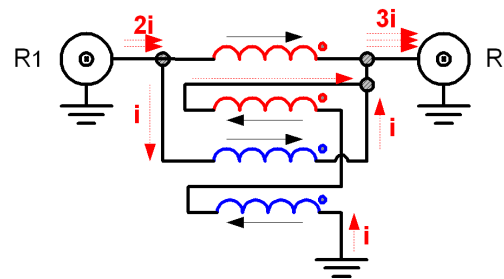

$$(2i)^2 R_1 = (3i)^2 R_2$$

$$R_1 = 4 R_2$$

**4:9 Transformer  
(approx. 1:2)**

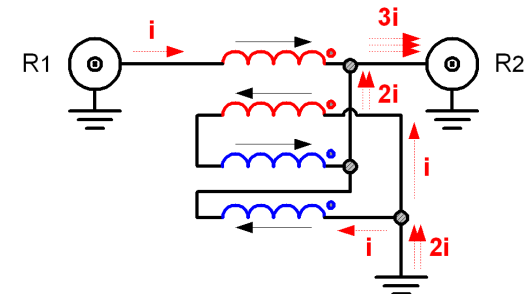

$$i^2 R_1 = (3i)^2 R_2$$


$$R_1 = 9 R_2$$

**9:1 Transformer  
version - B**



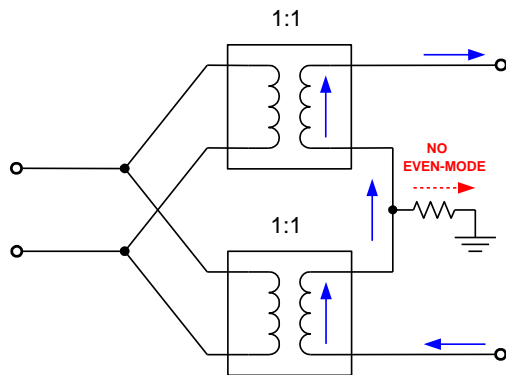
# Guanelle (4:1) Balanced Transformer


- Two 'unit' elements can be used to form a balanced 4:1 transformer
- Analysis based on currents
- $R_1 / R_2 = (I_2 / I_1)^2 = 4$
- Ferrite loading extends bandwidth (low end)



**CONVENTIONAL  
4:1 BALANCED  
TRANSFORMER**

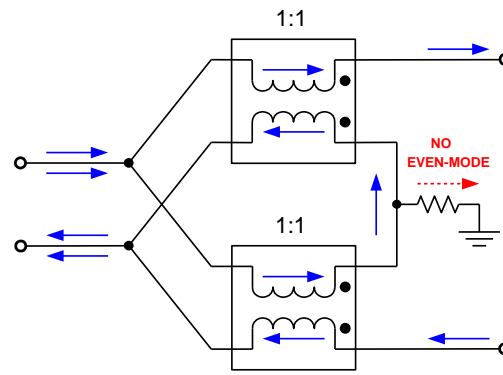


**GUANELLE 4:1  
SYMBOLIC**

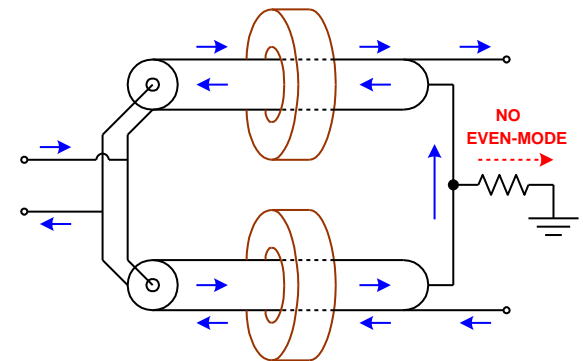

**GUANELLE 4:1  
PHYSICAL**
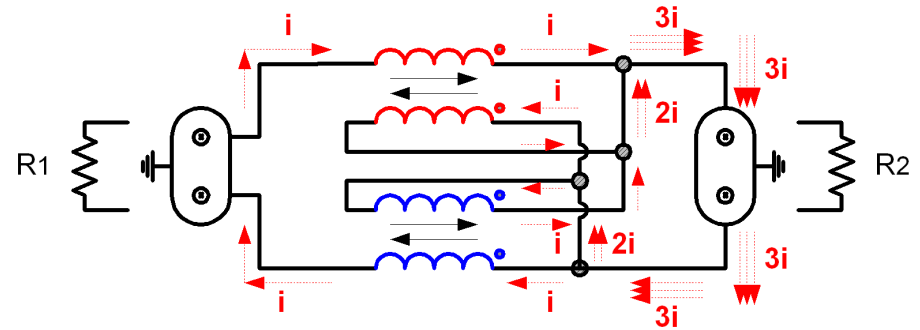
# Several Balanced Transformers


- Transmission line unit element building blocks
- Parasitic even mode characteristic impedance should be large ( $k \rightarrow 1$ )
- Z ratio available as squares of integer ratios
- First order analysis on basis of port current ratio
- Multiple line structures must have at least one shared current path
- DC path is present



$$i^2 R_1 = (3i)^2 R_2$$

$$R_1 = 9 R_2$$

**9:1 Transformer**

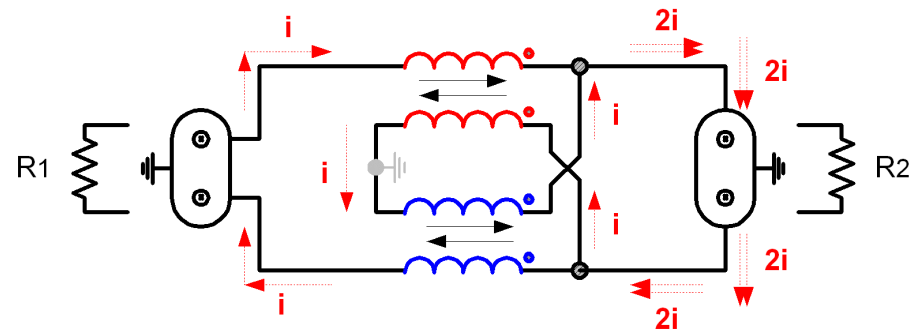


$$i^2 R_1 = (2i)^2 R_2$$

$$R_1 = 4 R_2$$



**4:1 Transformer**
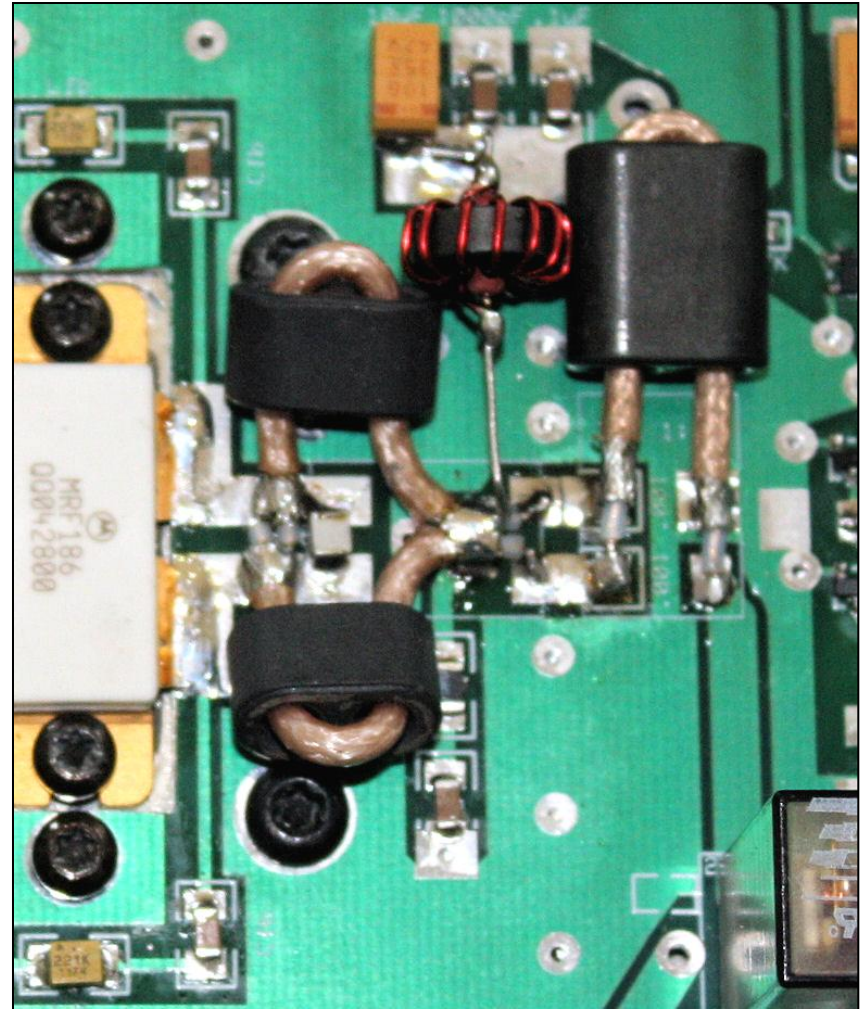
# Guanella Transformer and Choke Balun

- Pushpull PA match example
- Ferrite loaded 'unit' elements
- Guanella transformer from coax
- Choke balun (1:1) from coax



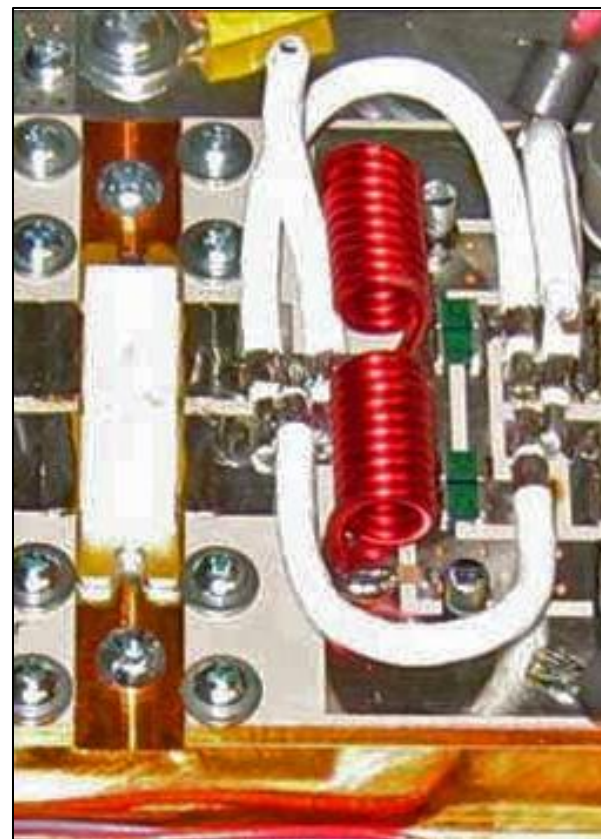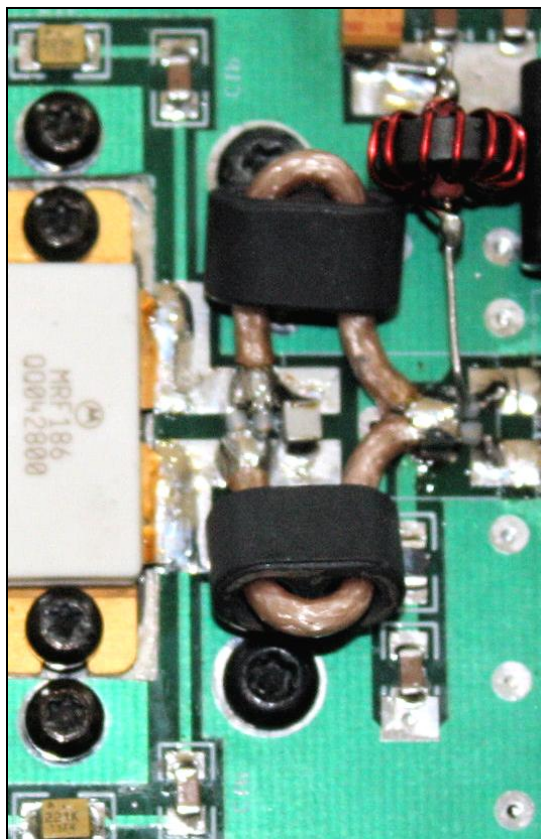
# More Guanella Transformers in PA Output



- Guanella transformer from coax
- 'Unit' elements with and without ferrite loading
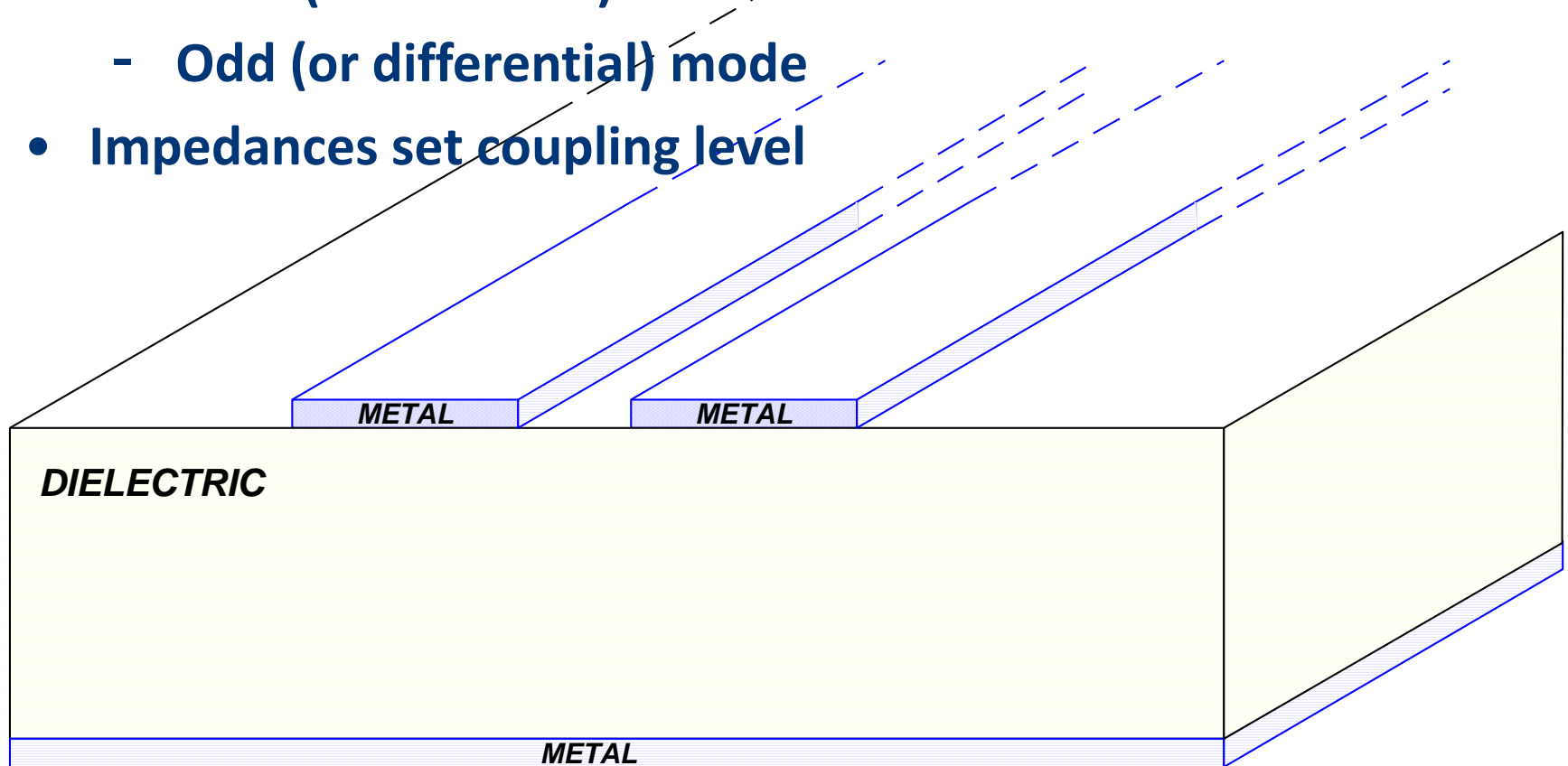
# Coupled Lines - Symmetric

- Two transmission-line modes
  - Even (or common) mode
  - Odd (or differential) mode
- Impedances set coupling level



# Coupling Coefficient

$$Z_{oe}/Z_{oo} = (C+2C_M)/C$$

$$k = \frac{Z_{oe}/Z_{oo} - 1}{Z_{oe}/Z_{oo} + 1}$$


$$k = \frac{C_M}{C_M + C}$$

$$k = \frac{C_M}{C_M + C} = \frac{\frac{C_M}{C}}{\frac{C_M}{C} + 1}$$

$$Z_{oe}/Z_{oo} \rightarrow \infty \Rightarrow K \rightarrow 1$$

$$C_M/C \rightarrow \infty \Rightarrow K \rightarrow 1$$

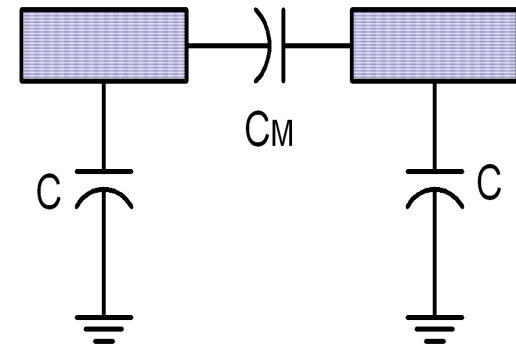- $Z_{oo}$  sets the desired  $Z_o$
- $Z_{oe}$  should be large !




STATIC CAPACITANCE  
REPRESENTATION FOR  
SYMMETRIC STRUCTURES



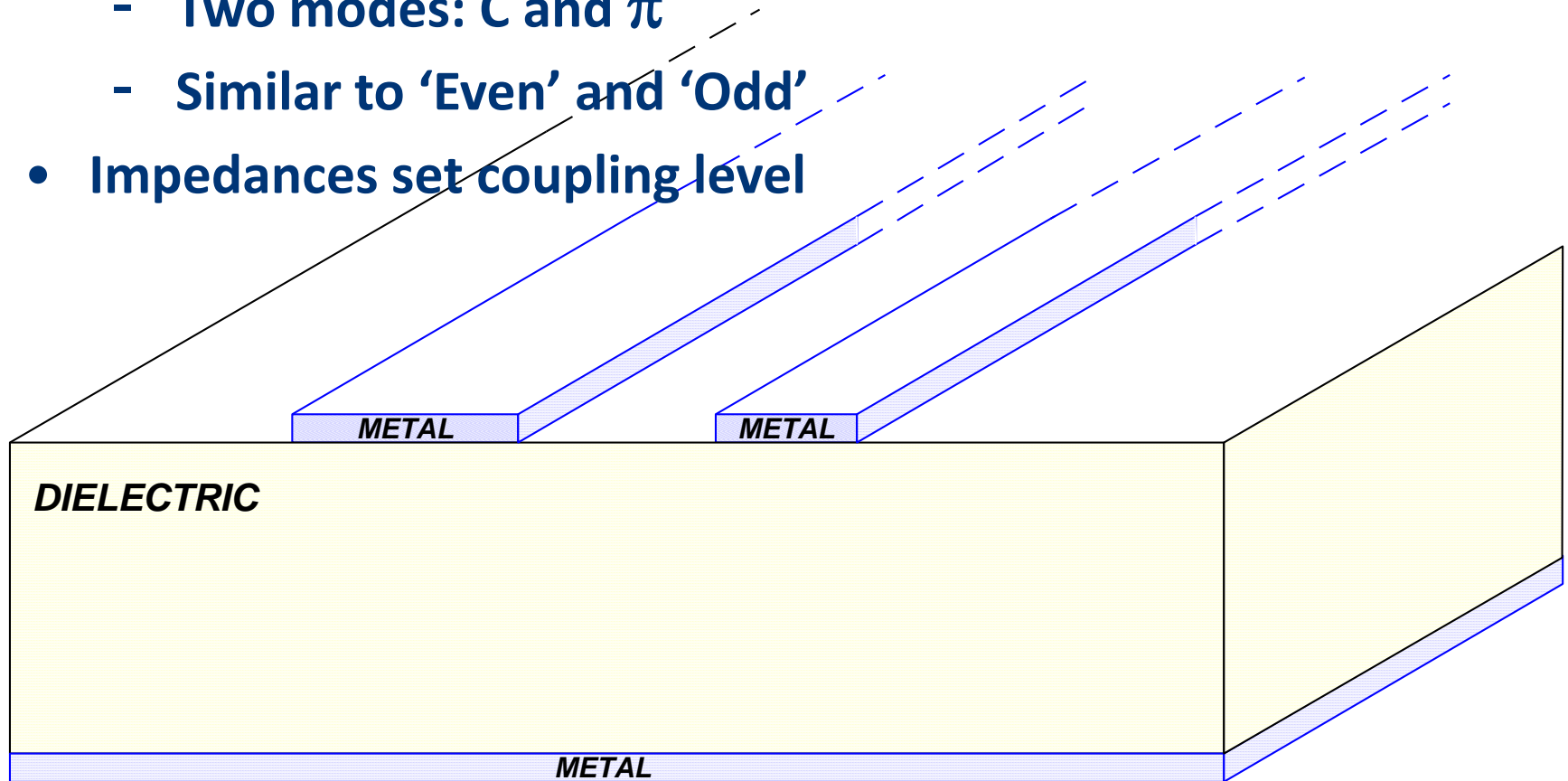
# Coupled Lines - Asymmetric

- Asymmetric coupled lines
  - Two modes:  $C$  and  $\pi$
  - Similar to 'Even' and 'Odd'
- Impedances set coupling level


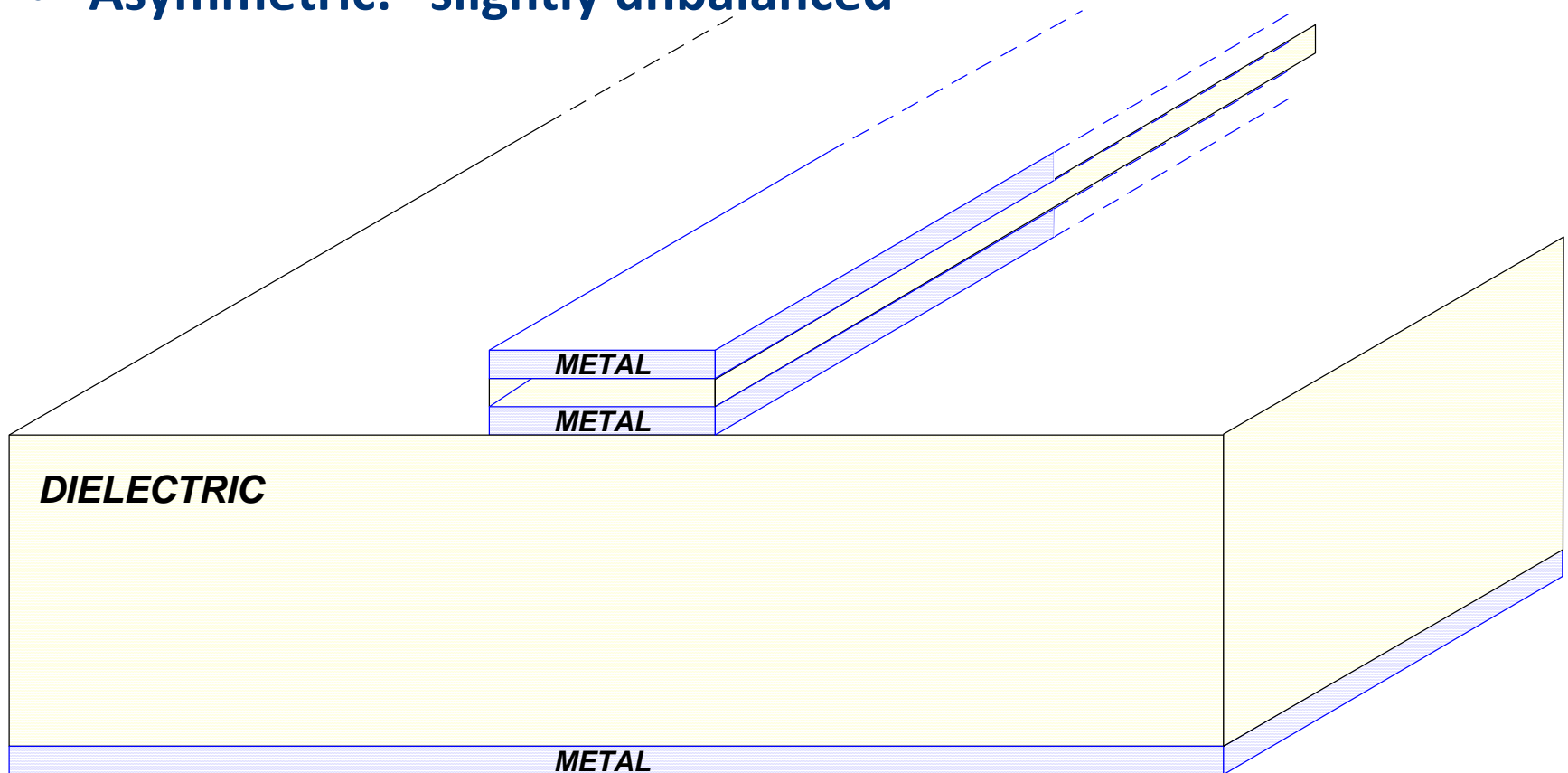
# Coupled Lines - Asymmetric


- Broadside coupling is better
- Asymmetric: slightly unbalanced





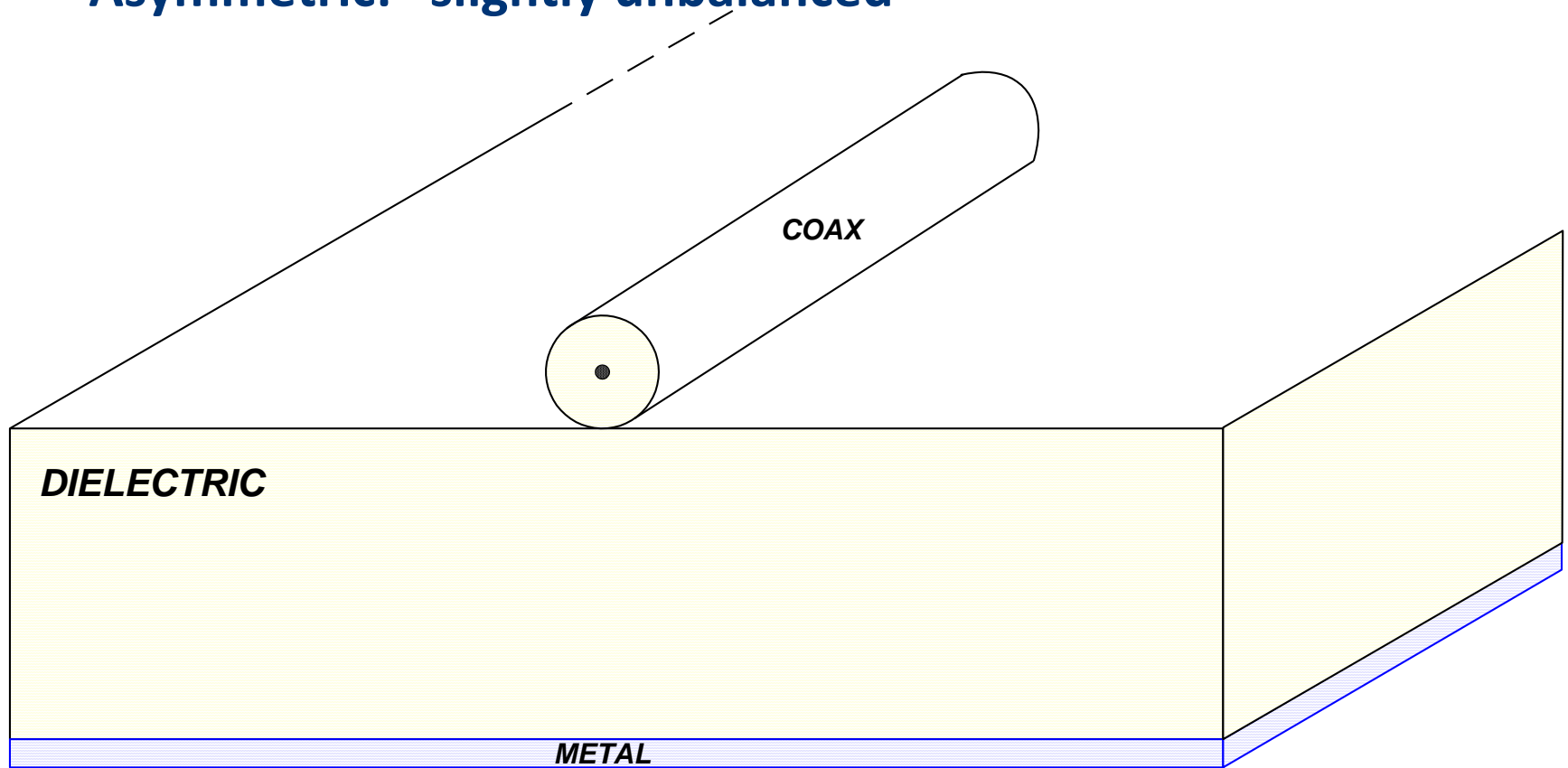
# Coax Over Ground


- Coax coupling is very good
- Asymmetric: slightly unbalanced




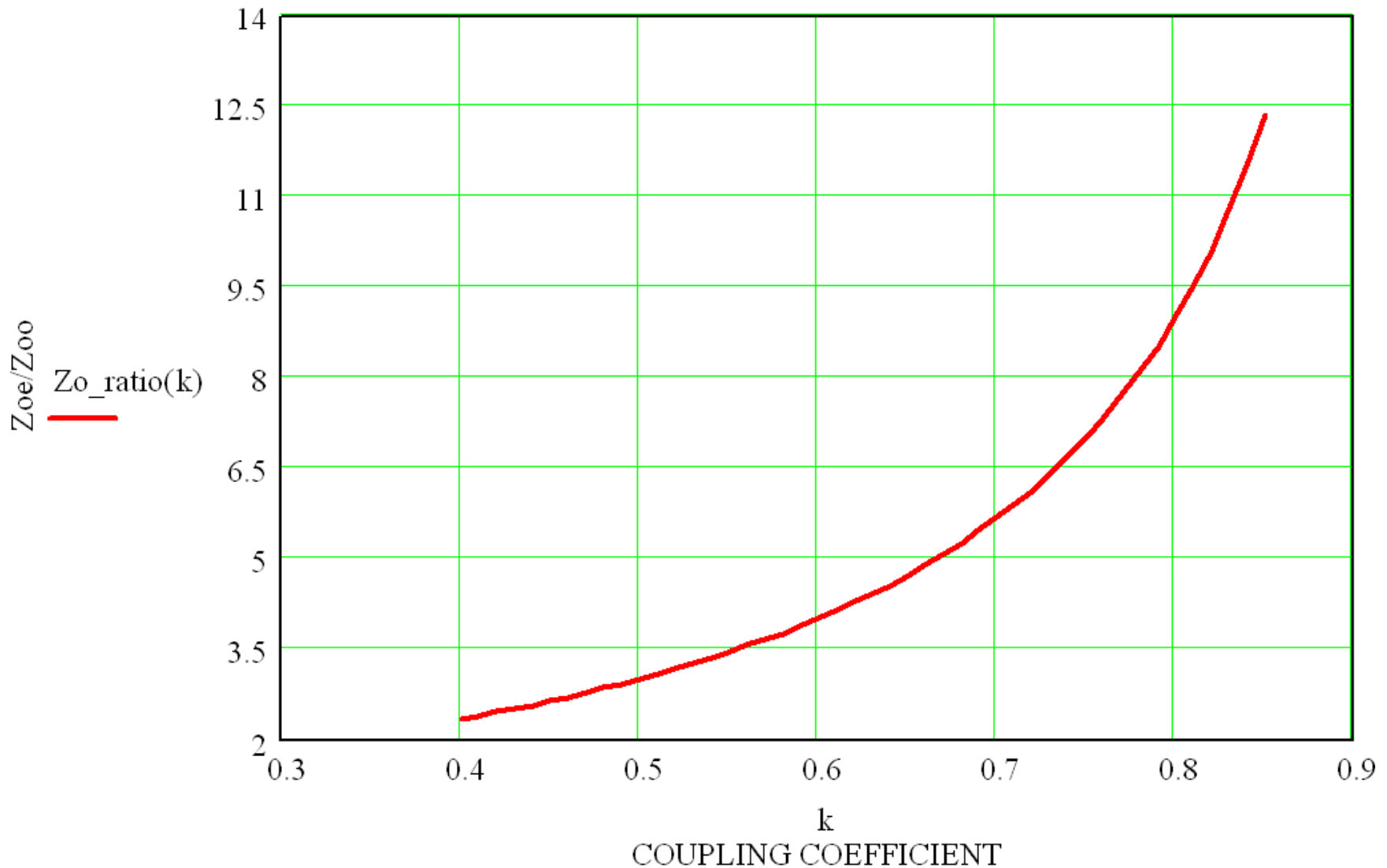
# Coupling Coefficient Relationship to $Z_{oe}/Z_{oo}$


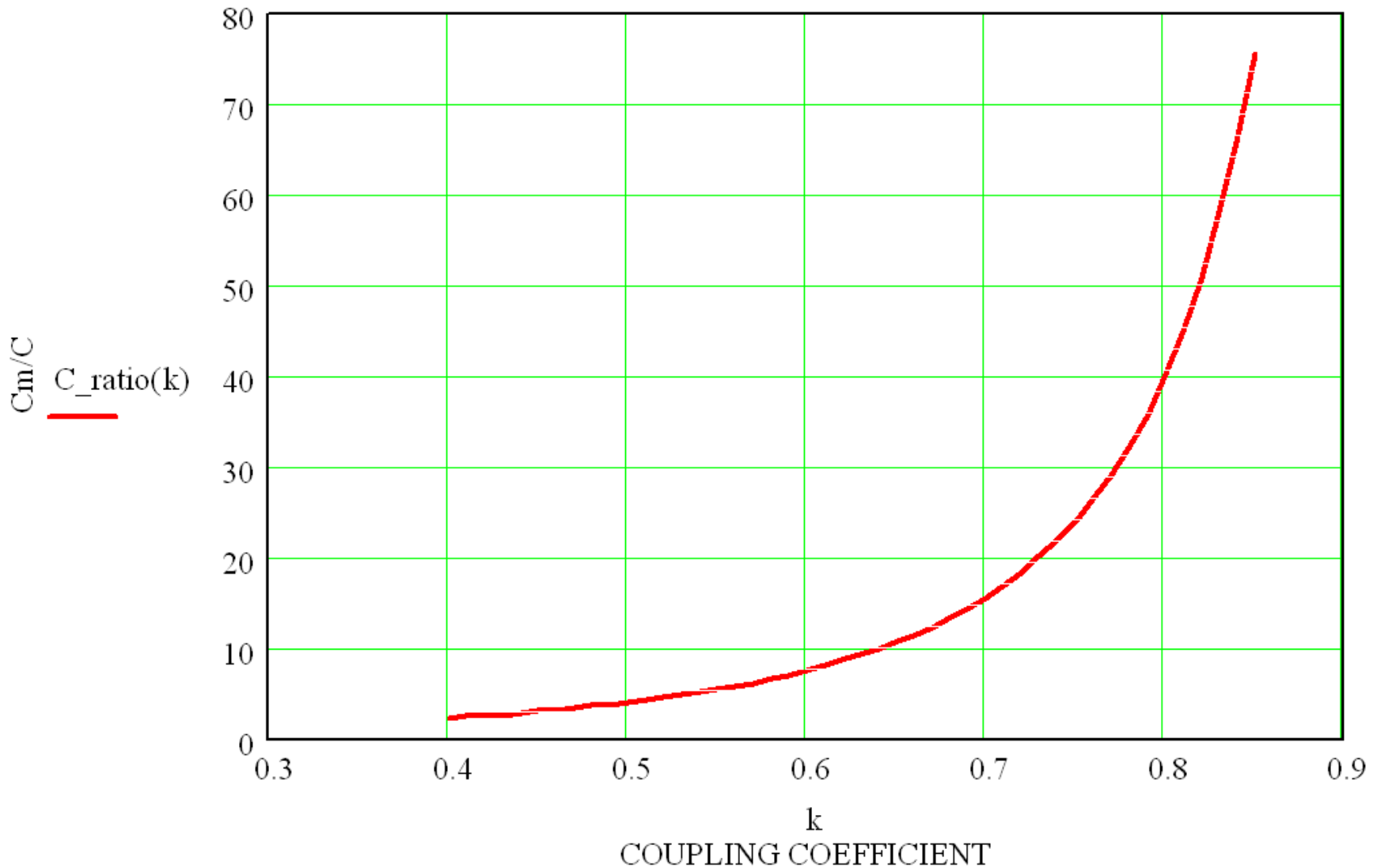
# Coupling Coefficient Relationship to $C_m/C$




# Ideal Ruthroff Loss vs Length (and Zo)

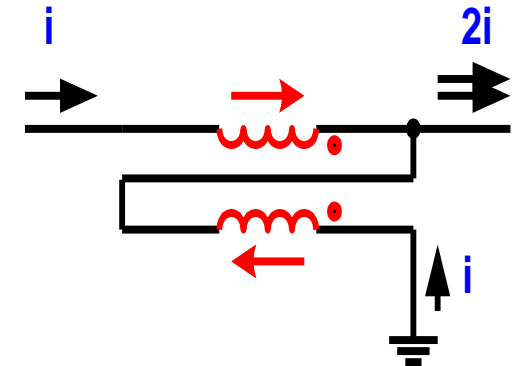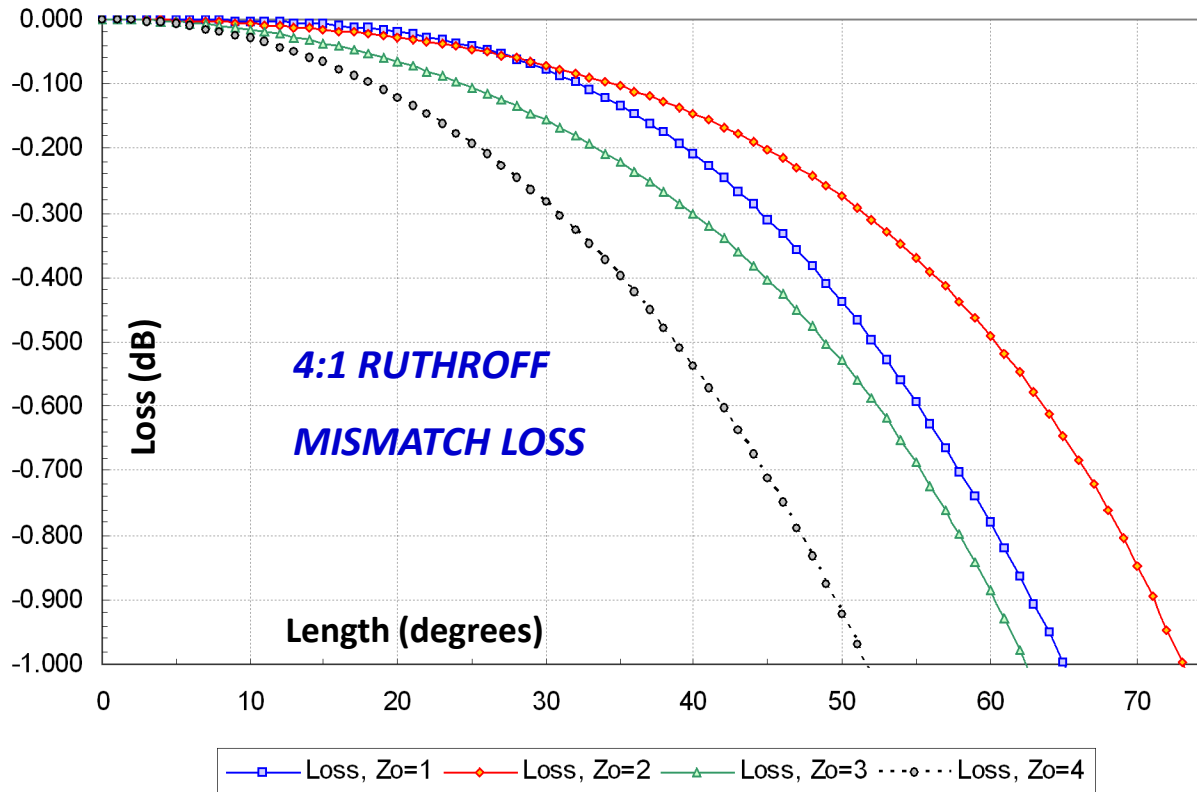


- Analysis of original 4:1 Ruthroff transformer ( $k = 1$ )
- Normalized port impedances ( $1\Omega$  and  $4\Omega$ )
- Best BW from  $Z_o=2$
- Lowest loss over less BW from  $Z_o=1$


# Ruthroff Loss vs Length (and k)

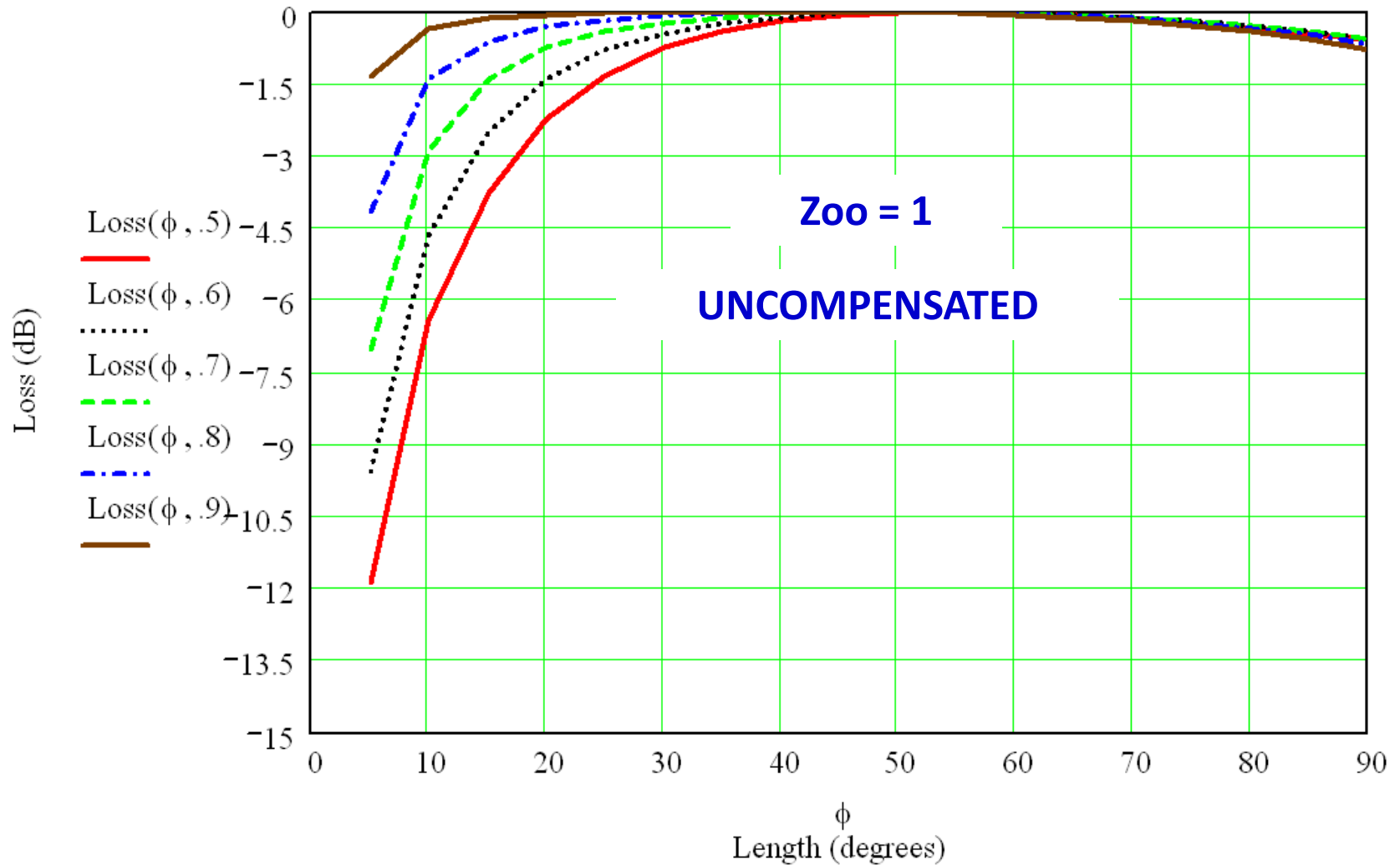

# Ruthroff Loss vs Length (and k)

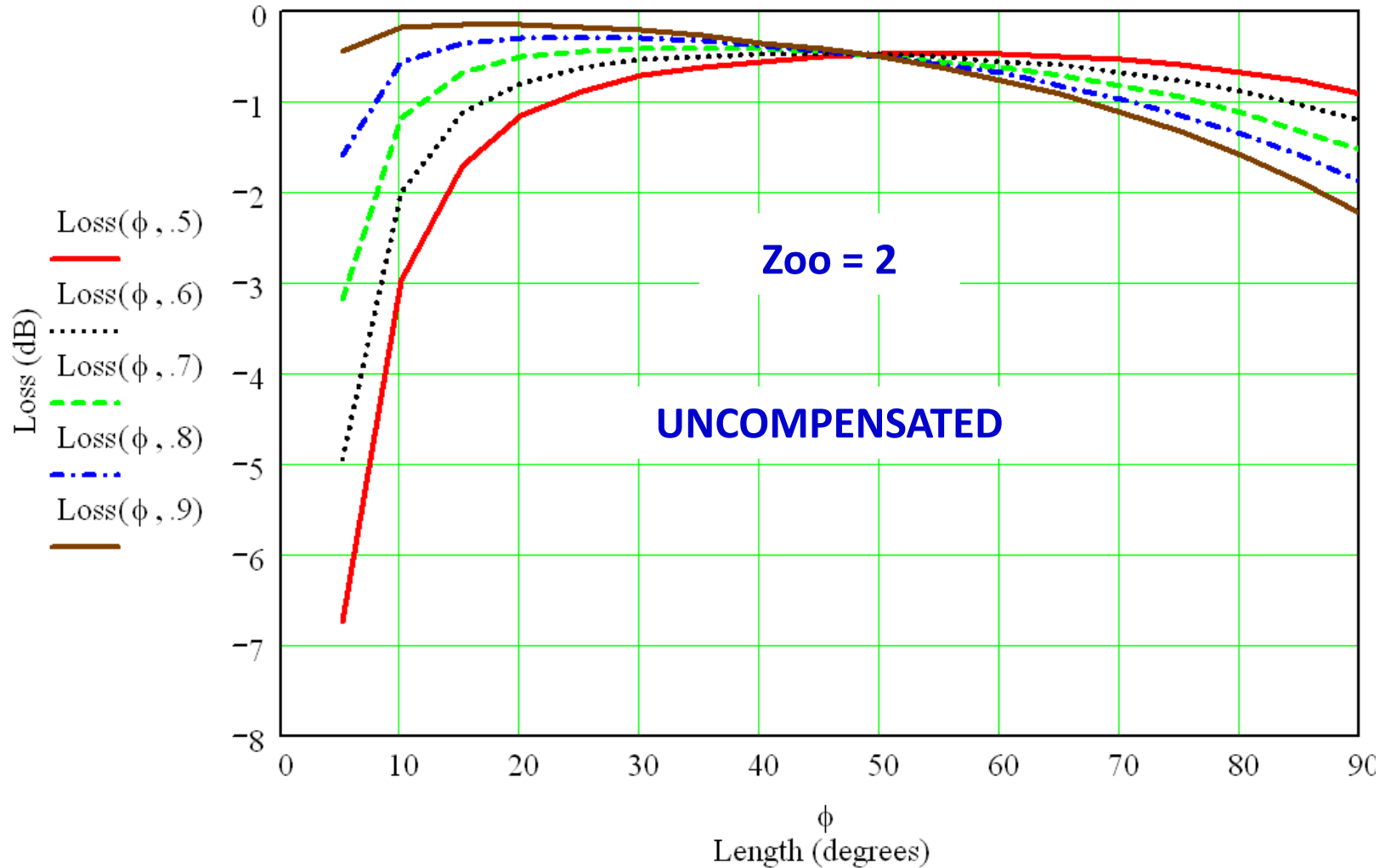


# Ruthroff Loss vs Length (and k)

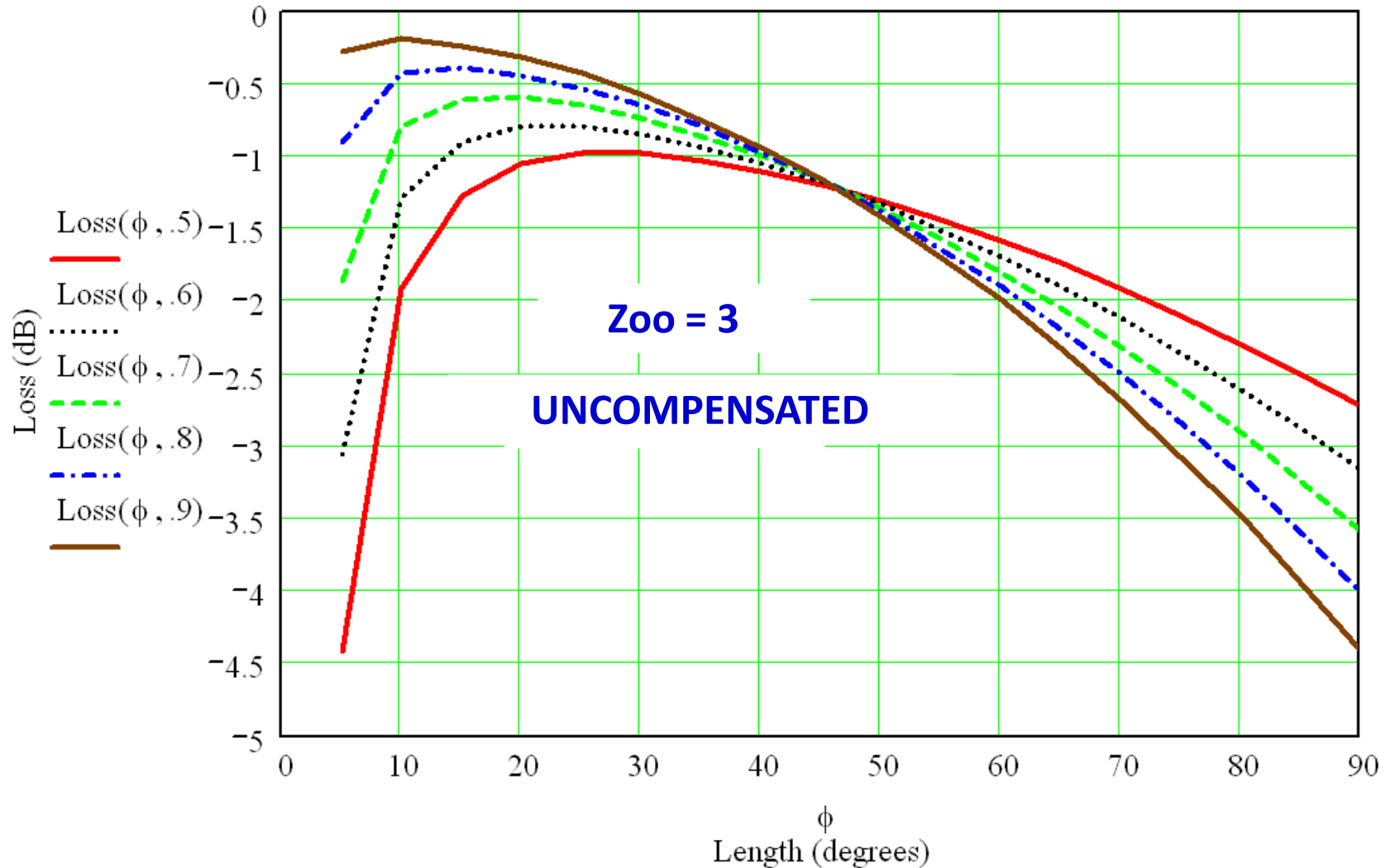

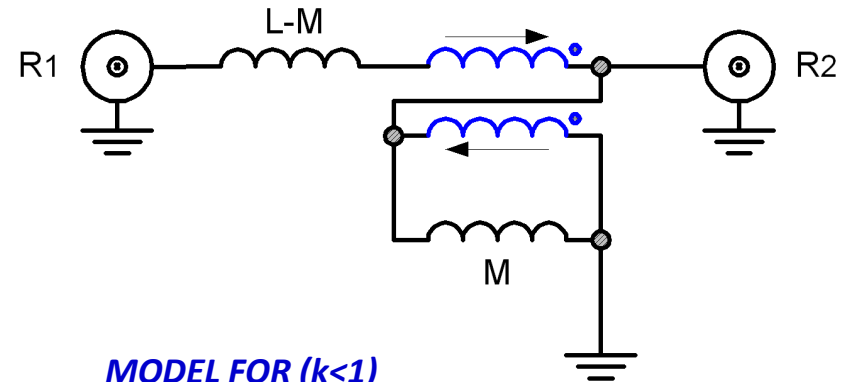
# Ruthroff Transformer Frequency Compensation

- Non-ideal coupling is modeled by leakage and magnetizing inductance
- $C_s$  provides DC block and low frequency compensation
- $CP1$  and  $CP2$  provide high frequency compensation
- If coupling is poor, or  $Z_{oo}$  is not optimal,  $C_p$  can be used to tune the transformer for the desired frequency band



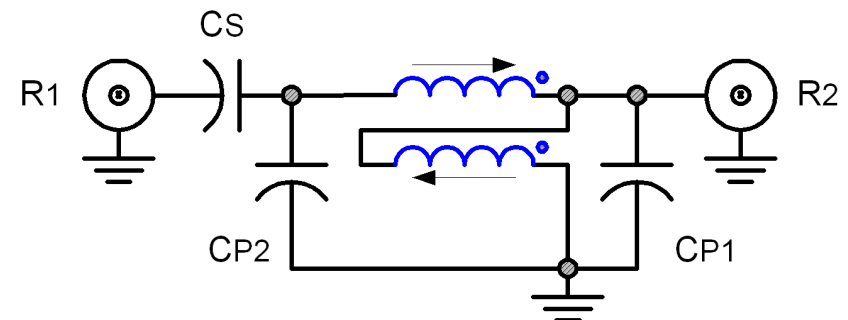
**MODEL FOR ( $k < 1$ )  
UNDERCOUPLED LINES**




**FREQUENCY  
COMPENSATION**




# Ruthroff Loss vs Length (and k)

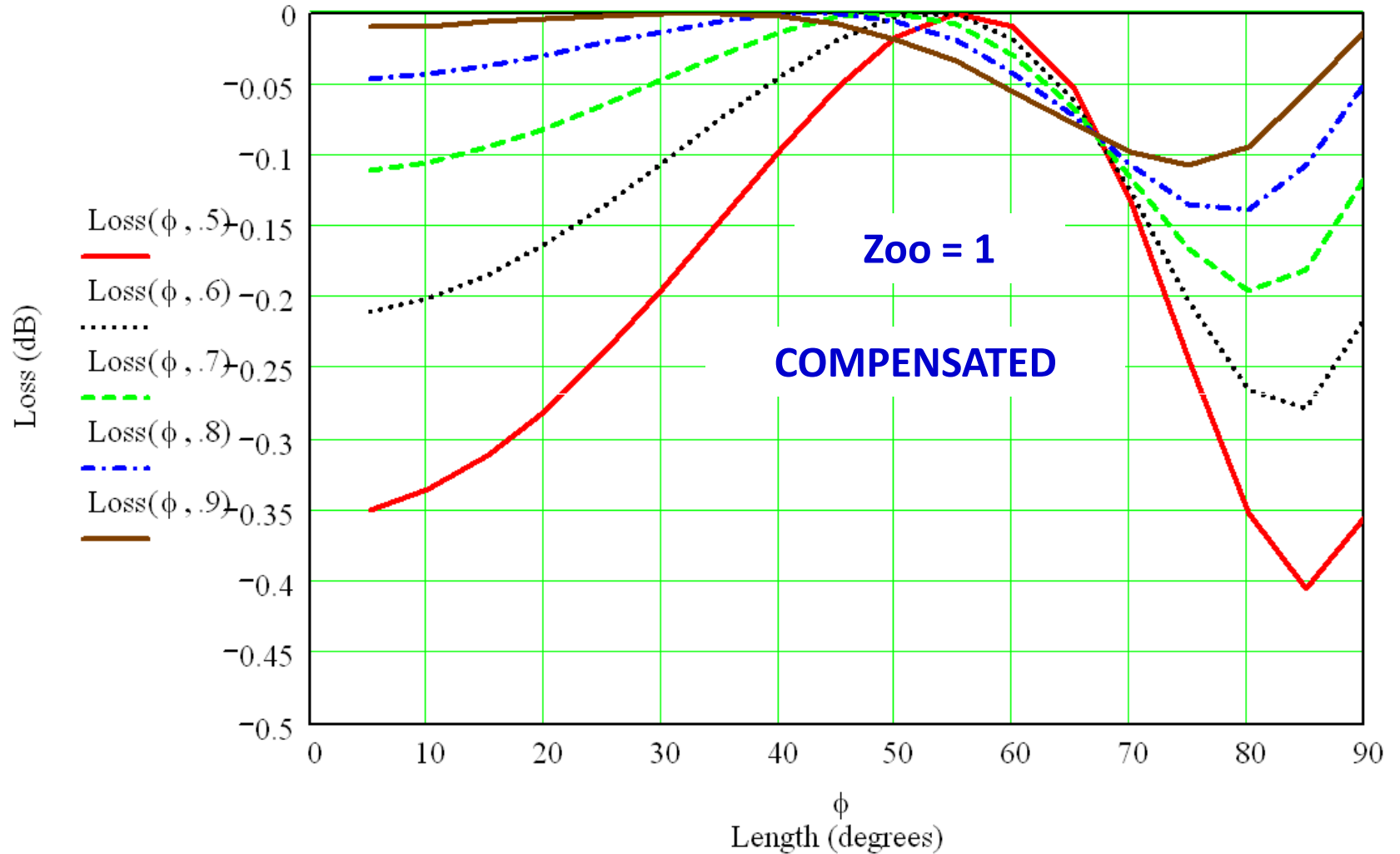


# Ruthroff Loss vs Length (and k)

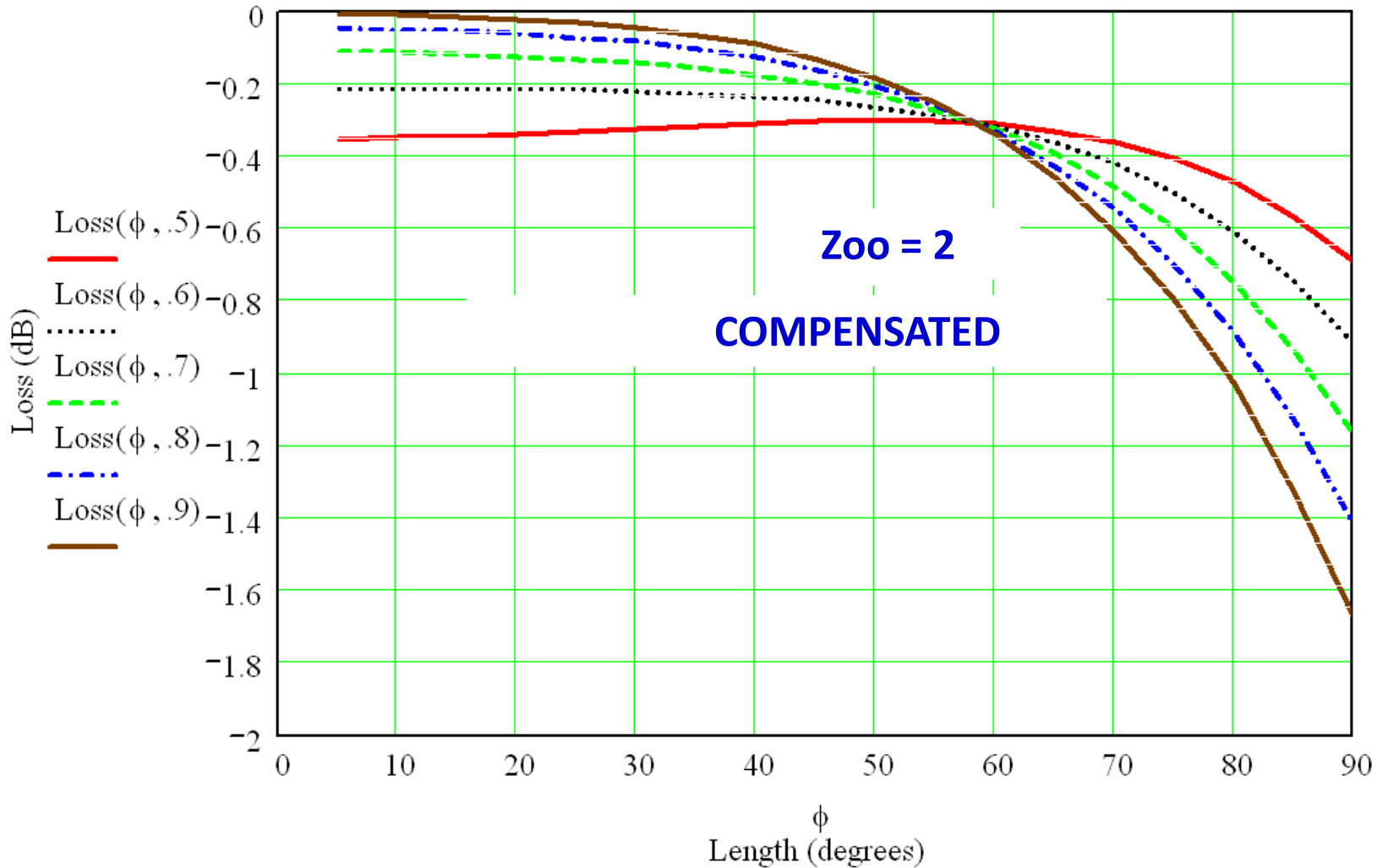

# Ruthroff Loss vs Length (and k)

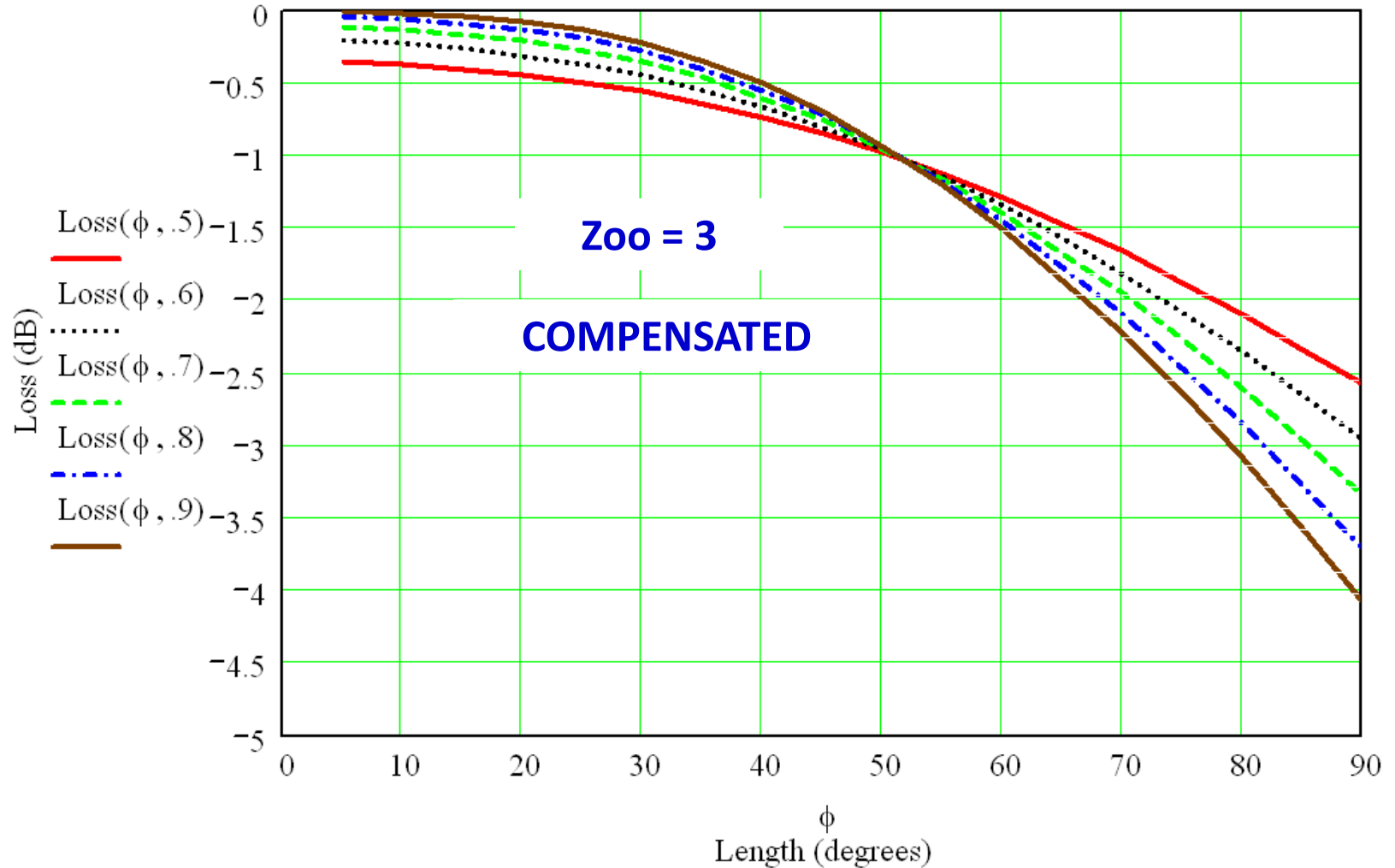

# Ruthroff Transformer Test Laminates

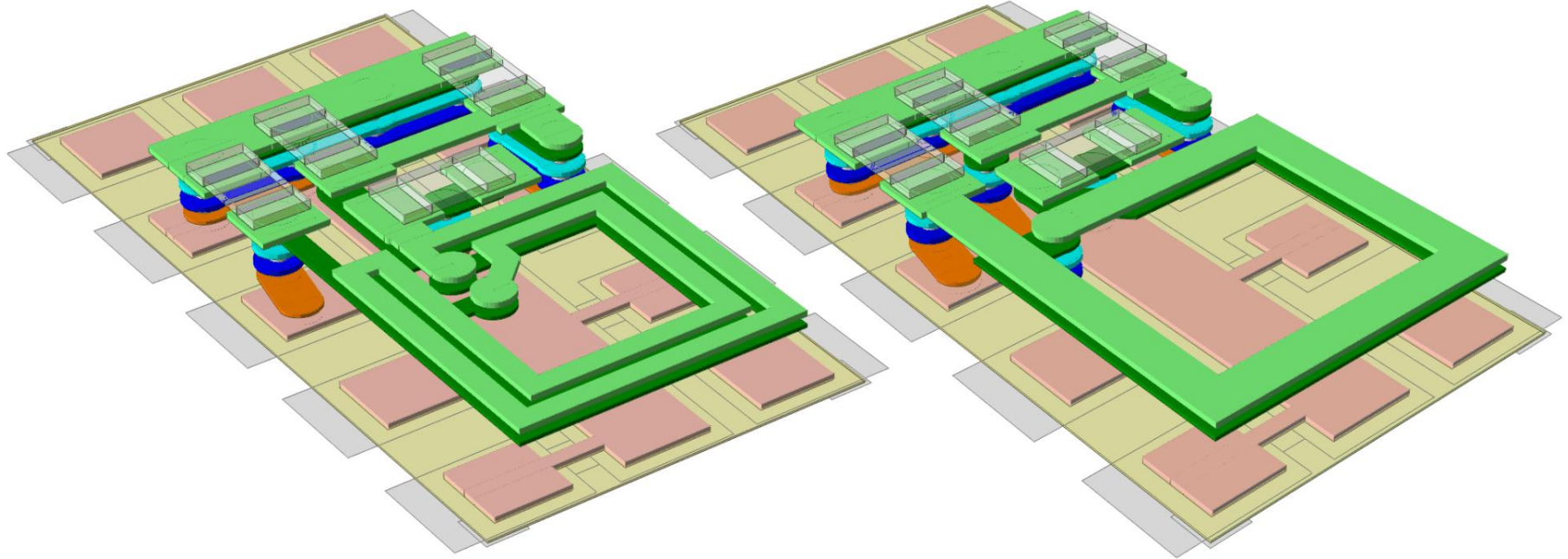


***9:1 TRANSFORMER***


***4:1 TRANSFORMER***

# Flip Chip Multiband PA with Ruthroff 4:1


**RUTHROFF 4:1  
TRANSFORMER**

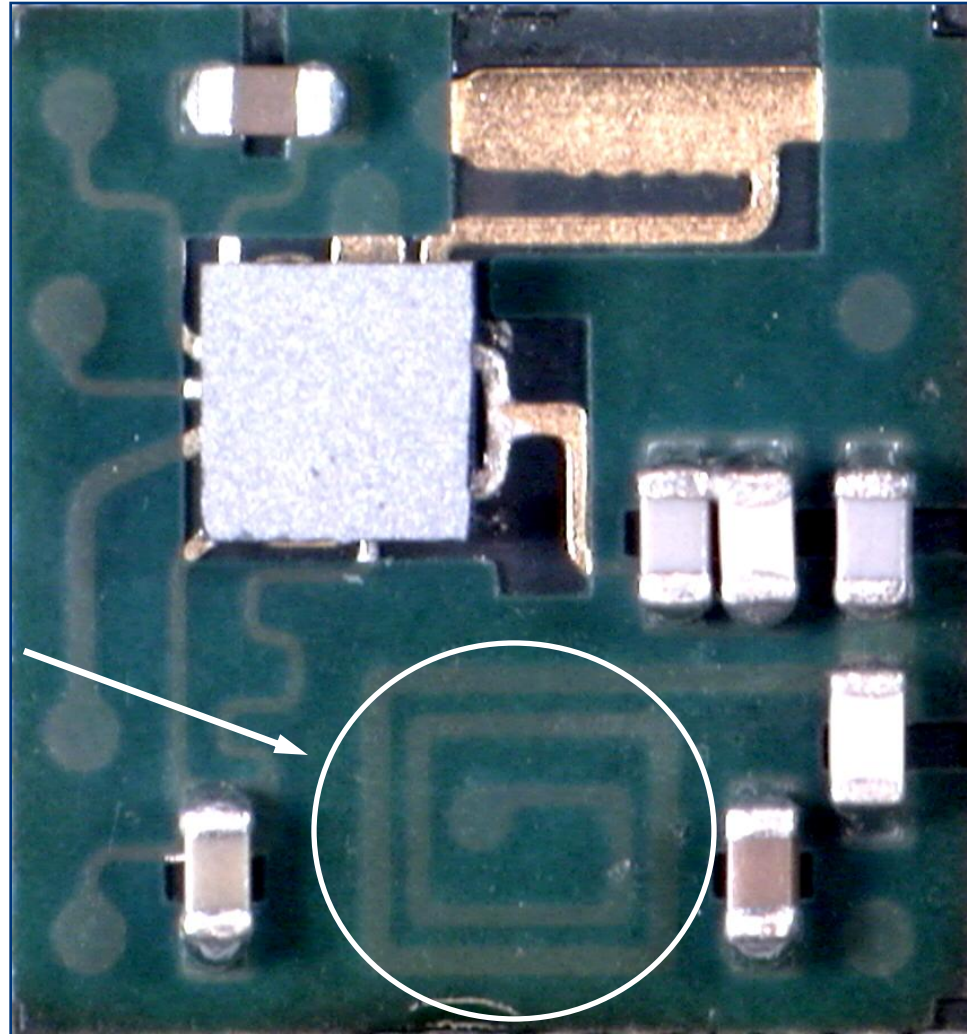


# Ruthroff Relationship to Auto Transformers

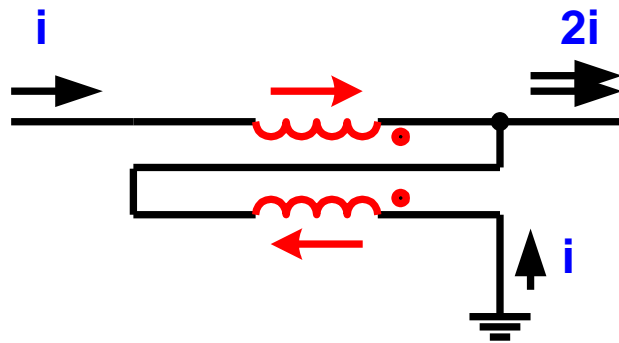

RUTHROFF 4:1  
UNBALANCED TRANSFORMER

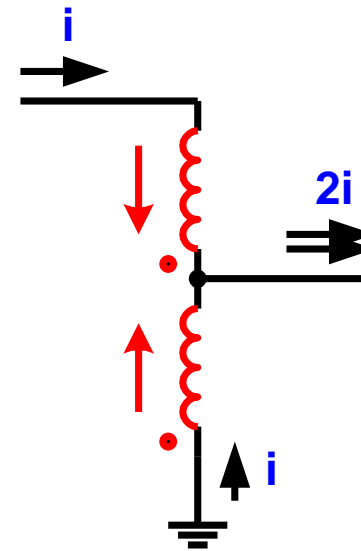

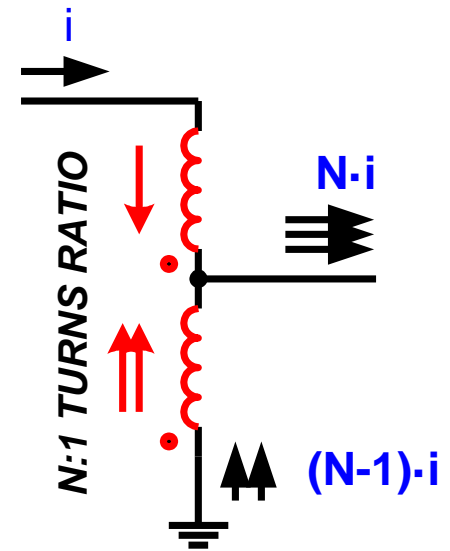
RUTHROFF 4:1  
SHOWN AS AUTO  
TRANSFORMER



GENERAL N:1  
UNBALANCED AUTO  
TRANSFORMER


- The Ruthroff structure can be redrawn as an auto transformer special case ( $N=2$ ).
- Transformation can be set by setting the tap ( $1/N$  is tapped fraction of total primary)

# Guanello Relationship to Auto Transformers

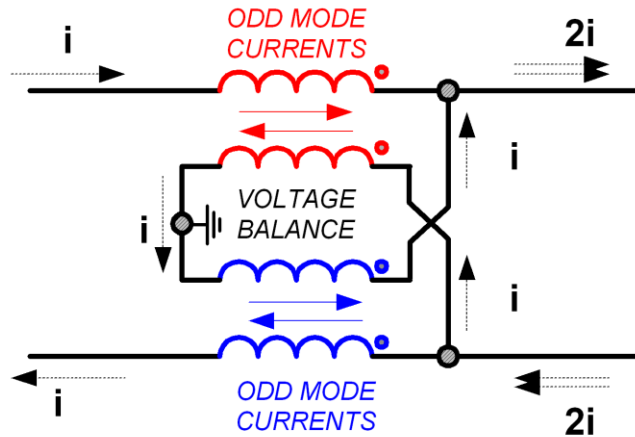


**GUANELLO 4:1 BALANCED TRANSFORMER (BALBAL)**

- The Guanello balanced structure can be redrawn as an auto transformer special case ( $N=2$ ). - note couplings -
- A more general auto transformer has secondary coupled to both primary segments
- Transformation can be set by setting the taps ( $1/N$  is tapped fraction of total primary)

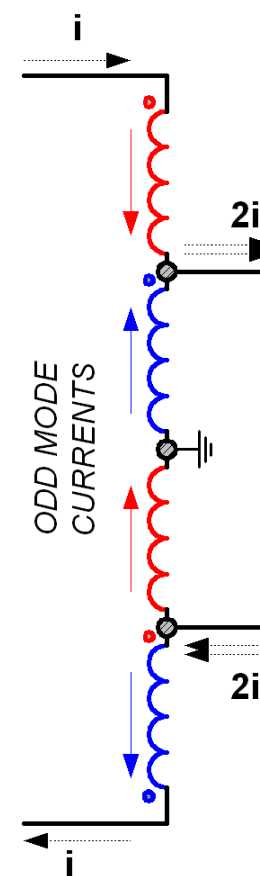


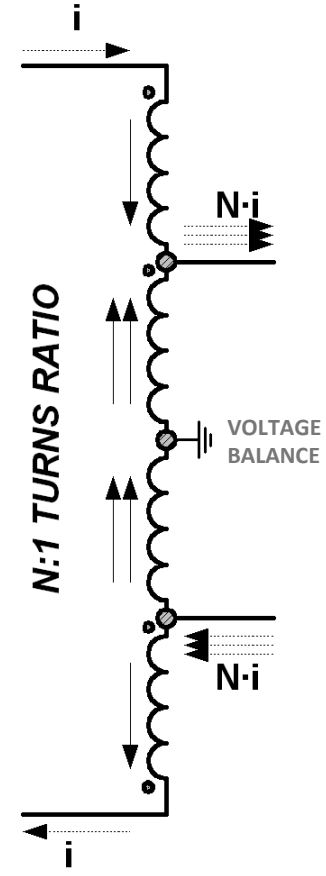**GUANELLO 4:1 SHOWN AS AUTO TRANSFORMER**




**GENERAL N:1 BALANCED AUTO TRANSFORMER**


# Guanella and Auto Transformers

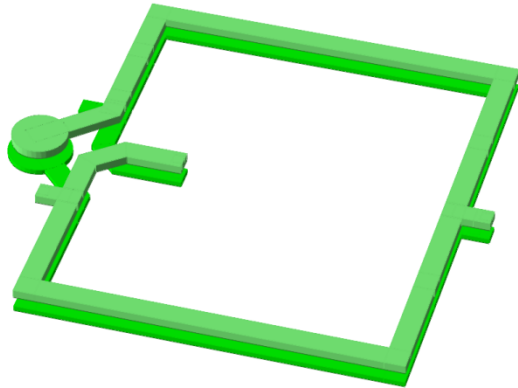

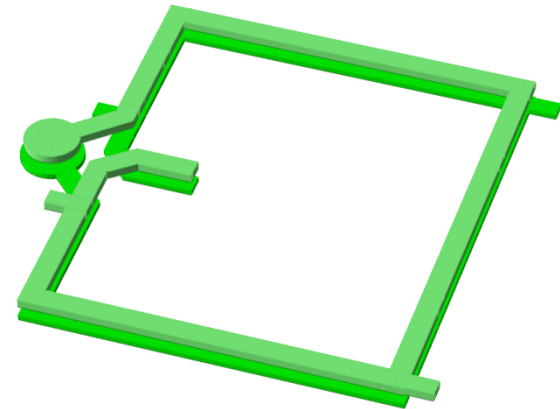**GUANELLA BALANCED TRANSFORMER  
(4:1 BALBAL)**




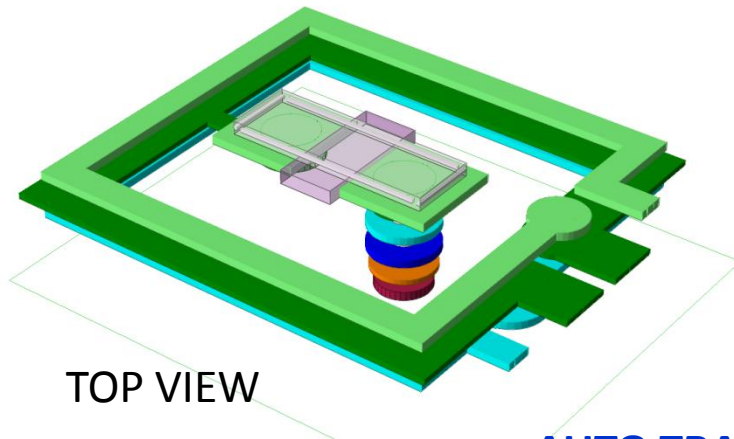**MODIFIED GUANELLA BALANCED  
TRANSFORMER (2.5:1)**



TOP VIEW




**AUTO TRANSFORMER (9:1)**

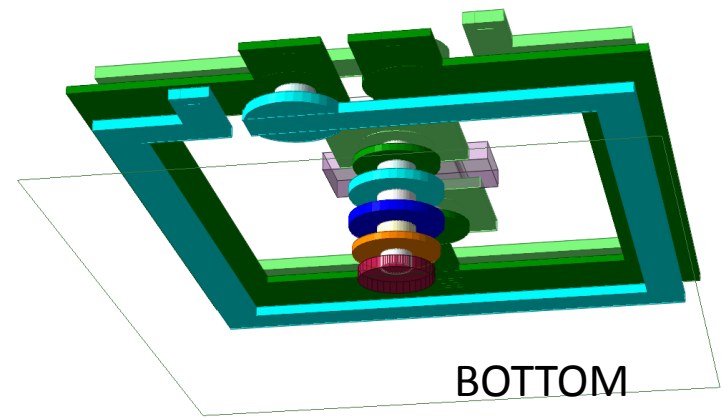

BOTTOM  
VIEW




# Wideband Flip Chip PA Module

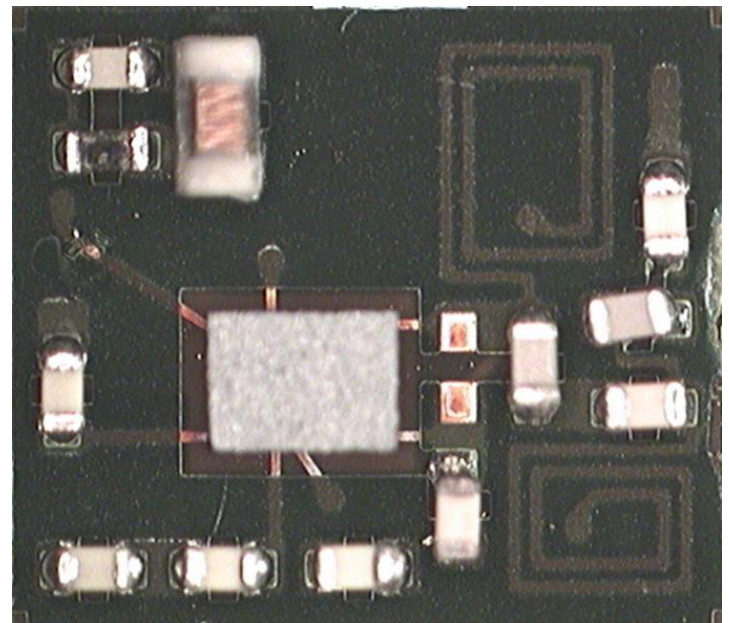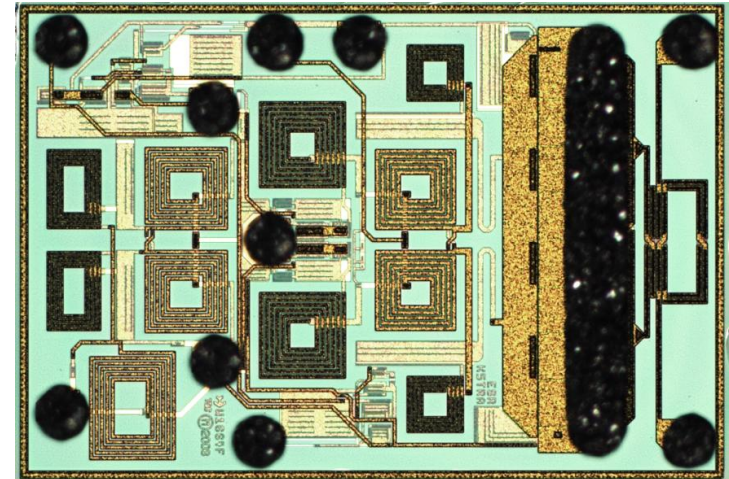
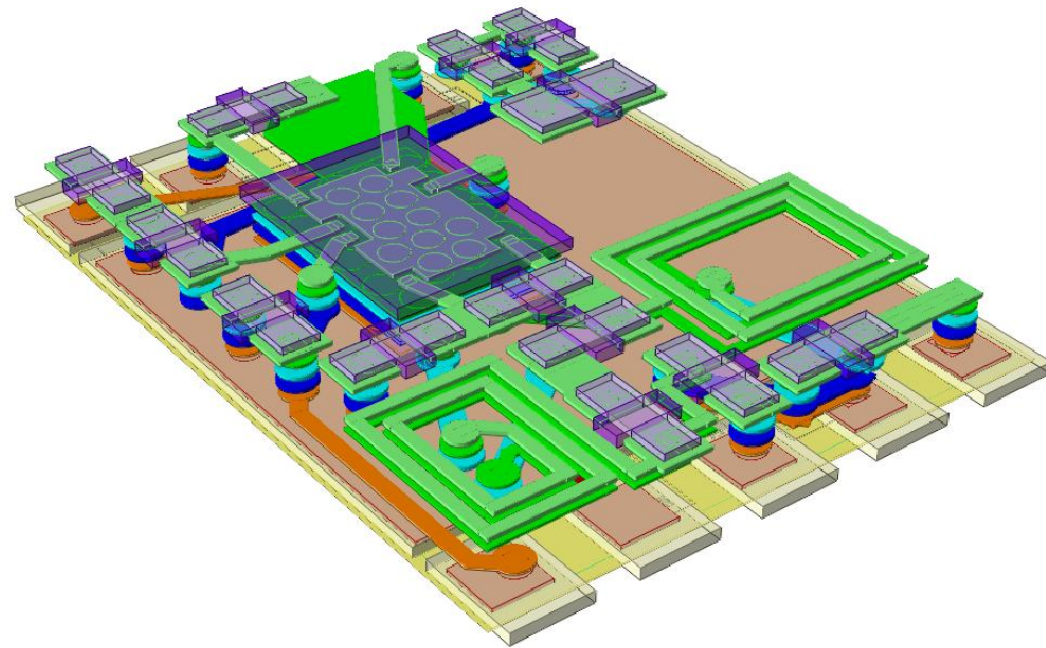


- 800 MHz – 2 GHz
- WCDMA operation

# Pushpull Multimode PA

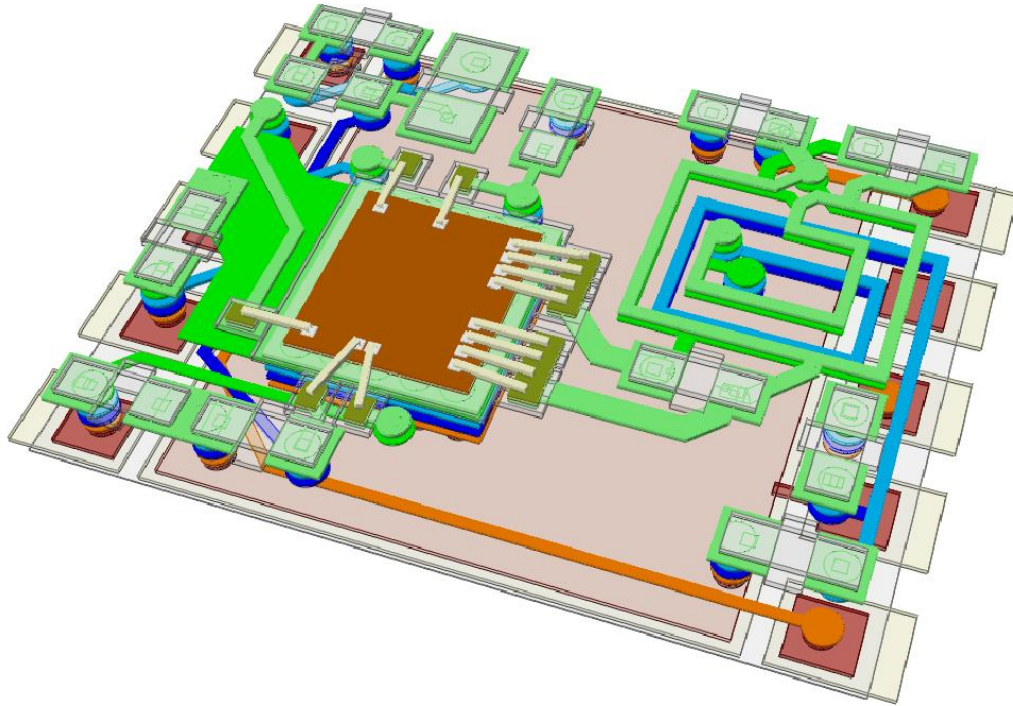


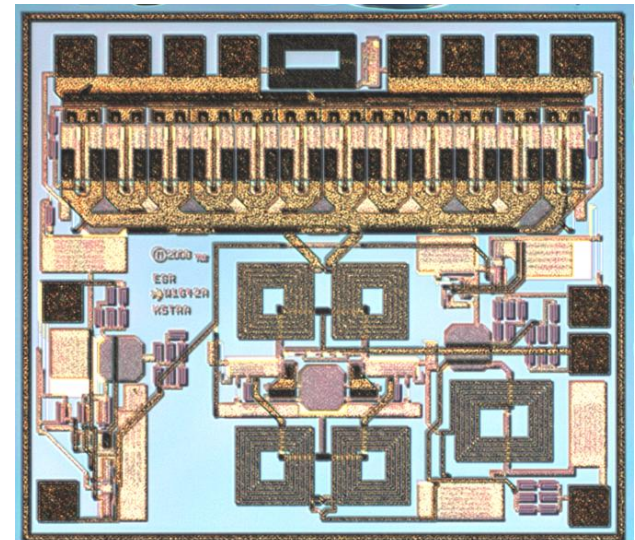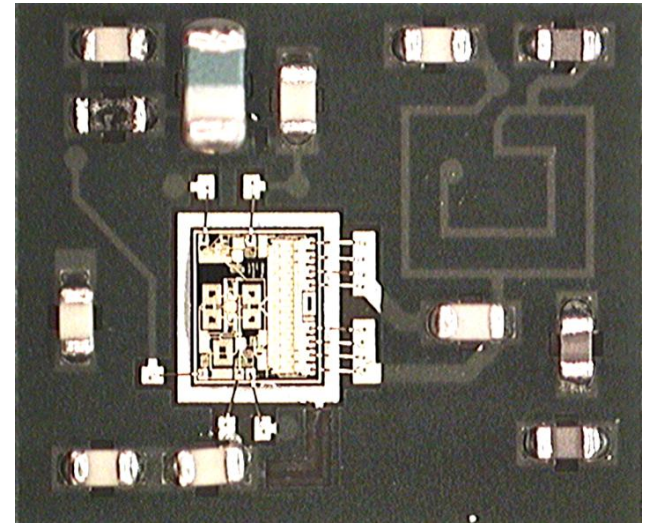- Laminate contains modified Guanella transformer stacked with choke balun
- Full 824 - 915 MHz operation
- WCDMA, EDGE, and GSM






# Low V Pushpull Multimode PA

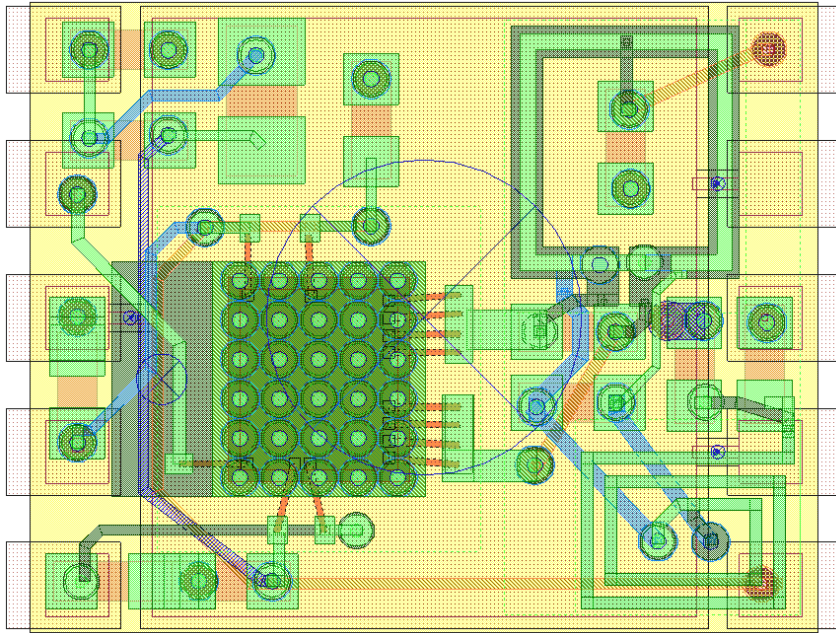


**5mm x 4mm PA MODULE**  
( .20" x .16" )

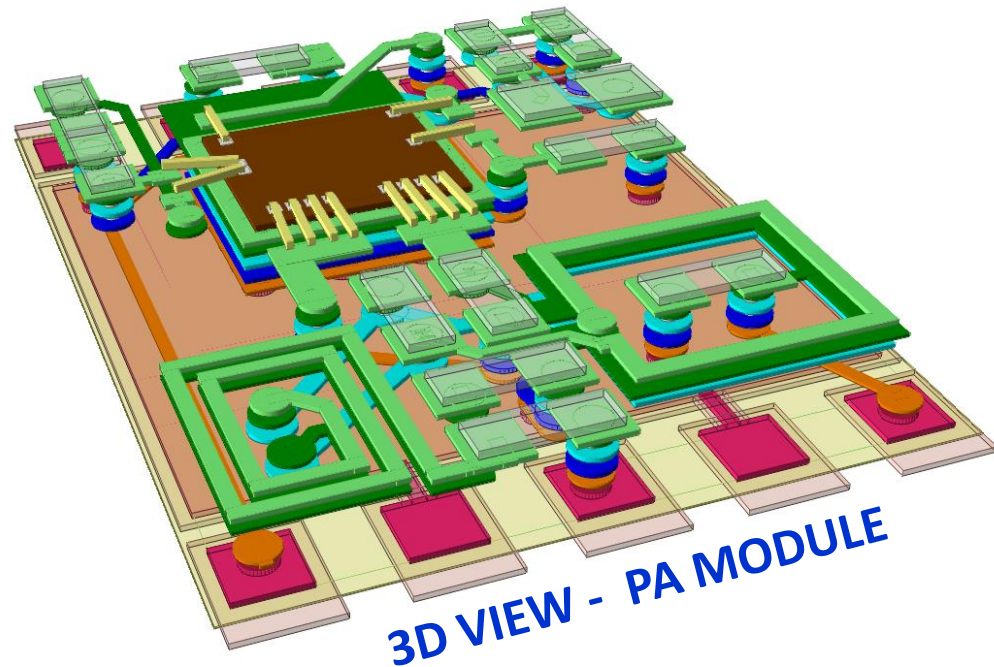
- Low Vcc operation provided by high ratio transformer
- Three metal layers are used in a 9:1 auto-transformer
- Choke balun




# GaAs Pushpull PA Circuit Blocks

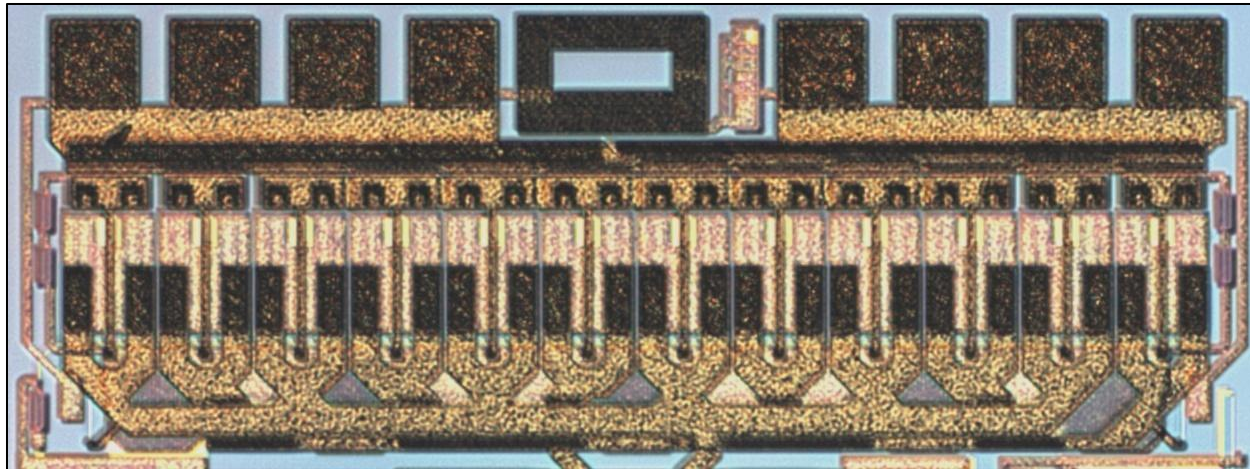

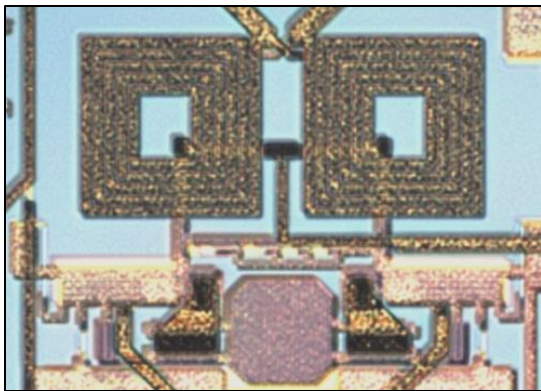ARRAY OF OUTPUT CELLS WITH INTERLEAVED  
MANIFOLD AND 3<sup>RD</sup> HARMONIC TUNING



INTERSTAGE GUANELLA  
TRANSFORMER

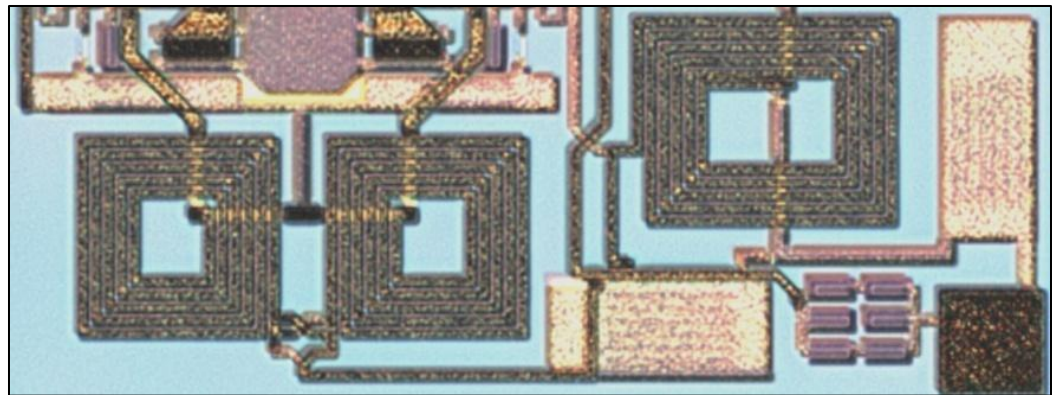

INPUT CHOKE BALUN and GUANELLA  
TRANSFORMER



# Summary

- Transmission-line transformers
  - 3 categories
- Coupled lines
  - Coupling coefficient
  - Capacitive compensation
- Unbalanced or balanced forms
  - Ruthroff : unbalanced
  - Guanella: balanced
- Autotransformers
- Some examples

