

# Remote PA & LNA

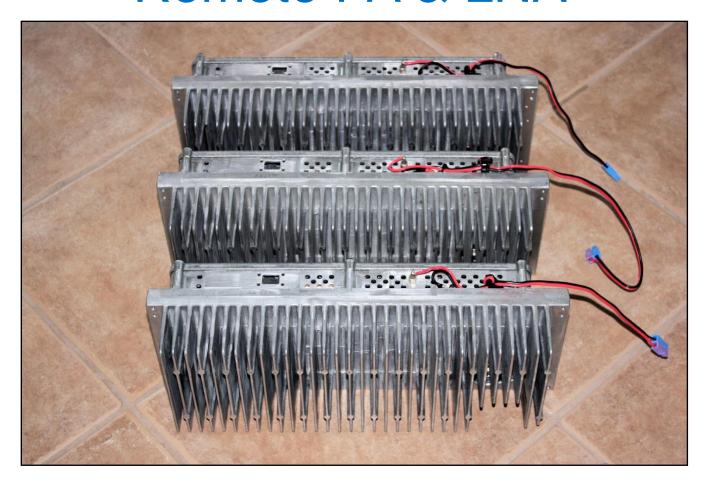

For 144, 222, and 432 MHz

# VHF-UHF Remote PA & LNAs

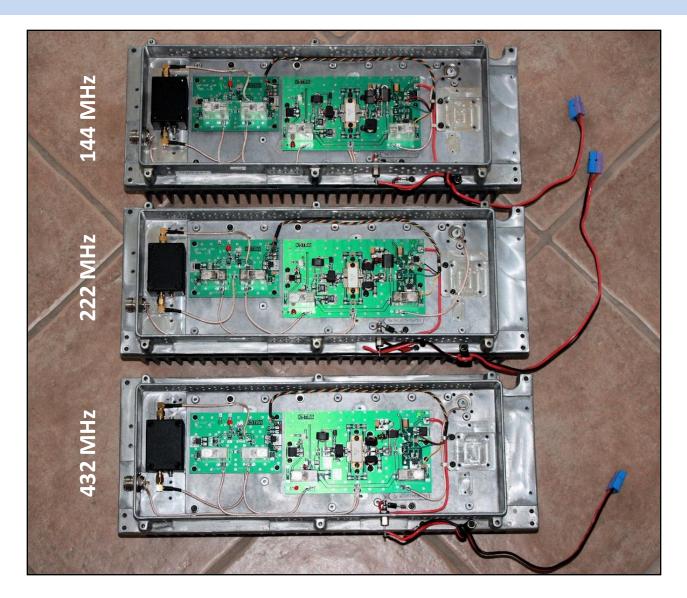

# 222 MHz Remote PA & LNA



### Overview

- Remote PAs and LNAs for operation at the antenna
- T/R switching is drive sensed
- Schottky detector circuit is tweaked for sensitivity
  - As low as +18 dBm will key the control circuit
- TX key hold time constant is 1.2 seconds
- Housing-heatsink from GE MASTR-III 120W PA
- Motorola MRF-186 LDMOS final provides:
  - 125 W output on each band: 144, 222, and 432 MHz
  - Gain (approx. +19 dB) padded at input for available drive
- Triquint TQP3M9008 LNA provides:
  - 0.8 dB NF on each band: 144, 222, and 432 MHz
  - Gain (approx.+22 dB) padded at output to + 12 dB

# **Important Details**

### LNA preselector filter is required

- FM and TV broadcast signals will overwhelm the LNA without filtering
- Two helical resonator BPF used

### LNA protection diodes required

- Leading edge protection while relay control activates
- Leakage capacitance in relay can allow excessive RF into LNA when transmitting

### PA input pad prevents overdrive

- MRF186 easily provides +19 dB of gain
- Two resistor, compact L-pad topology
- For added ruggedness to overdrive and mismatch, the final can be changed to MRF151G for VHF or MRF372 for UHF



### Control

#### • Off mode:

RF pass through


#### RX mode:

- LNA is powered ON
- PA BIAS is removed
- Relays select LNA signal path

#### • TX mode:

- LNA is powered OFF
- LNA PIN protect is turned ON
- PA BIAS turned ON
- Relays select PA signal path


# **PA Board Layout**

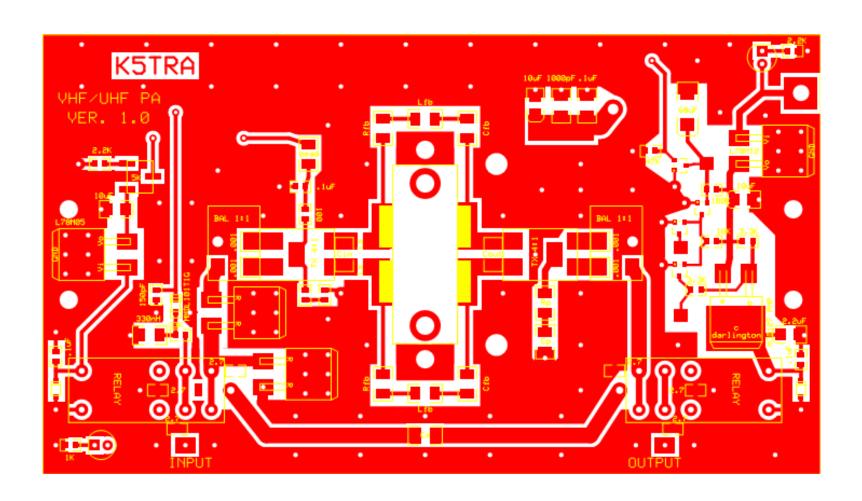

# Remote PA



### **PA Schematic**

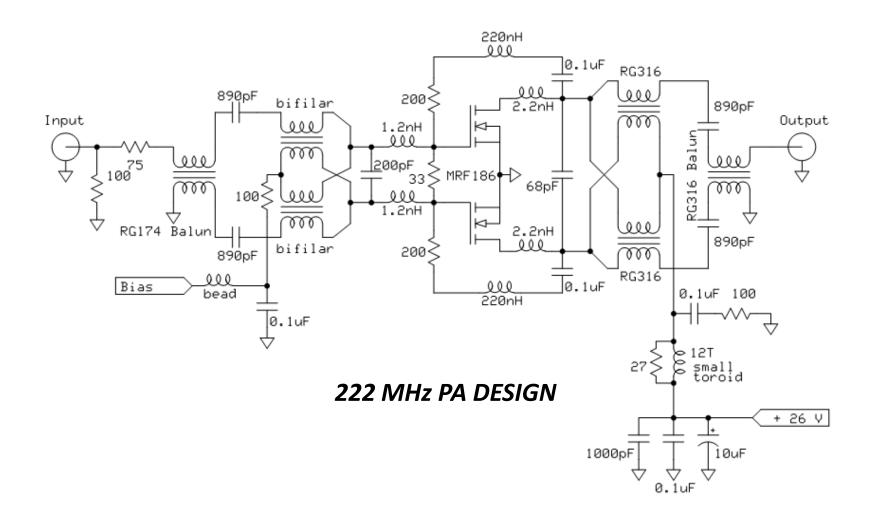

# PA Input L-Pad Design


#### S21 (dB)

	Rp = 10	Rp = 20	Rp = 25	Rp = 30	Rp = 50	Rp = 75	Rp = 100	Rp = 150
Rs= 0	-10.88	-7.04	-6.02	-5.26	-3.52	-2.50	-1.94	-1.34
Rs= 10	-12.26	-8.30	-7.23	-6.44	-4.61	-3.52	-2.92	-2.28
Rs= 20	-13.44	-9.40	-8.30	-7.48	-5.58	-4.44	-3.81	-3.13
Rs= 25	-13.98	-9.90	-8.79	-7.96	-6.02	-4.86	-4.22	-3.52
Rs= 30	-14.49	-10.37	-9.25	-8.41	-6.44	-5.26	-4.61	-3.90
Rs= 50	-16.26	-12.04	-10.88	-10.01	-7.96	-6.72	-6.02	-5.26
Rs= 75	-18.06	-13.76	-12.57	-11.67	-9.54	-8.24	-7.51	-6.72
Rs= 100	-19.55	-15.19	-13.98	-13.06	-10.88	-9.54	-8.79	-7.96
Rs= 150	-21.94	-17.50	-16.26	-15.32	-13.06	-11.67	-10.88	-10.01


#### S11 (dB)

		Rp = 10	Rp = 20	Rp = 25	Rp = 30	Rp = 50	Rp = 75	Rp = 100	Rp = 150
Rs=	0	-2.92	-5.11	-6.02	-6.85	-9.54	-12.04	-13.98	-16.90
Rs=	10	-3.01	-5.38	-6.41	-736	-10.63	-13.98	-16.90	-22.28
Rs=	20	-3.07	-5.59	-6.702	-7.78	-11.60	-15.92	-20.29	-32.67
Rs=	25	-3.10	-5.68	-6:85	-7.96	-12.04	-16.90	-22.28	-323.53
Rs=	30	-3.12	-5.76	-6.97	-8.13	-12.47	-17.91	-24.61	-33.44
Rs=	50	-3.19	-6.02	-7,36	-8.67	-13.98	-22.28	-800.00	-20.83
Rs=	75	-3.25	-6.25	-7.71	-9.17	-15.56	-29.83	-25.58	-16.26
Rs=	100	-3.30	-6.41	7.96	-9/54	-16.90	-328.31	-20.83	-13.98
Rs=	150	-3/3/5	-6-62	-8.30	-10.05	-19.09	-27.24	-16.90	-11.60

# **PA Control Schematic**

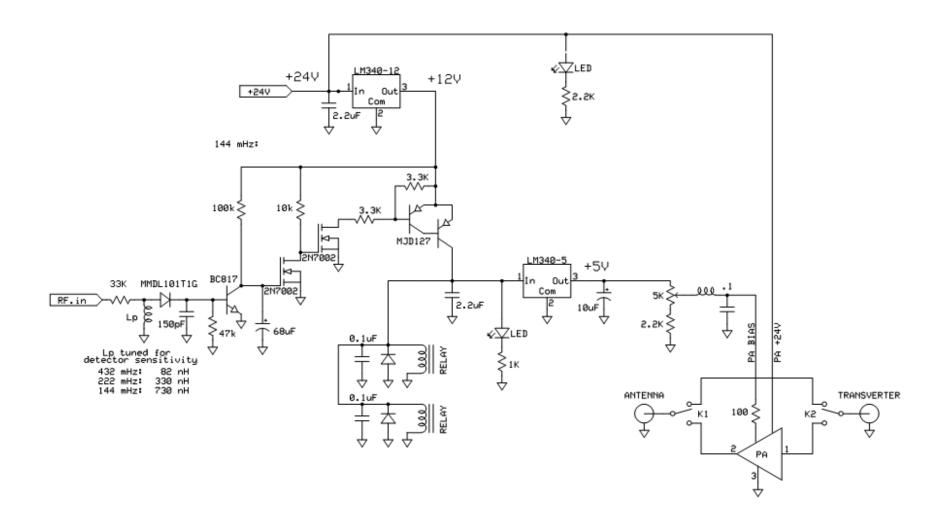

# **LNA Board Layout**

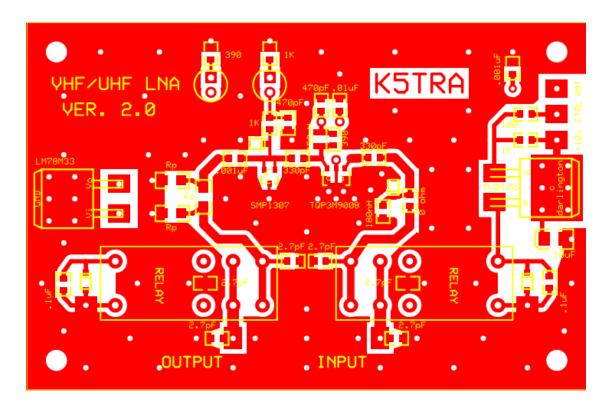


LNA BOARD IS OPTIONAL


# Remote LNA





### **LNA Control Schematic**

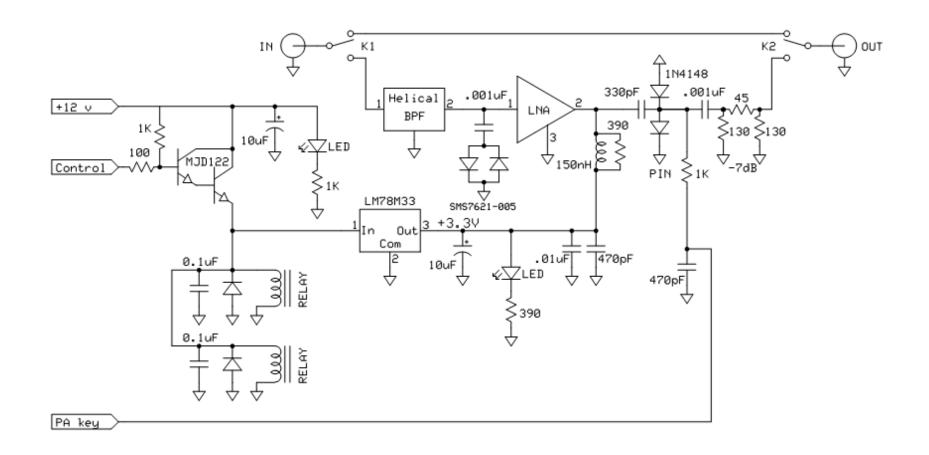


# Preselector Design

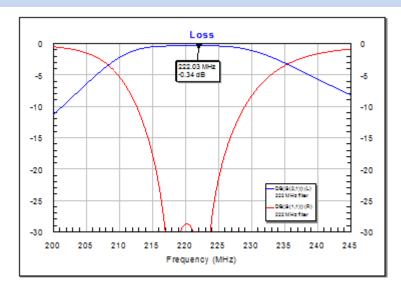

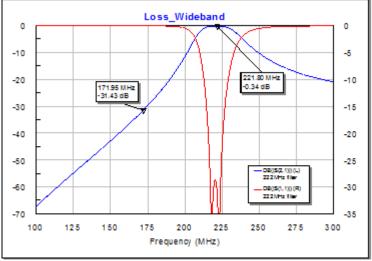

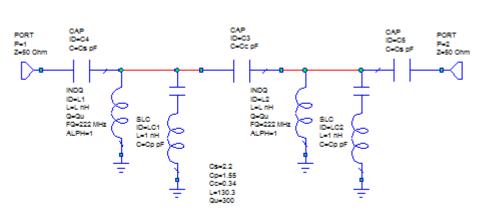

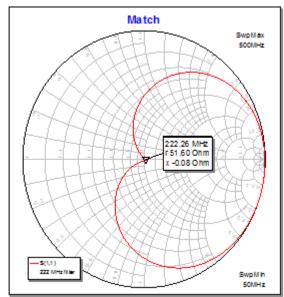


222 MHz BPF

# Helical BPF



# LNA Preselector Response

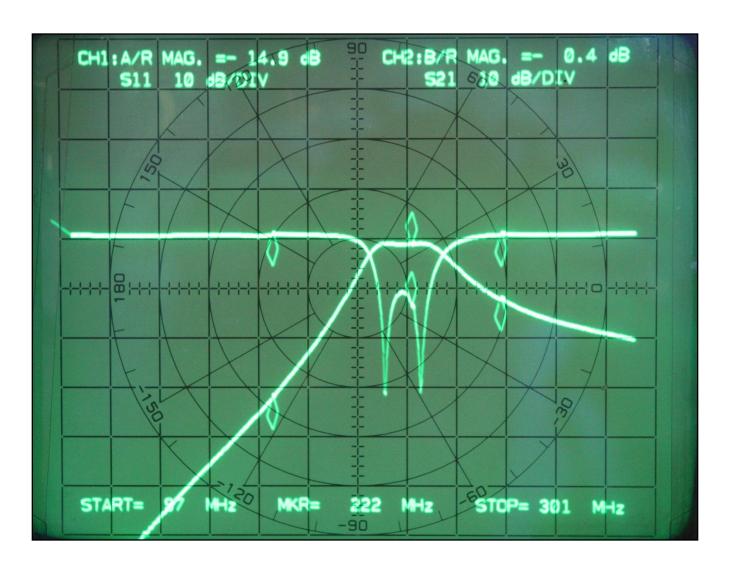


# More Helical BPFs






# 222 MHz Remote Amplifier in Attic

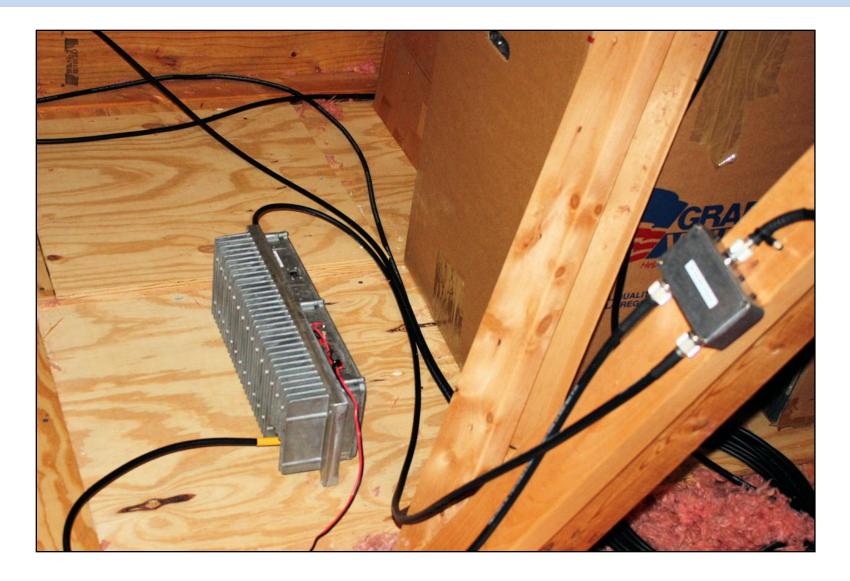
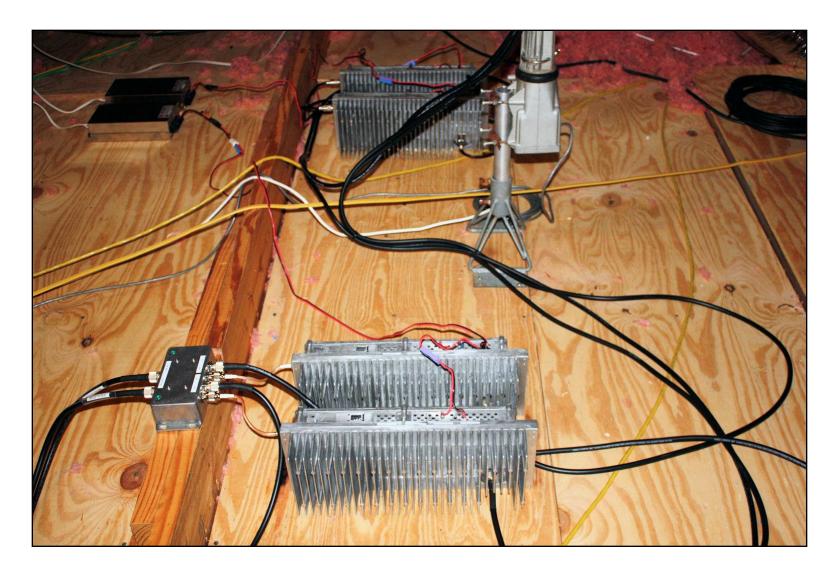
# 902, 1296, 144, & 432 Remote Amplifiers



# WEB-IP Power Strip



# 144 MHz Remote PA & LNA

