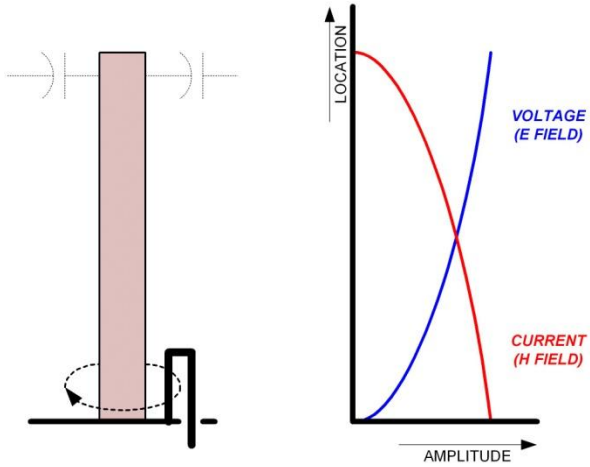


## CAVITY and COMBLINE FILTERS, COMBINERS and DUPLEXERS




**K5TRA**


# COUPLED QUARTER WAVE RESONATORS




$\lambda/4$  RESONATOR

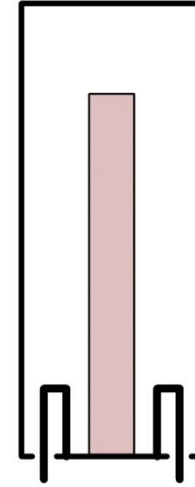

LOOP COUPLED  $\lambda/4$  CAVITY


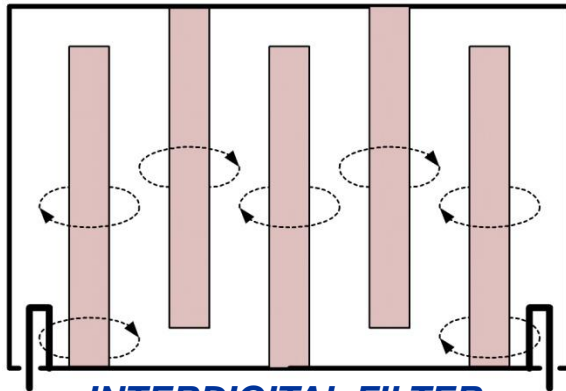


INTERDIGITAL FILTER

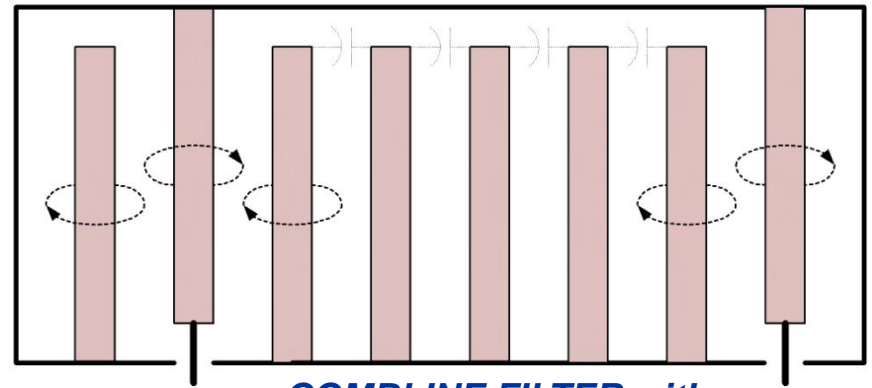

COMBLINE FILTER with  
INTERDIGITAL PORT COUPLING

# PARALLEL RESONATORS

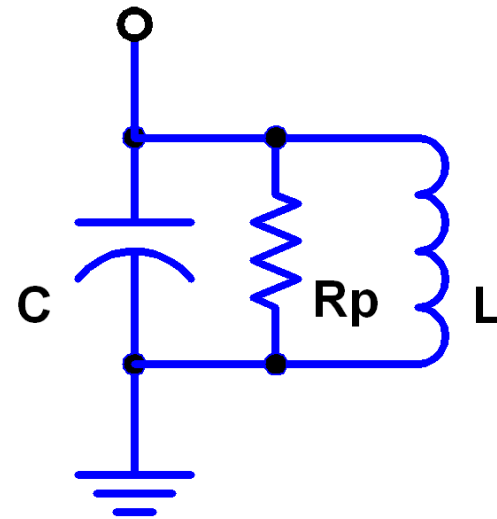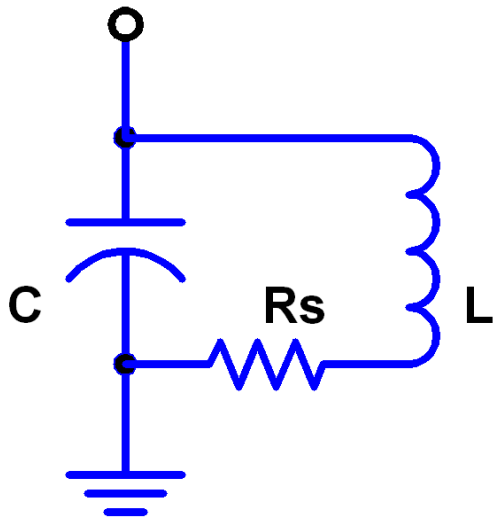


$$R_p = (Q_u^2 + 1) R_s$$



$$Q_u = 5000 \text{ (typical)}$$

*THIS IS A GOOD LUMPED REPRESENTATION OF A  $\lambda/4$  RESONATOR*


# CAVITY RESONATOR with LOOP COUPLING

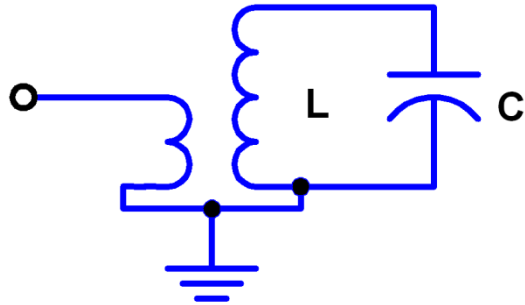

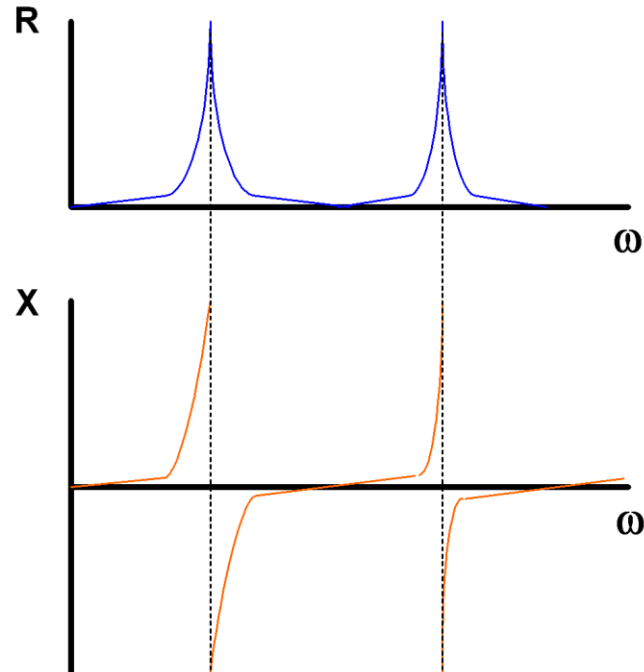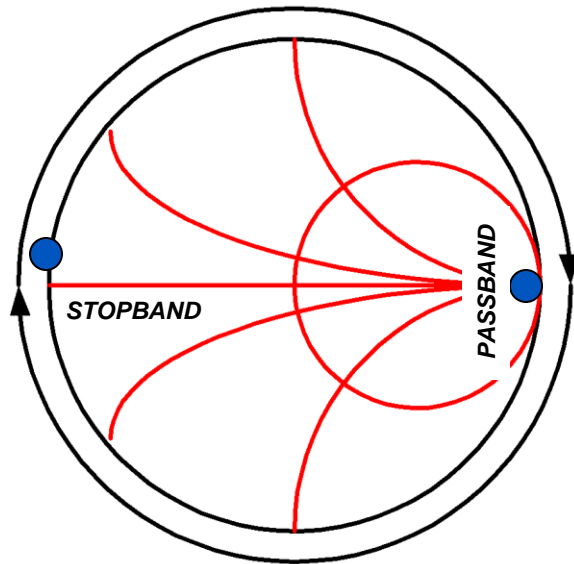- Parallel LC model
- High Z at resonance
- Low Z (slightly inductive) in stopband
- Resonance at  $\lambda/4$  and  $3\lambda/4$
- 70% more Qu typical at  $3\lambda/4$





# LADDER FILTER BASIC BUILDING BLOCK

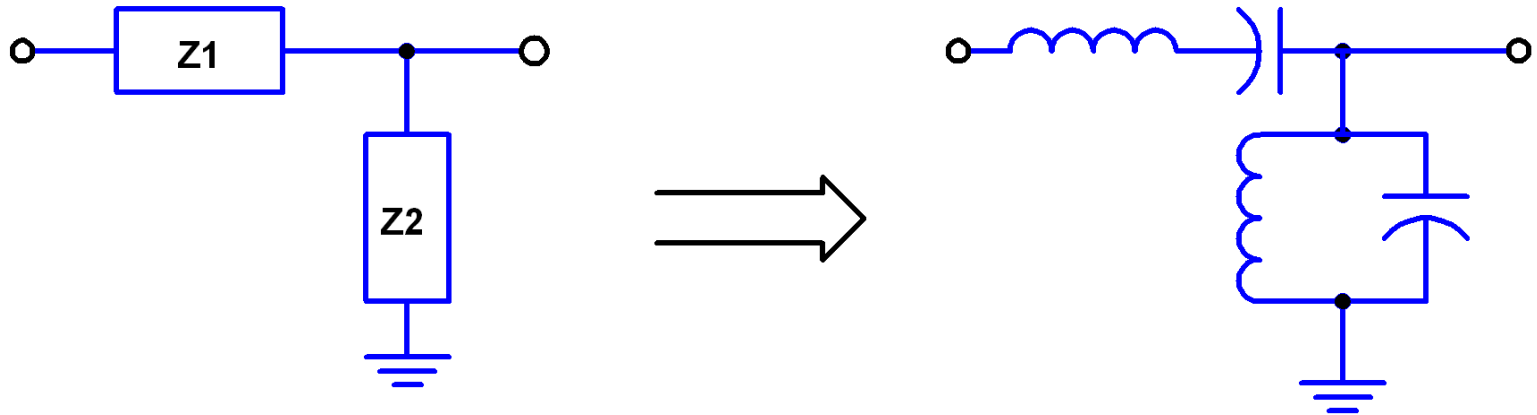

- Passband:  $Z_1 \Rightarrow \textit{short}$  and  $Z_2 \Rightarrow \textit{open}$
- Stopband:  $Z_1 \Rightarrow \textit{open}$  and  $Z_2 \Rightarrow \textit{short}$

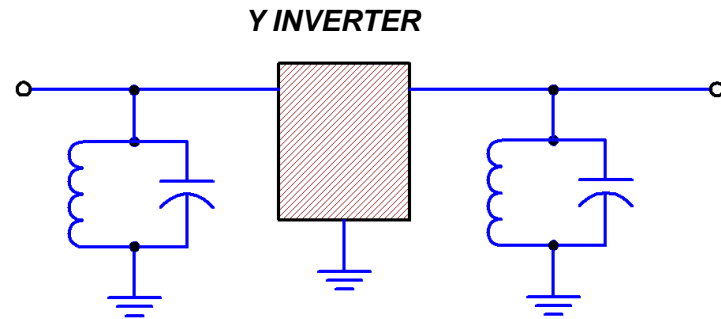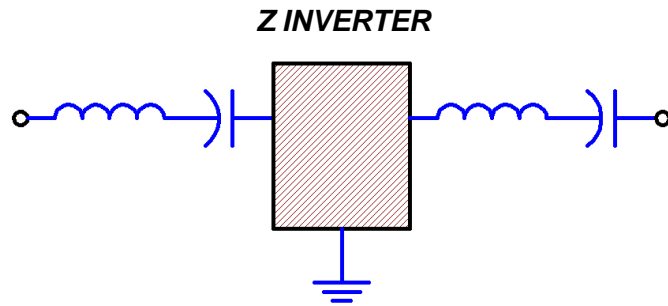
# IMPEDANCE INVERTERS PROVIDE REUSE OF RESONATOR TYPE



- Impedance inverter interface between similar resonators provides maximum stopband attenuation
- Most common impedance inverter is transmission line that is an odd multiples of  $\lambda/4$

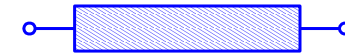
# IMPEDANCE INVERTERS

- Impedance (or admittance) inverters can be used to convert parallel resonance to a series resonance characteristic.
- The canonic impedance inverter is the  $\lambda/4$  line.
- LC forms provide moderate bandwidth Z inversion.
- Capacitive T and  $\pi$  sections are for narrow band applications. Negative C is absorbed into resonator (cancels some positive C).




Transmission Line  
J (or K) Inverter

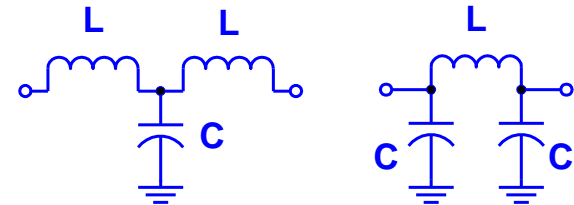
$$Z_0, \quad \theta = \frac{\lambda}{4}$$


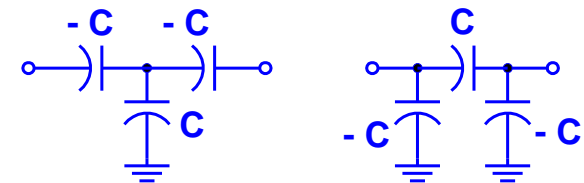
$$Z_0 = \sqrt{\frac{L}{C}}, \quad \omega_0 = \frac{1}{\sqrt{LC}}$$




$$Z_0 = \frac{1}{\omega_0 C}$$

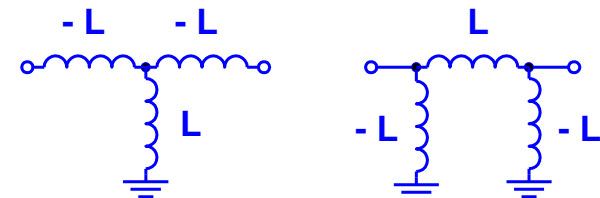



$$Z_0 = \omega_0 L$$
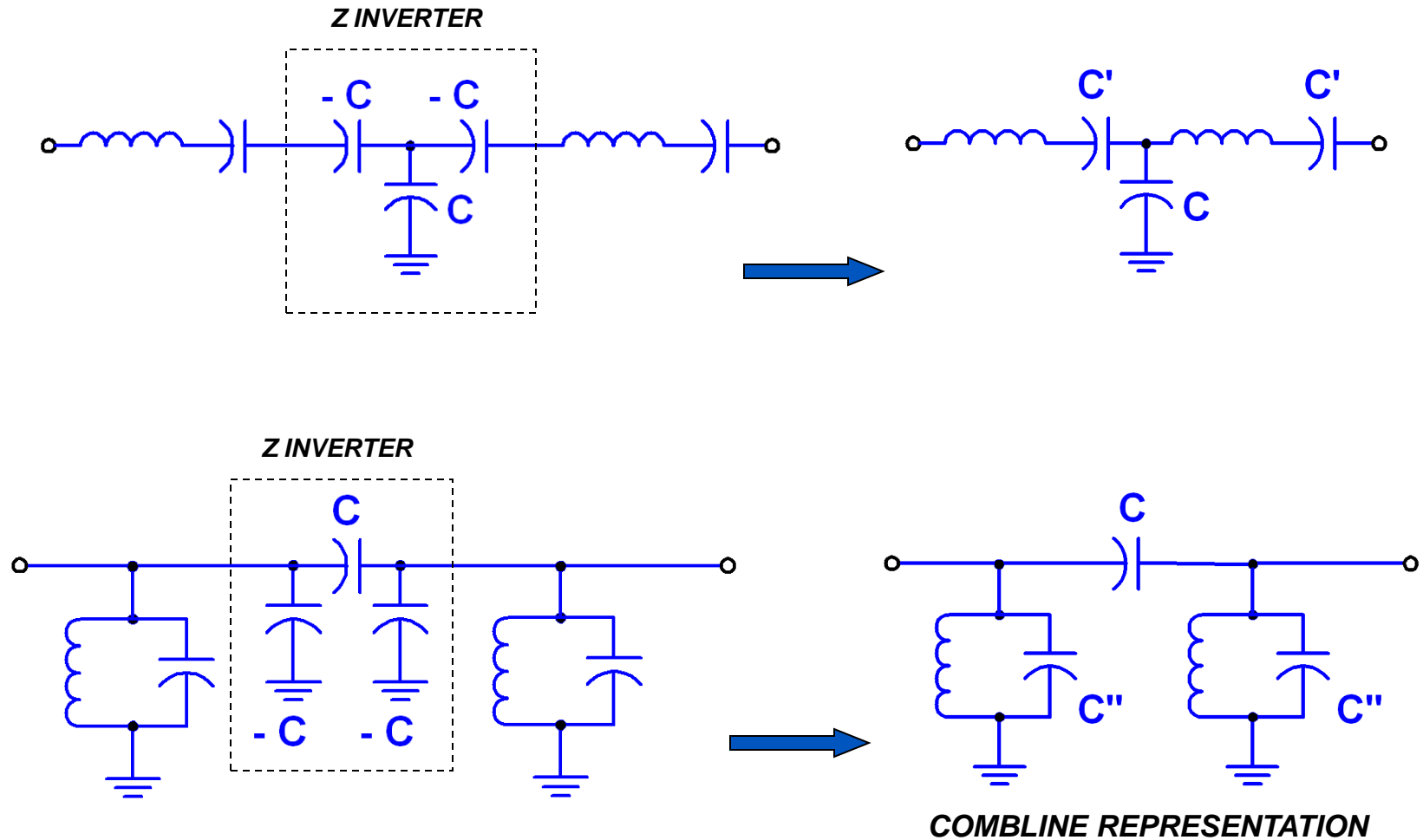
# NARROW FILTERS WITH CAPACITIVE Z INVERTER






# COMBLINE FILTERS in UHF DUPLEXER

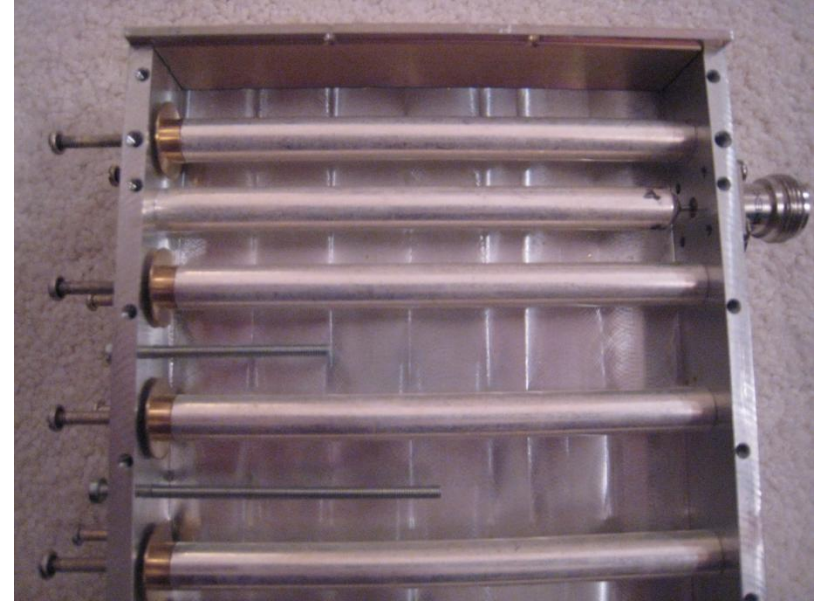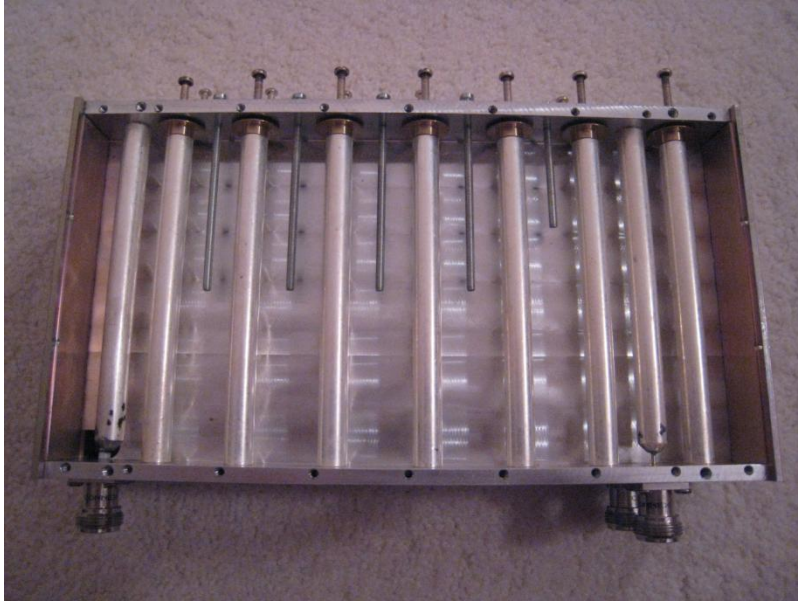


- Comblines filter formed by capacitive coupled (E field)  $\lambda/4$  resonators.
- Resonator tuning with capacitive probe into open end.
- Inverter coupling capacitance tuned with grounded screw between resonators.
- Port coupling resonators are interdigital inductive coupled (H field).
- Outer port reflective resonator sets near stopband rejection.


# 900 MHz COMBLINE DUPLEXER

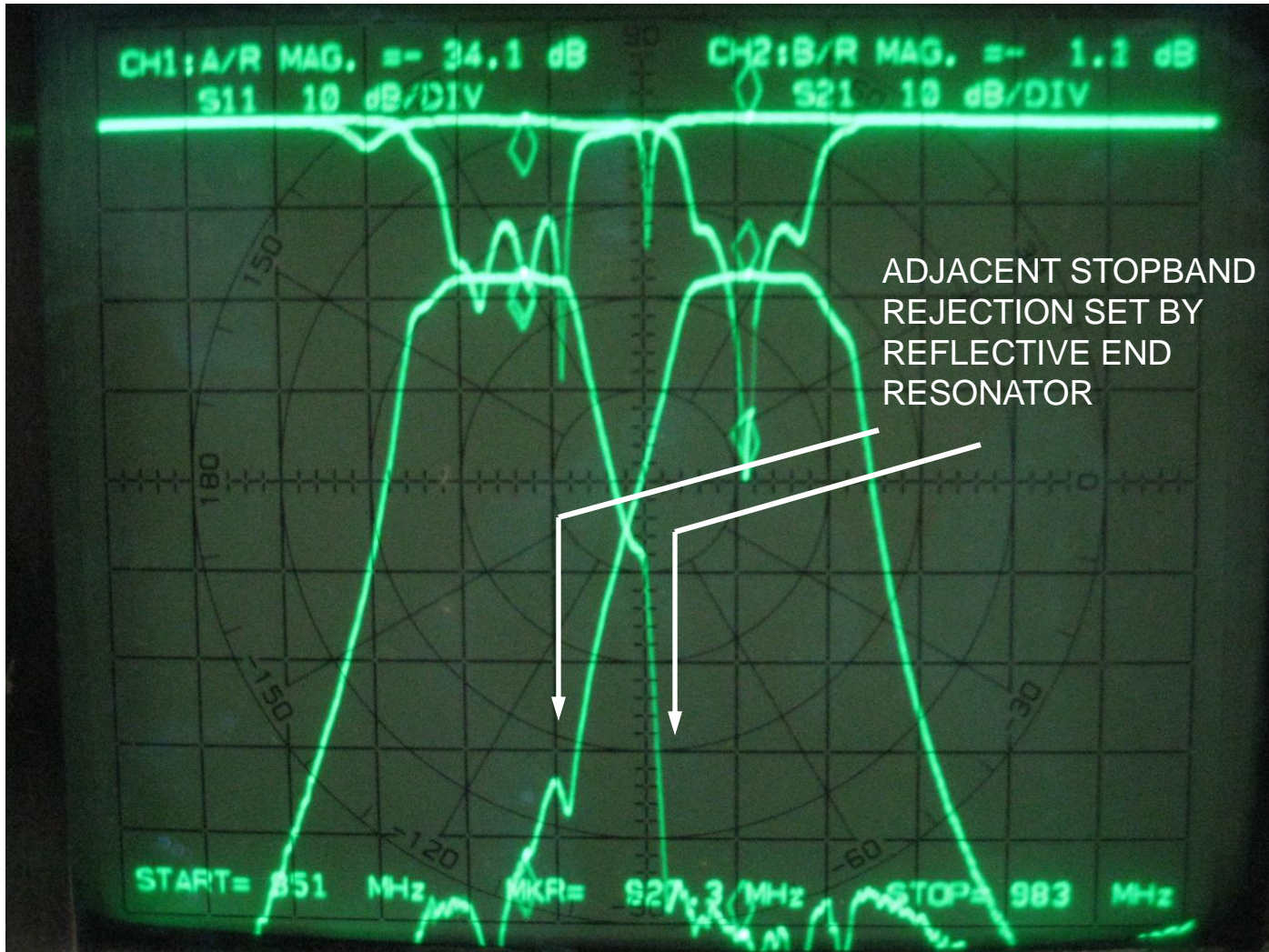

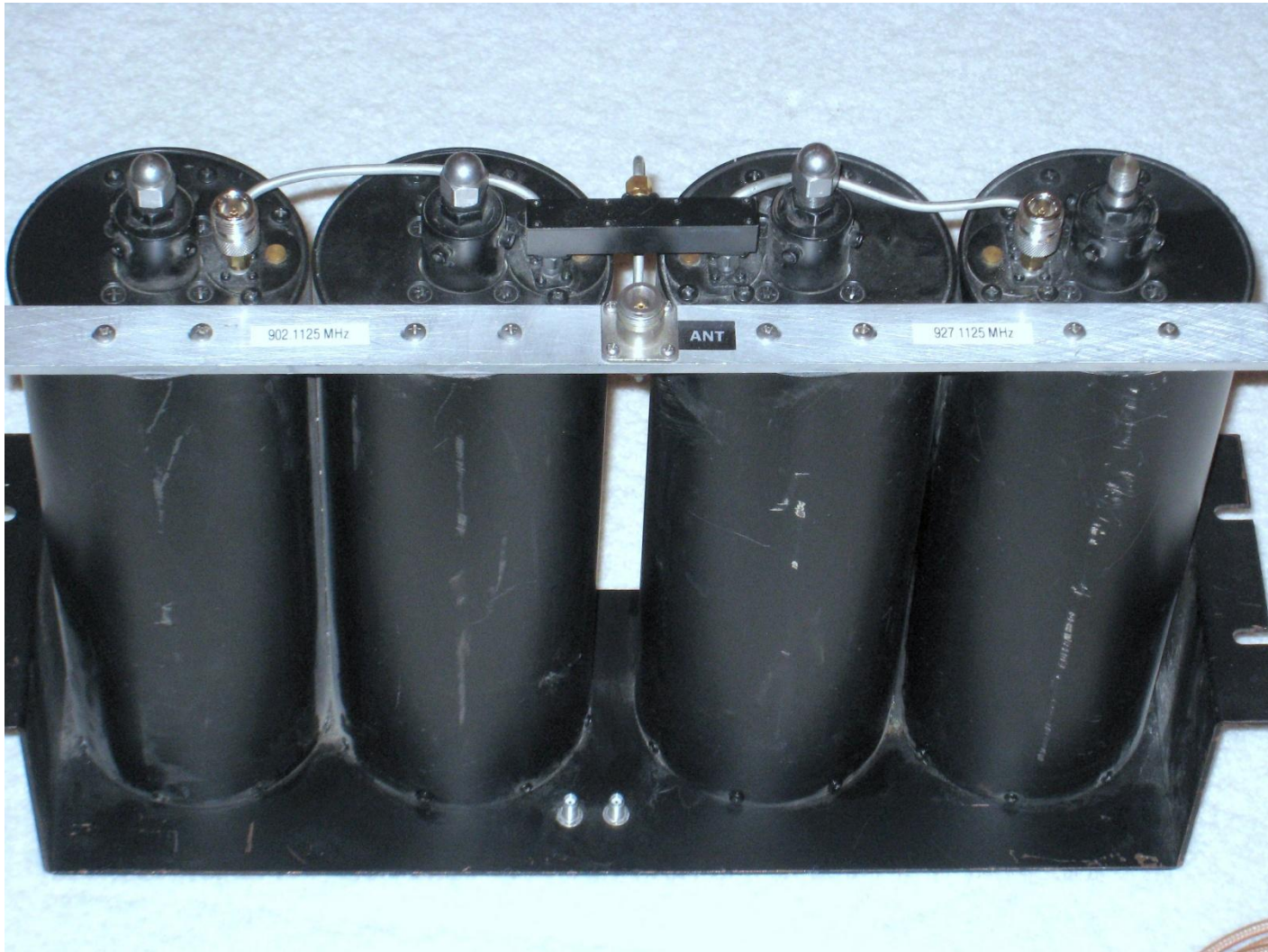
# 900 MHz DUPLEXER with $3\lambda/4$ CAVITIES



# SIX $\lambda/4$ CAVITY FILTER


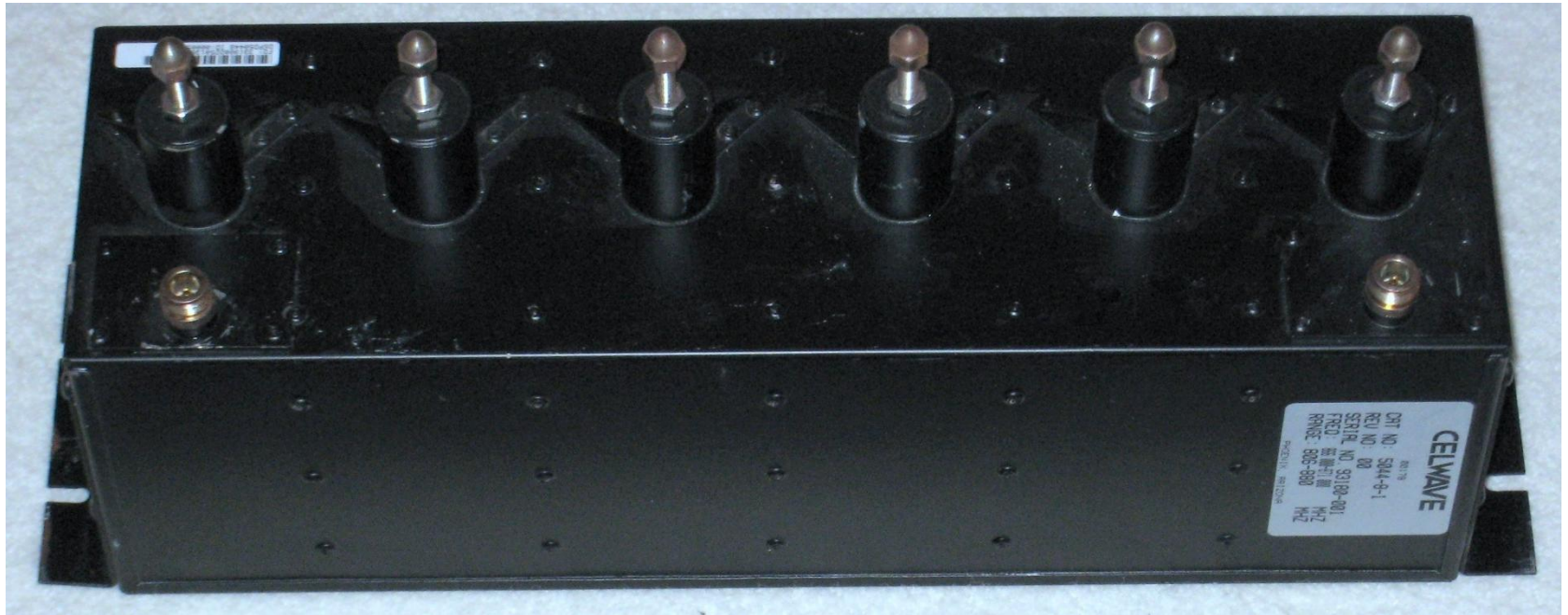


# $\lambda/4$ CAVITIES

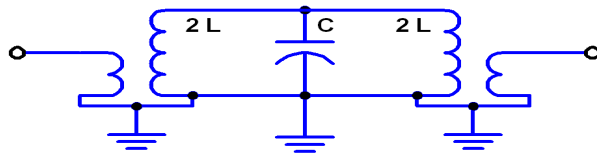


LOOP COUPLED PASS CAVITY

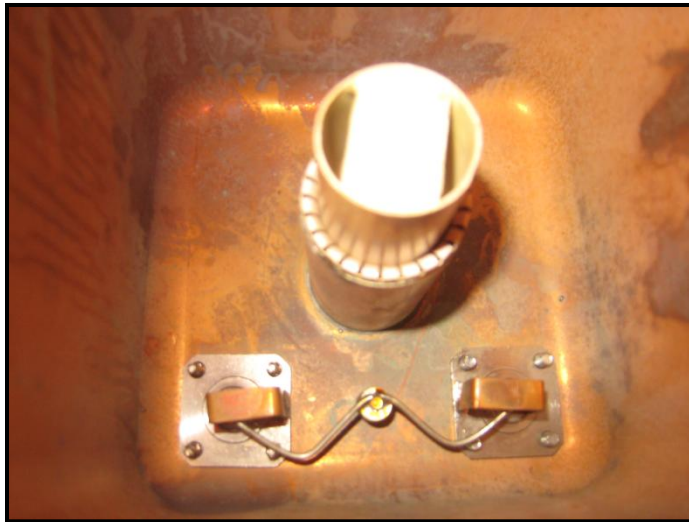
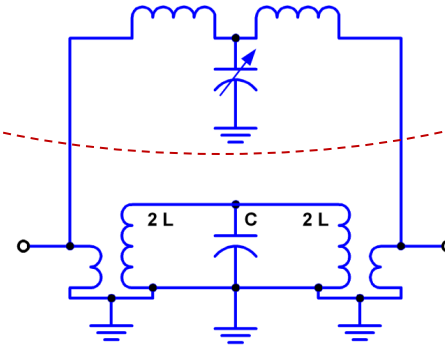
*with added*  
**REJECTION ENHANCEMENT NOTCH**






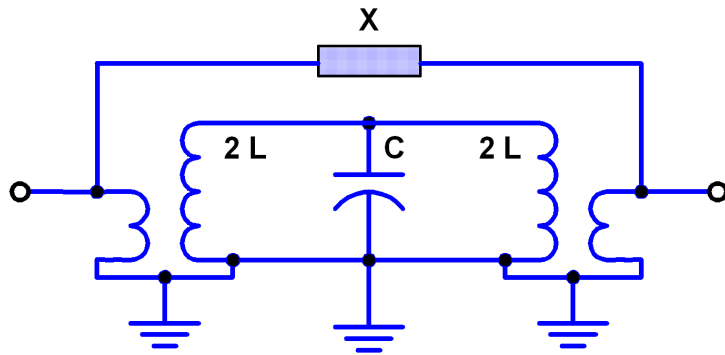
# REJECTION ENHANCEMENT ADDED TO PASS CAVITY



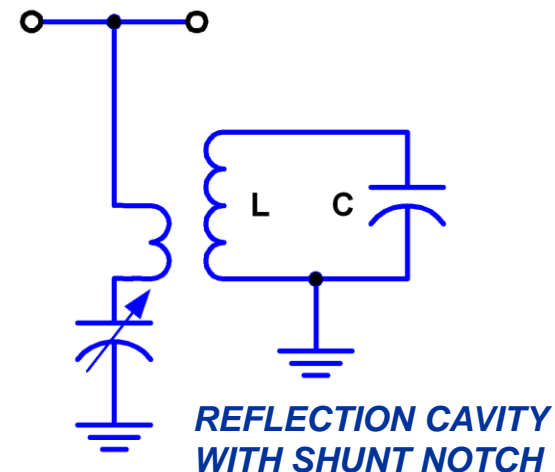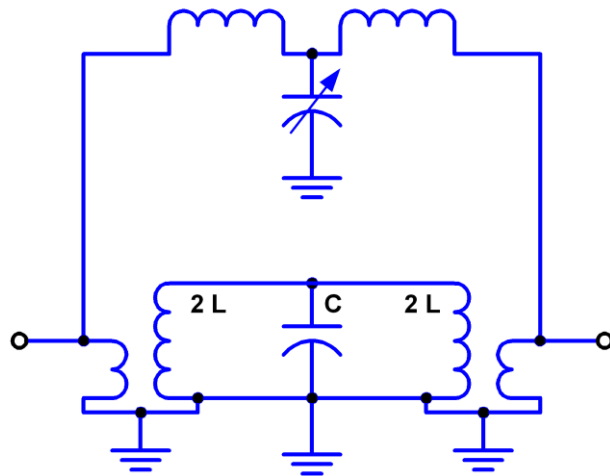
- $X$  can be an inductor for a notch above the pass frequency
- $X$  can be a capacitor for a notch below the pass frequency
- $X$  can be an LC network to provide adjustable rejection above or below the pass frequency


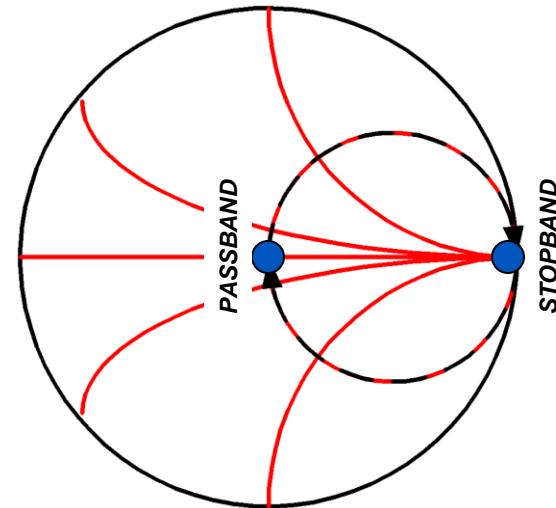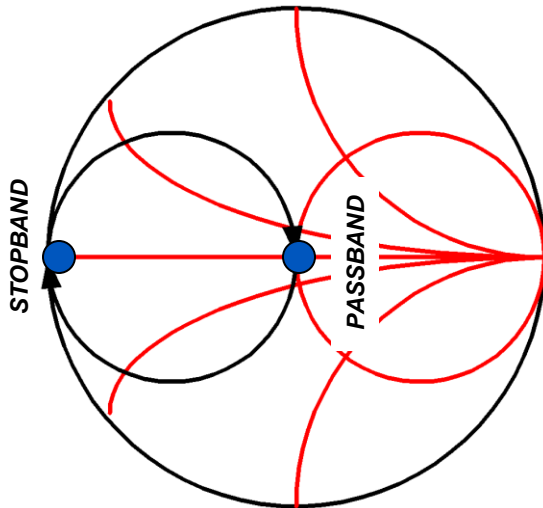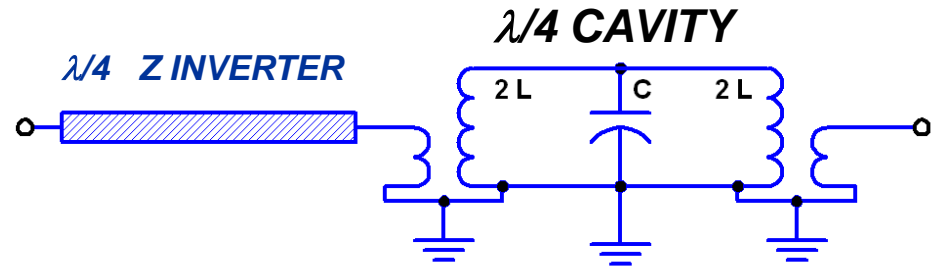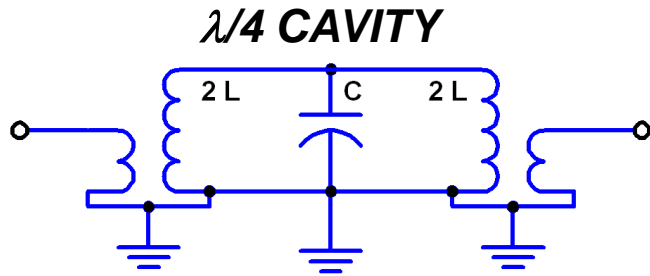
# Z INVERTER 'FLIPS' TERMINAL CHARACTERISTIC



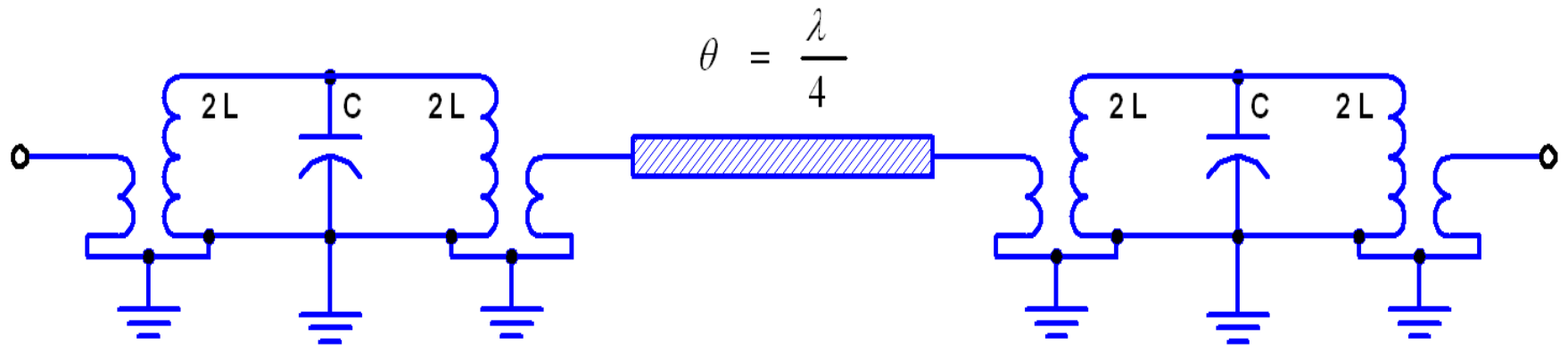
# TWO CAVITY CASCADE FILTER with $\lambda/4$ Z-INVERTER






# CAVITY TRANSMITTER COMBINER

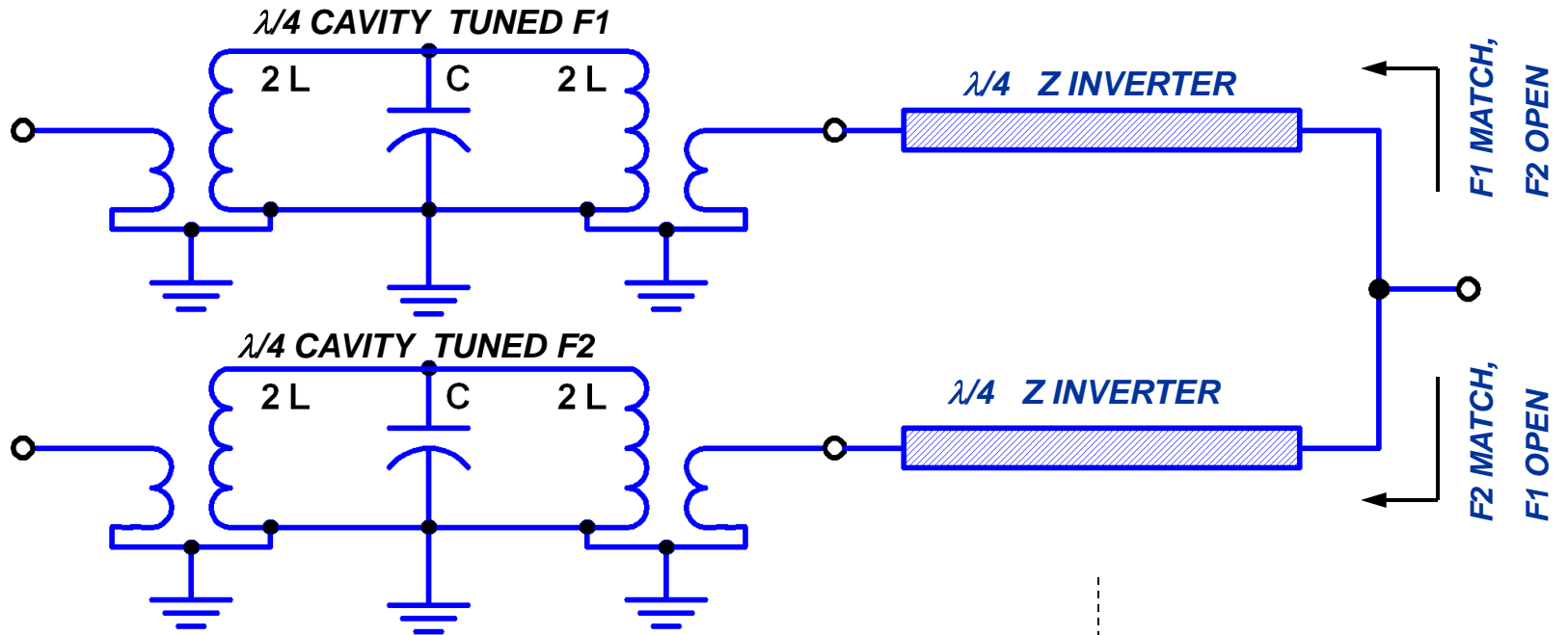


CAN BE EXTENDED TO MORE PORTS AS A 'STAR' COMBINER

# FOUR CAVITY DUPLEXER

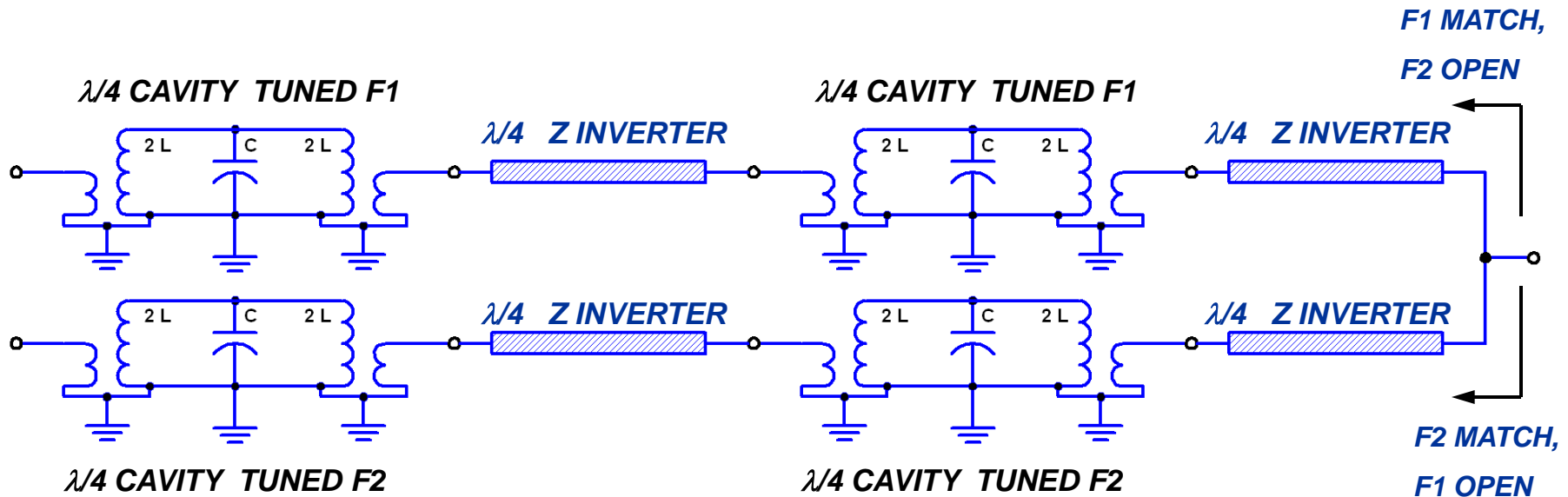

- Duplexer operation is the same as with cavity transmitter combiner
- Duplexer performance requires better rejection of other cavity channel frequency. (Isolation of transmitter from receiver in repeater)
- Additional rejection of alternate channel can be added to cavity response.

# DUPLEX NARROW AND WIDE BAND PORTS

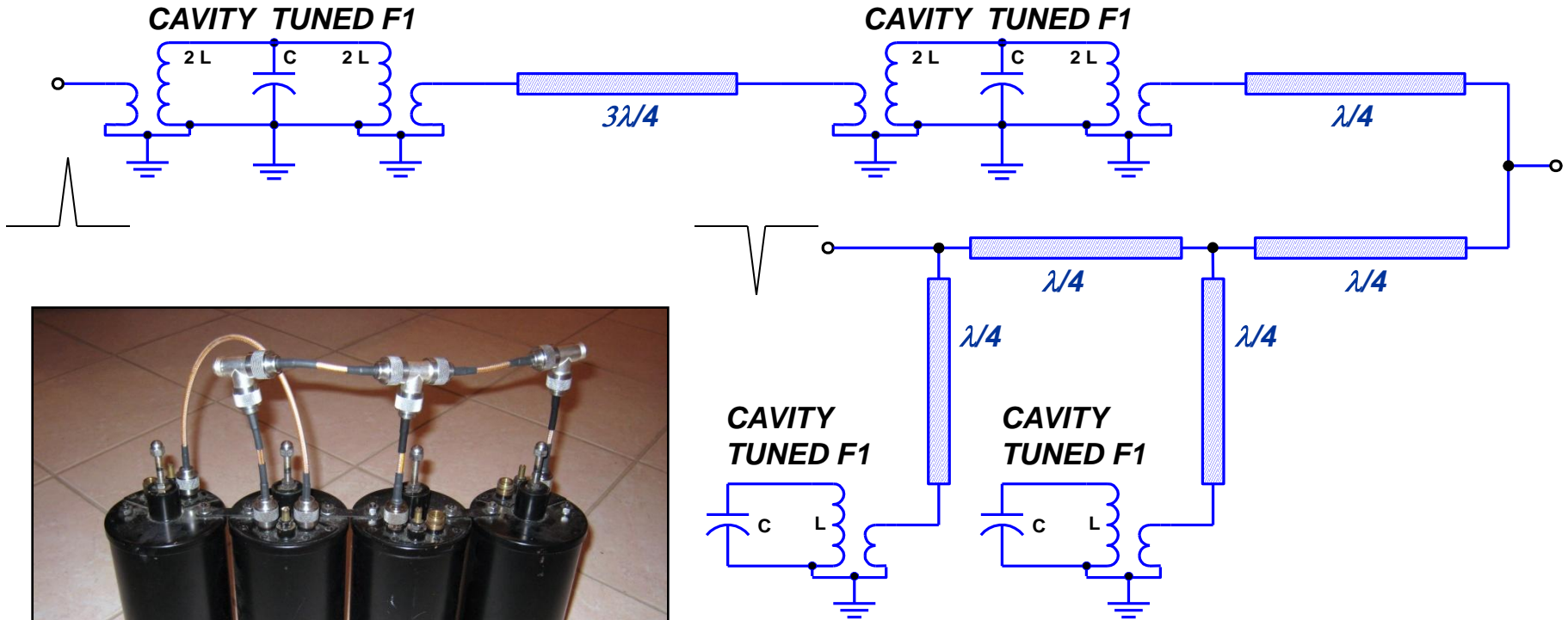

- Notch filter formed by BP cavities offset by  $\lambda/4$
- Narrow and wide band duplexer formed by combined pass and notch filters