
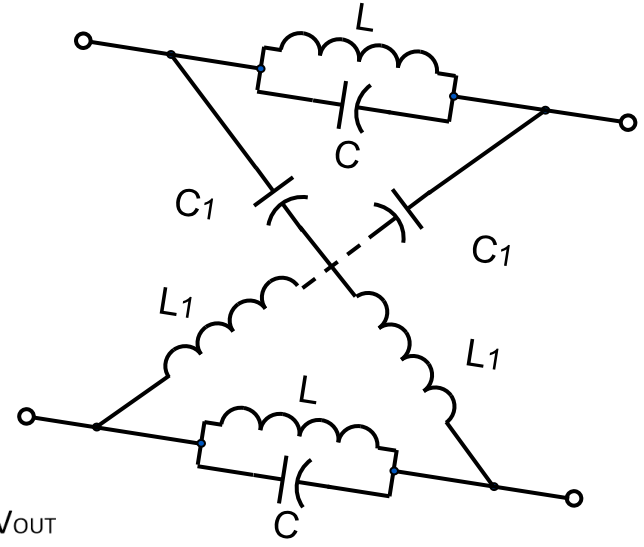
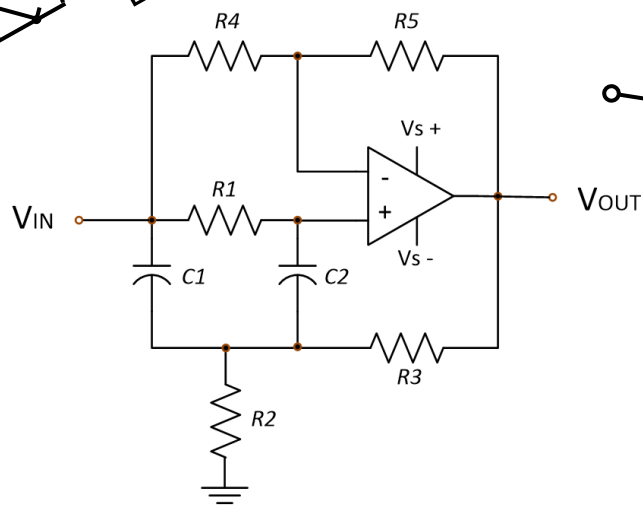


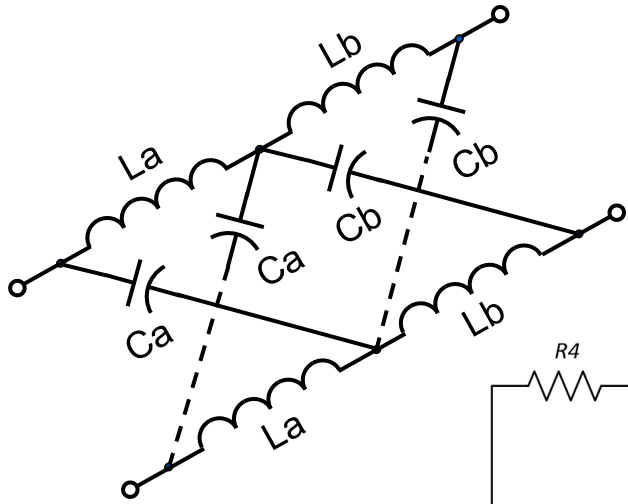Filters for SSB Direct Conversion Transceivers




K5TRA


OVERVIEW

- SSB (Image Reject) direct conversion – phasing method
- Allpass approach to constant phase difference
 - Active Filters
 - Biquad cascades
- Low sensitivity approaches
- Audio phase difference networks
- Audio band limiting LPF (or BPF) low sensitivity filters

TX / RX SSB DIRECT CONVERSION

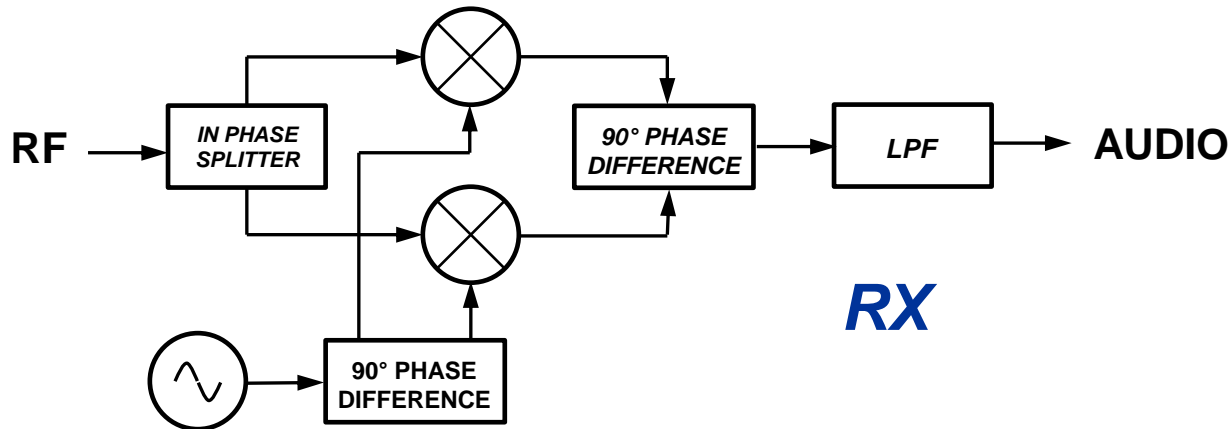


RX

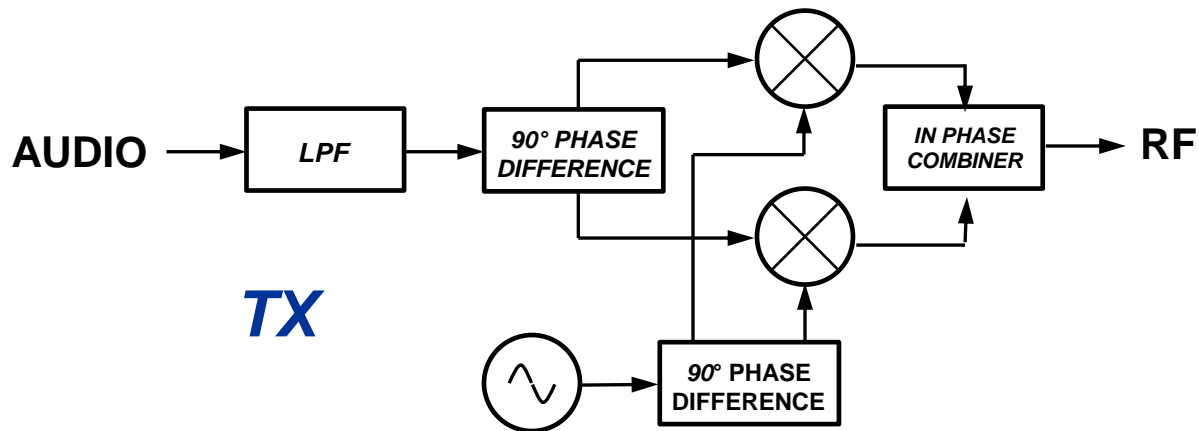


TX



DUAL ALLPASS 90° PHASE SPLITTER

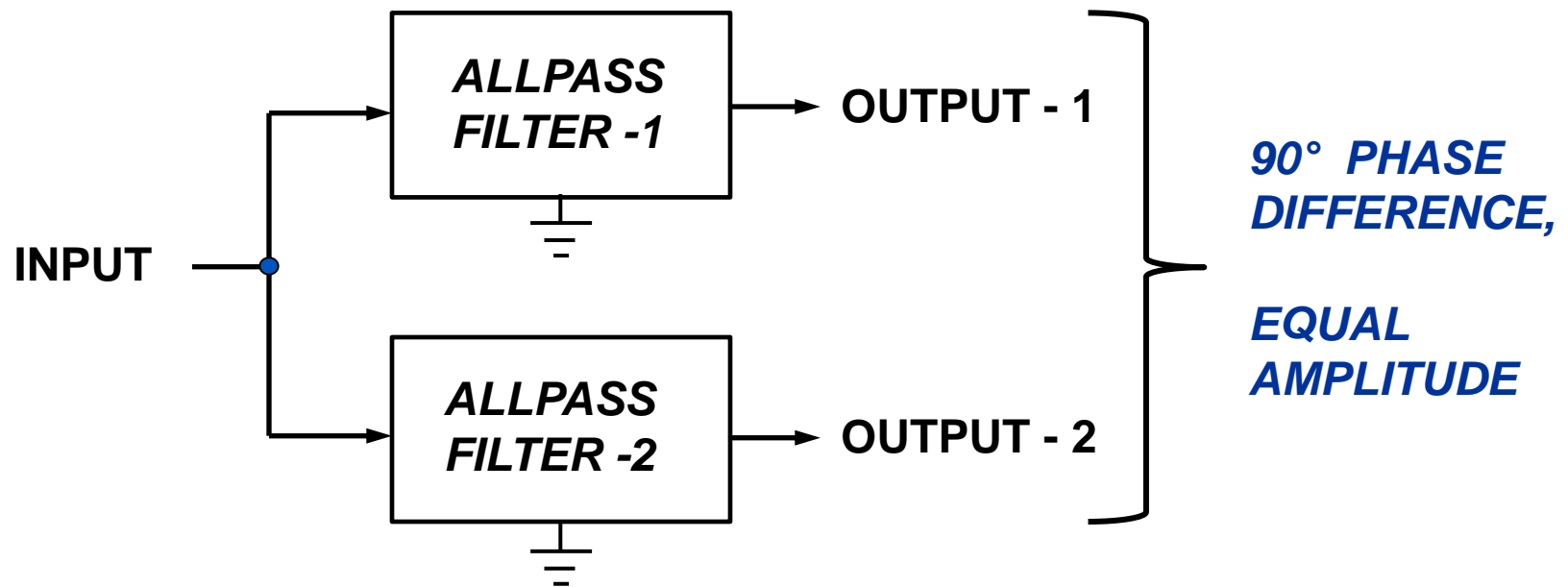

DUAL ALLPASS 90° PHASE COMBINER

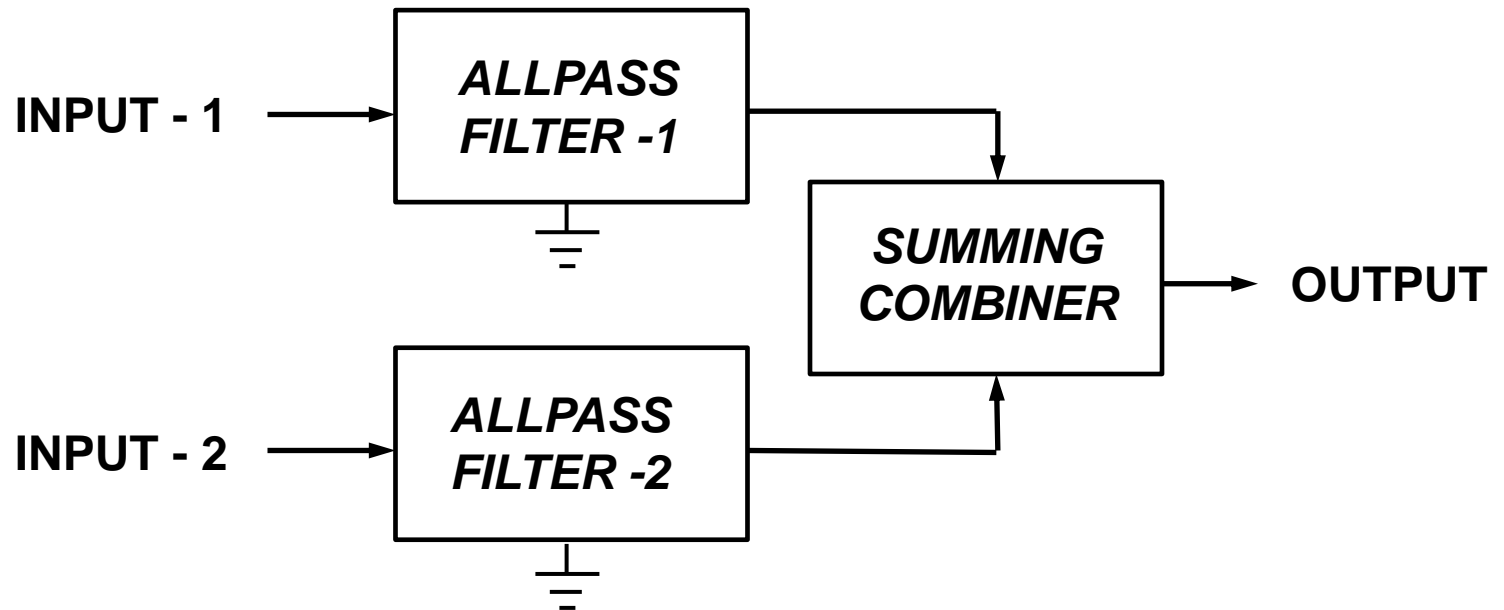

ALLPASS FILTER RESPONSE

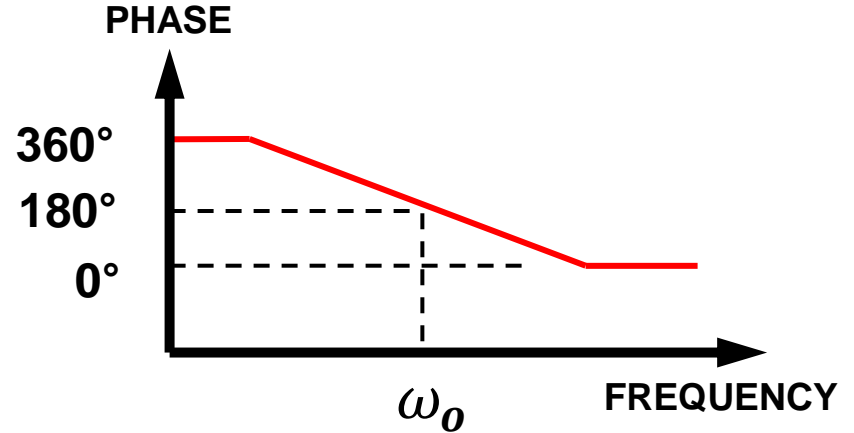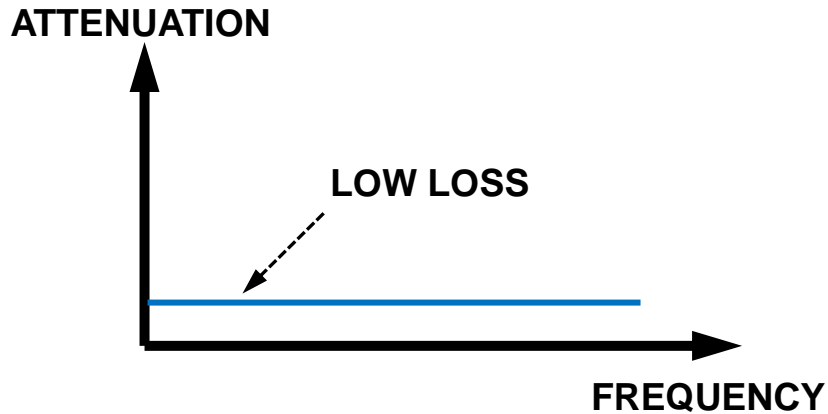


$$\frac{V_{output}}{V_{input}} = \frac{-\omega^2 - j\frac{\omega_0}{Q}\omega + \omega_0^2}{-\omega^2 + j\frac{\omega_0}{Q}\omega + \omega_0^2}$$

$\omega = 2\pi \text{ frequency}$

ω_0 and Q are constants

DUAL ALLPASS PHASE RESPONSE

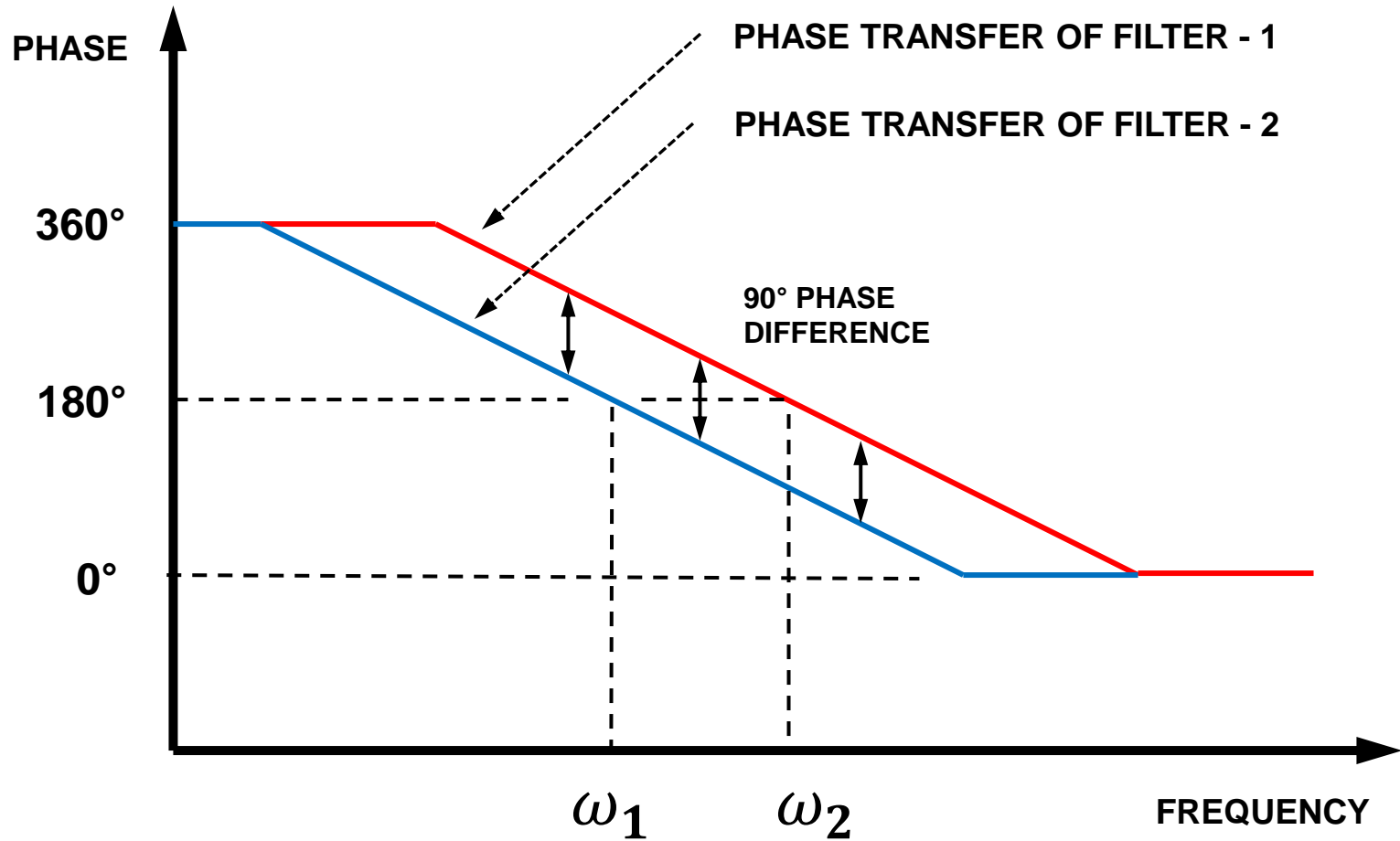

SECOND ORDER FILTER FUNCTIONS (BIQUADS)

FILTER RESPONSE TYPE

LOW PASS

HIGH PASS

BAND PASS

BAND REJECT

ALLPASS
(DELAY EQUALIZER)

TRANSFER FUNCTION

$$K \frac{1}{S^2 + \frac{\omega_o}{Q} S + \omega_o^2}$$

$$K \frac{S^2}{S^2 + \frac{\omega_o}{Q} S + \omega_o^2}$$

$$K \frac{S}{S^2 + \frac{\omega_o}{Q} S + \omega_o^2}$$

$$K \frac{S^2 + \omega_o^2}{S^2 + \frac{\omega_o}{Q} S + \omega_o^2}$$

$$K \frac{S^2 - \frac{\omega_o}{Q} S + \omega_o^2}{S^2 + \frac{\omega_o}{Q} S + \omega_o^2}$$


BIQUAD TRANSFER FUNCTION

$$T(S) = \frac{S^2 + \frac{\omega_Z}{Q_Z} S + \omega_Z^2}{S^2 + \frac{\omega_P}{Q_P} S + \omega_P^2}$$


ω_Z and ω_P are zero and pole frequencies

Q_Z and Q_P are zero and pole Qs

ACTIVE FILTER BIQUAD REALIZATIONS

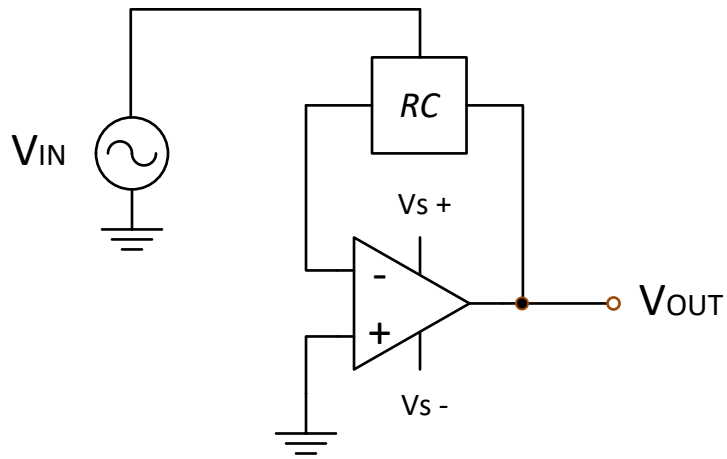


**NEGATIVE FEEDBACK
TOPOLOGY**

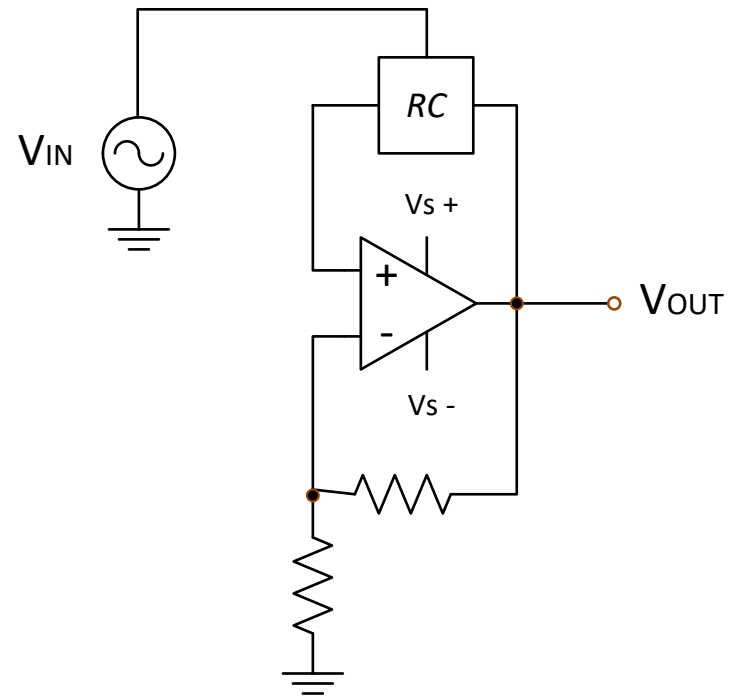

**POSITIVE FEEDBACK
TOPOLOGY**


STEFFEN ALLPASS FILTER

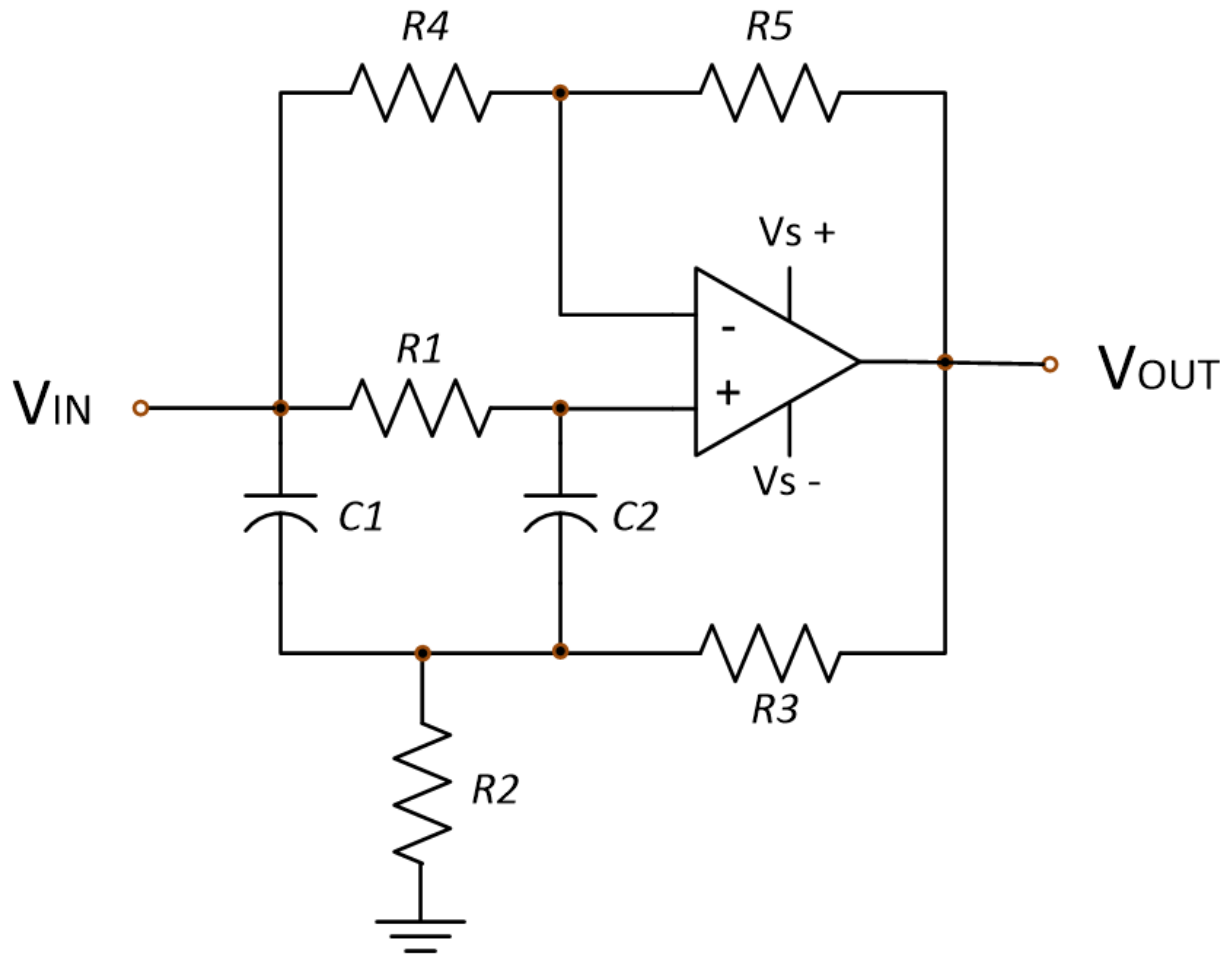

STEFFEN ALLPASS TRANSFER FUNCTION

$$\frac{V_{out}}{V_{in}} = \frac{-\omega^2 - j\omega \left[\frac{R_4}{R_5} \left(\frac{1}{R_2} + \frac{1}{R_3} \right) \frac{1}{C_1} - \frac{1}{R_1 C_1} - \frac{1}{R_1 C_2} \right] + \frac{1}{R_1 C_1 C_2} \left(\frac{1}{R_2} + \frac{1}{R_3} \right)}{-\omega^2 + j\omega \left[\frac{1}{R_1 C_2} + \frac{1}{R_1 C_1} + \left(\frac{1}{R_2} + \frac{1}{R_3} \right) \frac{1}{C_1} - \frac{1}{R_3 C_1} \left(1 + \frac{R_4}{R_5} \right) \right] + \frac{1}{R_1 C_1 C_2} \left(\frac{1}{R_2} + \frac{1}{R_3} \right)}$$

STEFFEN DUAL ALLPASS FILTERS

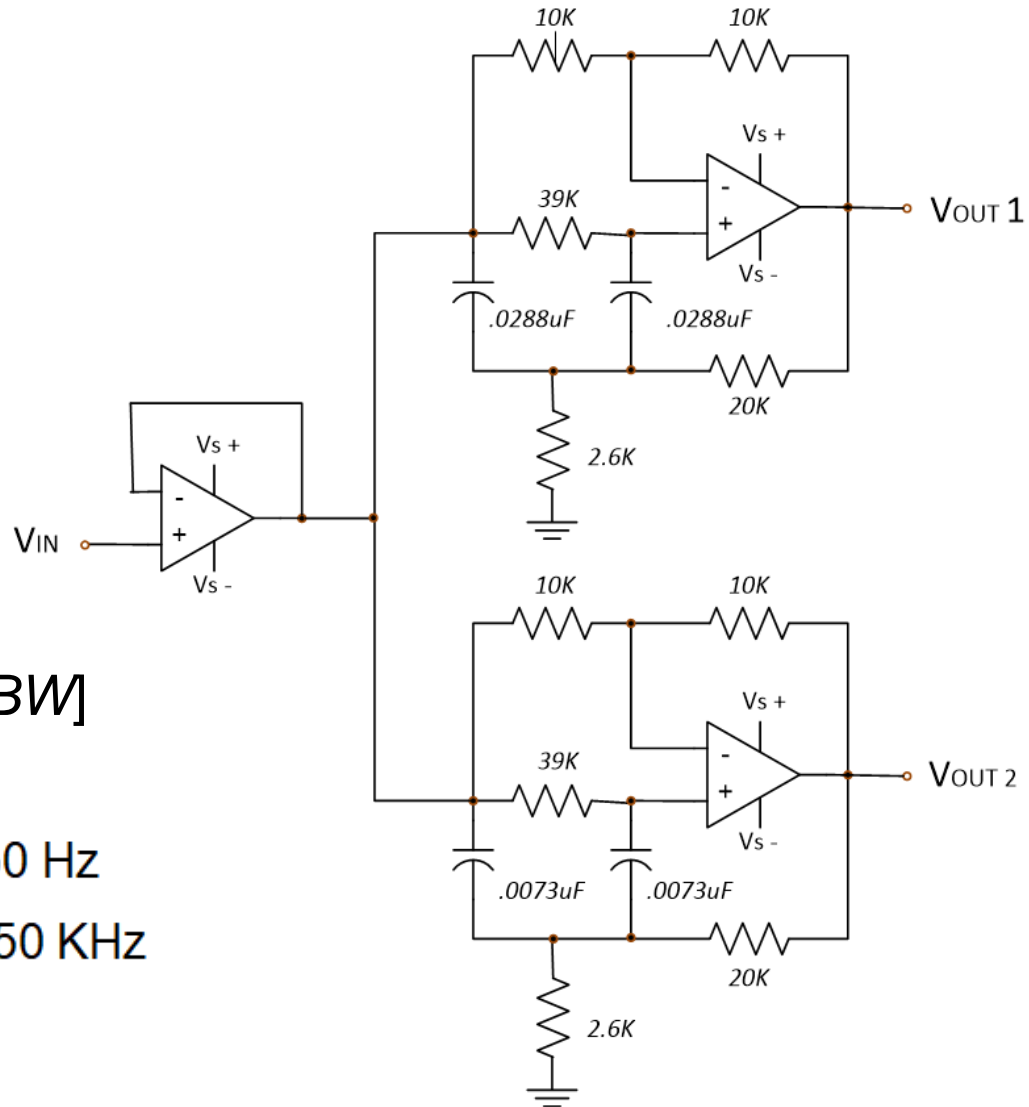


[for decade BW]

$$Q = 0.27553$$


$$\omega_1 = (2\pi) 350 \text{ Hz}$$

$$\omega_2 = (2\pi) 3.50 \text{ KHz}$$

DUAL ALLPASS FILTER – PHASE RESPONSES

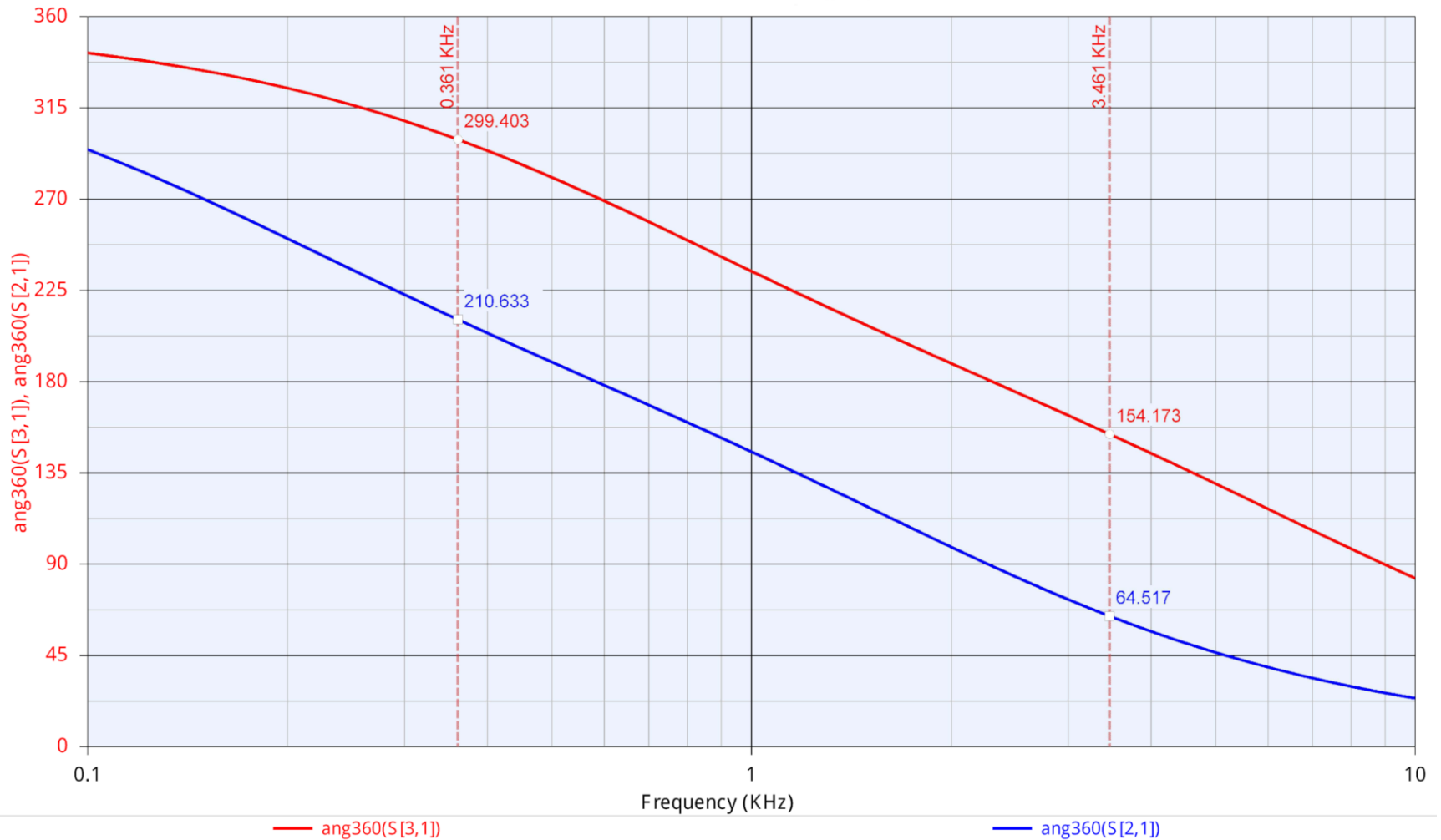

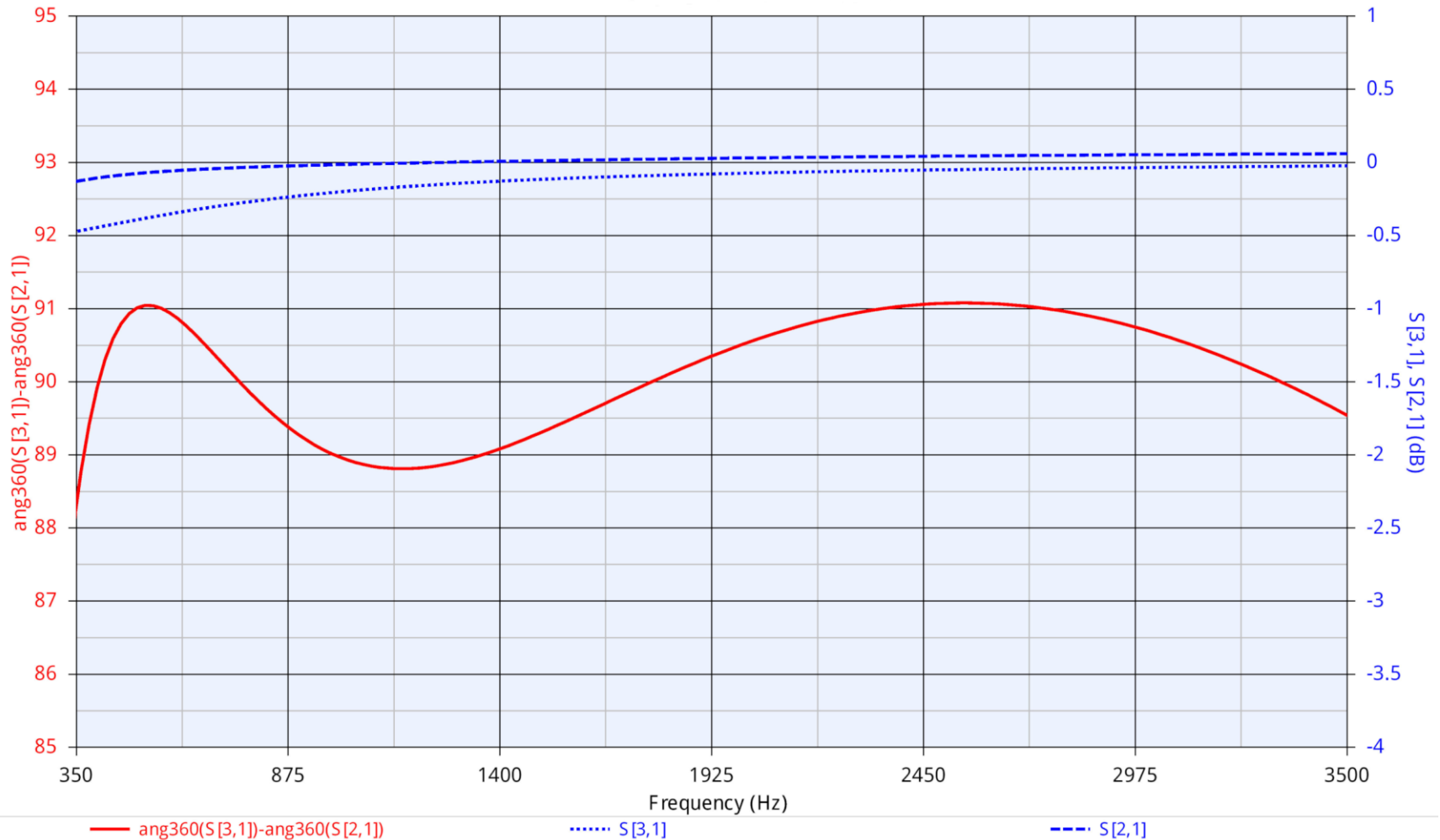DUAL ALLPASS FILTER – RESPONSE COMPARISON



NORMALIZED PROTOTYPE PARAMETERS

SECOND ORDER PROTOTYPE

BW RATIO	Q	ω_1	ω_2	PHASE ERROR
3	0.31011	0.53488	1.87003	0.074°
4	0.30348	0.52811	1.89315	0.178°
5	0.29767	0.52381	1.90940	0.308°
6	0.29206	0.51853	1.92700	0.455°
8	0.28334	0.50984	1.95934	0.770°
10	0.27553	0.50292	1.98650	1.080°
15	0.26010	0.48829	2.04241	1.910°
20	0.25003	0.47960	2.08534	2.550°

$$T_1(S) = \frac{S^2 - \frac{\omega_1}{Q_1}S + \omega_1^2}{S^2 + \frac{\omega_1}{Q_1}S + \omega_1^2}$$

$$T_2(S) = \frac{S^2 - \frac{\omega_2}{Q_2}S + \omega_2^2}{S^2 + \frac{\omega_2}{Q_2}S + \omega_2^2}$$

$$\omega_0 = \sqrt{\omega_1\omega_2} = 1$$

THIRD ORDER PROTOTYPE

BW RATIO	Q1	ω_1	γ_1	Q2	ω_2	γ_2	PHASE ERROR
6	0.19231	0.5500	0.7310	0.19206	1.81750	1.3700	0.020°
8	0.18354	0.5458	0.7200	0.18347	1.83064	1.3880	0.040°
10	0.17560	0.5420	0.7110	0.17652	1.84217	1.4100	0.070°

$$T_1(S) = \left(\frac{S^2 - \frac{\omega_1}{Q_1}S + \omega_1^2}{S^2 + \frac{\omega_1}{Q_1}S + \omega_1^2} \right) \left(\frac{\gamma_1 - S}{\gamma_1 + S} \right) \quad T_2(S) = \left(\frac{S^2 - \frac{\omega_2}{Q_2}S + \omega_2^2}{S^2 + \frac{\omega_2}{Q_2}S + \omega_2^2} \right) \left(\frac{\gamma_2 - S}{\gamma_2 + S} \right)$$


$$\omega_0 = \sqrt{\omega_1\omega_2} = 1 \quad \gamma_0 = \sqrt{\gamma_1\gamma_2} = 1$$

ALLPASS FILTER CONSIDERATIONS

- Baseband audio filters
 - Active biquad designs, like Steffen
 - Low Q poles and zeros
- RF filters
 - Passive filters
 - Non-minimum phase transfer cannot be realized as ladder
 - ✓ Lattice networks with baluns
 - ✓ Bridge-T networks
- Allpass filters always have pole-zero symmetry *WRT* $j\omega$ axis
- First order:
$$T(S) = \left(\frac{\gamma - S}{\gamma + S} \right)$$
- Second order:
$$T(S) = \frac{S^2 - \frac{\omega_0}{Q_0} S + \omega_0^2}{S^2 + \frac{\omega_0}{Q_0} S + \omega_0^2}$$
- Third order:
$$T(S) = \left(\frac{S^2 - \frac{\omega_0}{Q_0} S + \omega_0^2}{S^2 + \frac{\omega_0}{Q_0} S + \omega_0^2} \right) \left(\frac{\gamma - S}{\gamma + S} \right)$$

LATTICE ALLPASS FILTERS


FIRST ORDER

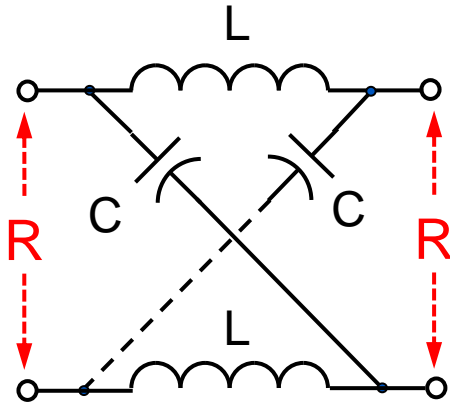

$$L = \frac{R}{\gamma}$$

$$C = \frac{L}{R^2}$$

SECOND ORDER

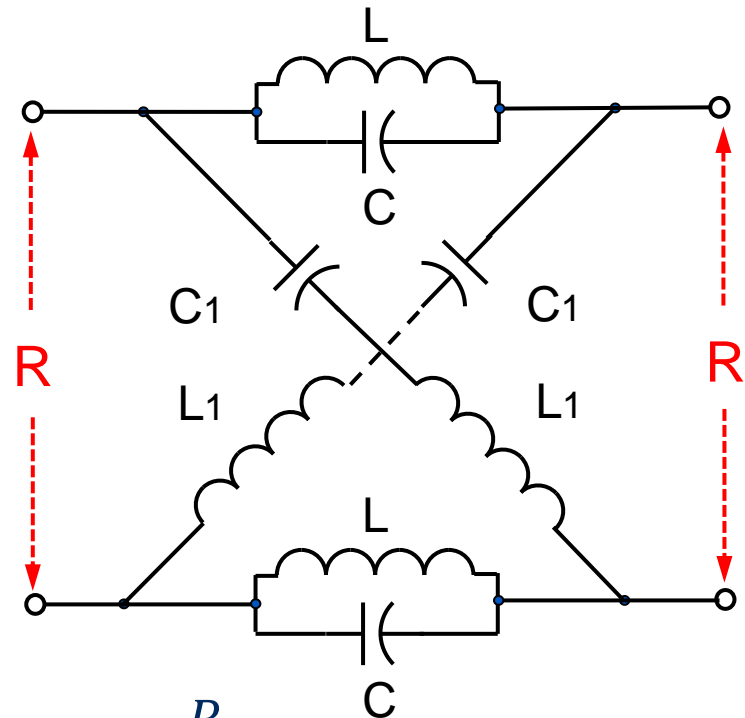

$$L = \frac{R}{\omega_0}$$

$$L_1 = CR^2$$

$$C = \frac{1}{L \omega_0^2}$$

$$C_1 = \frac{L}{R^2}$$

CASCADE 1st ORDER to 2nd ORDER LATTICE


- For applications here, the pole / zero Q is always < 0.5
- System is over-damped; so, poles and zeros are real and distinct
- Allows: 2nd order lattice equivalence to cascaded 1st order lattices

$$T(S) = A(S)B(S) = \left(\frac{S_a - S}{S_a + S} \right) \left(\frac{S_b - S}{S_b + S} \right)$$


$$T(S) = \frac{S^2 - (S_a + S_b)S + S_a S_b}{S^2 + (S_a + S_b)S + S_a S_b}$$

$$\omega_o = \sqrt{S_a S_b} \quad Q = \frac{\sqrt{S_a S_b}}{S_a + S_b} \quad \frac{\omega_o}{Q} = S_a + S_b$$

CASCADE 1st ORDER to 2nd ORDER LATTICE

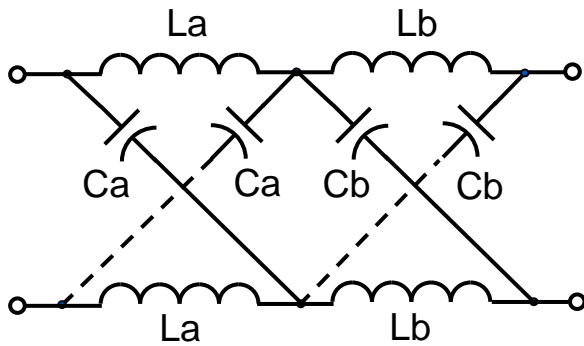

=

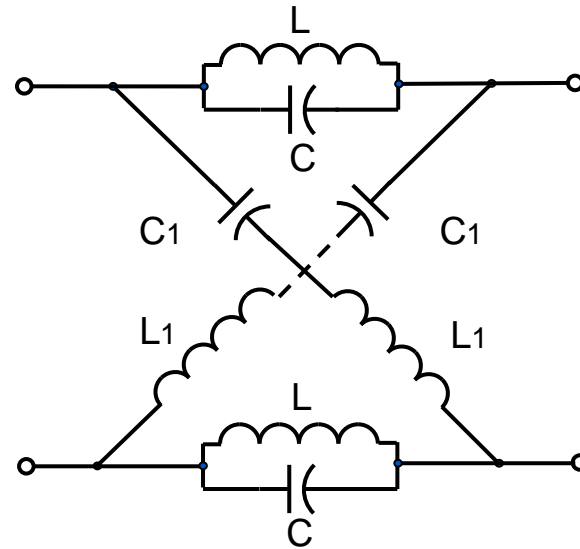

$$L = L_a + L_b$$



$$C_1 = C_a + C_b$$

$$C = \frac{C_a C_b}{C_a + C_b}$$

$$L_1 = \frac{L_a L_b}{L_a + L_b}$$


LOWPASS BASEBAND AUDIO FILTER

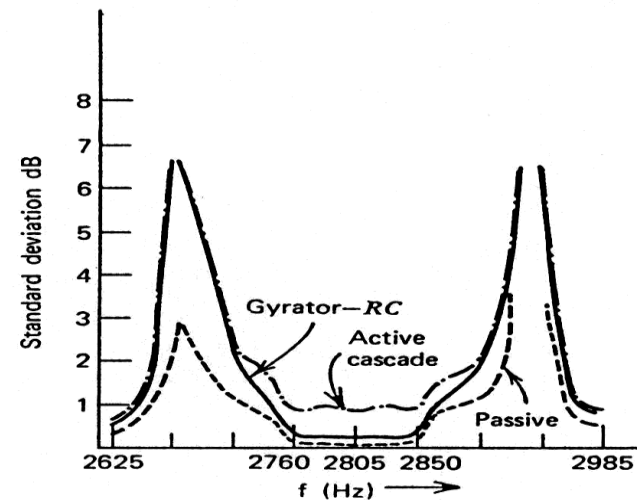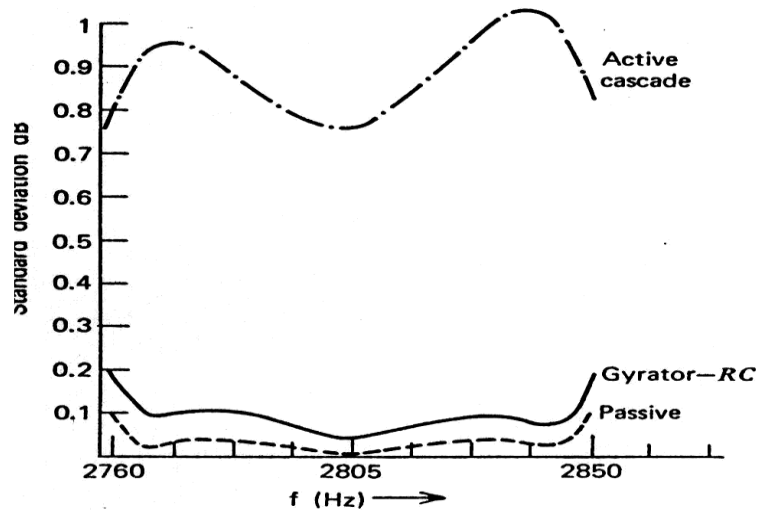- Lowpass active filters have high Q poles




- Cascaded biquad blocks are have higher sensitivity than passive
- Active filters based on passive designs have lower sensitivity:
 - Gyrator substitution for inductors
 - Frequency Dependent Negative Resistor (FDNR)

FOURTH ORDER PASSIVE BPF

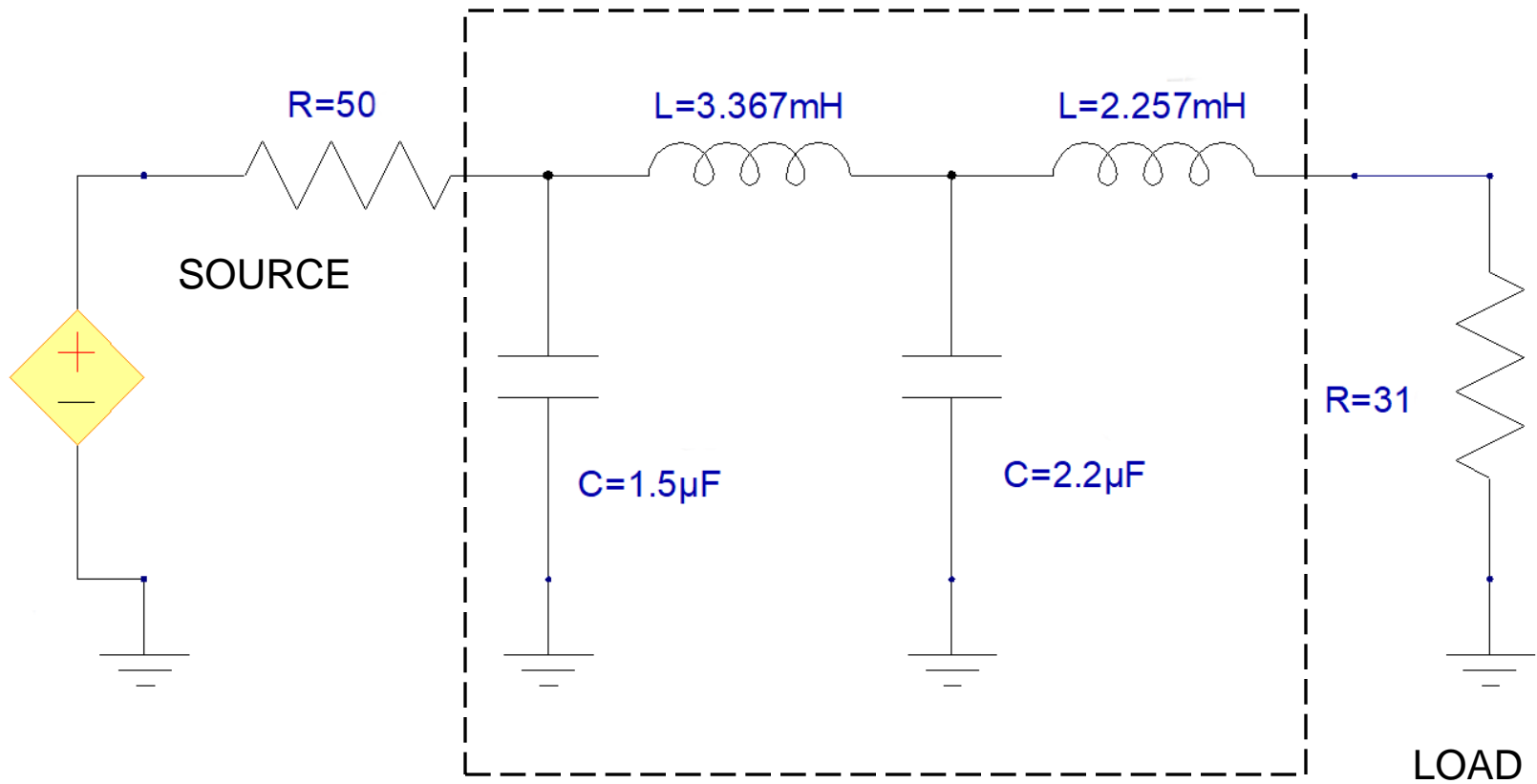


PASSIVE BASED ACTIVE BPF

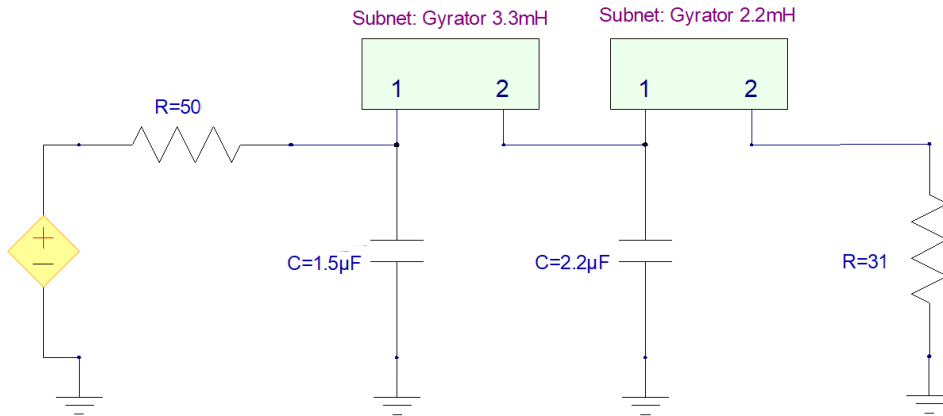

**GYRATORS PROVIDE
INDUCTOR EQUIVALENT BY
INVERTING CAPACITOR
IMPEDANCE**


$$L_{eqv} = K^2 C$$

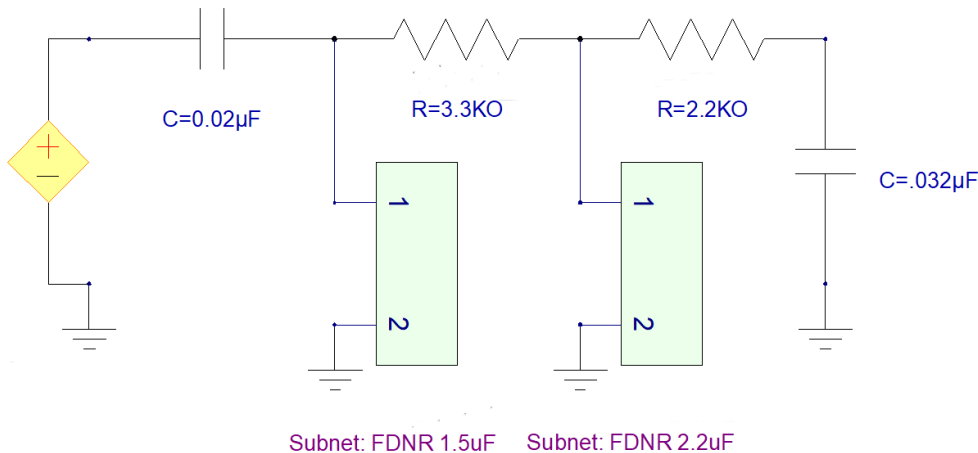


**FDNR SOLUTION OBTAINED
BY Z-SCALING PASSIVE
LADDER ELEMENTS BY: K/S**

<u>PASSIVE</u>		<u>FDNR</u>
R	\Rightarrow	$\frac{R K}{S}$
$S L$	\Rightarrow	$L K$
$\frac{1}{S C}$	\Rightarrow	$\frac{K}{S^2 C} = \frac{1}{S^2 D}$

LPF RESPONSE

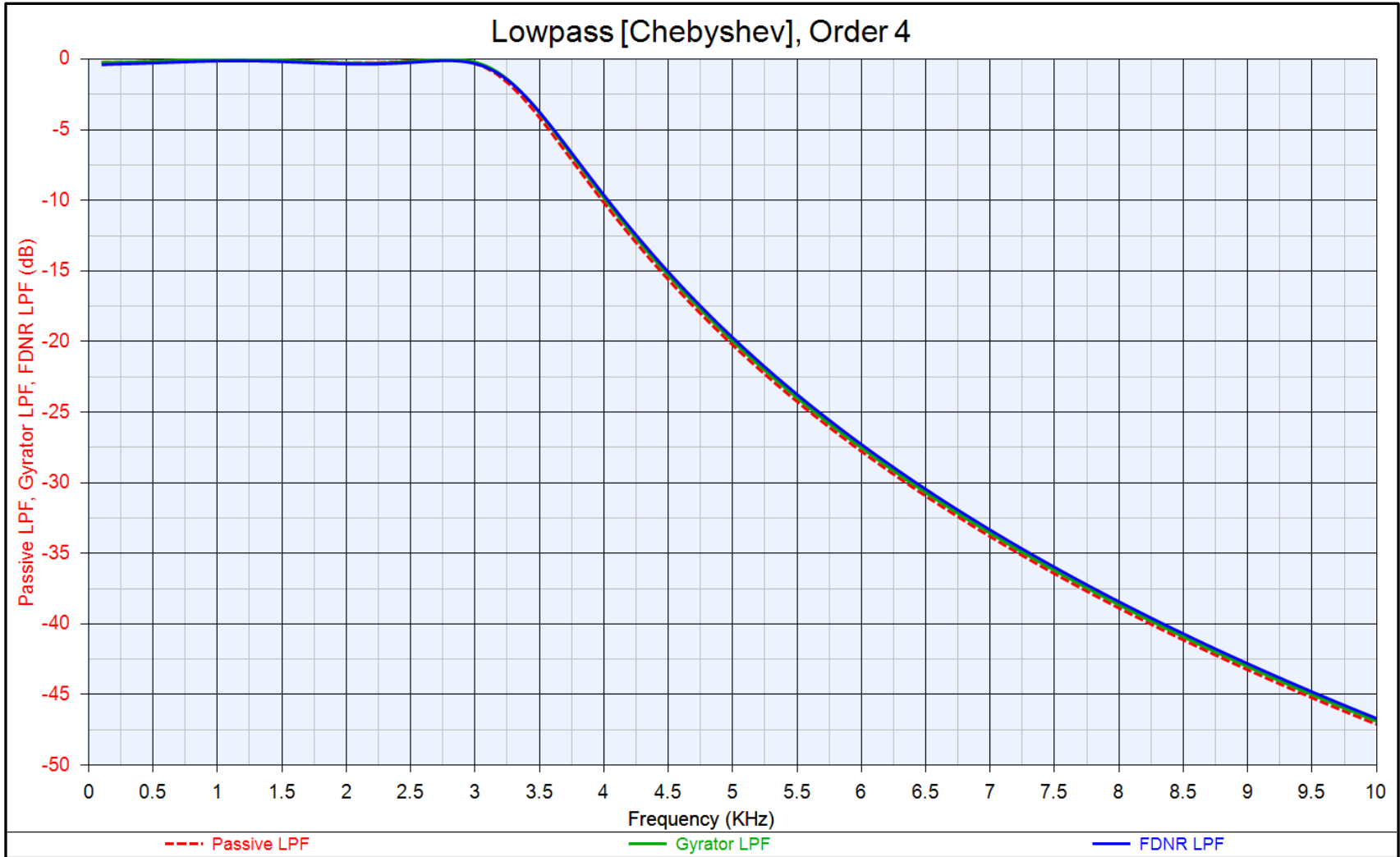

RIORDAN'S GYRATOR – AS INDUCTOR

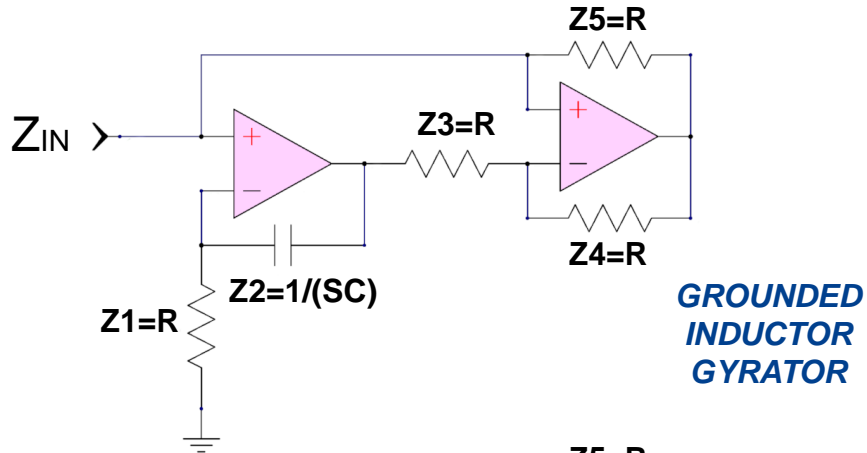


$$Z_{IN} = \frac{Z_1 Z_3 Z_5}{Z_2 Z_4}$$

$$Z_2 = (C S)^{-1}$$


$$Z_1 = Z_3 = Z_4 = Z_5 = R$$

$$Z_{IN} = SCR^2$$

$$L_{eff} = CR^2$$

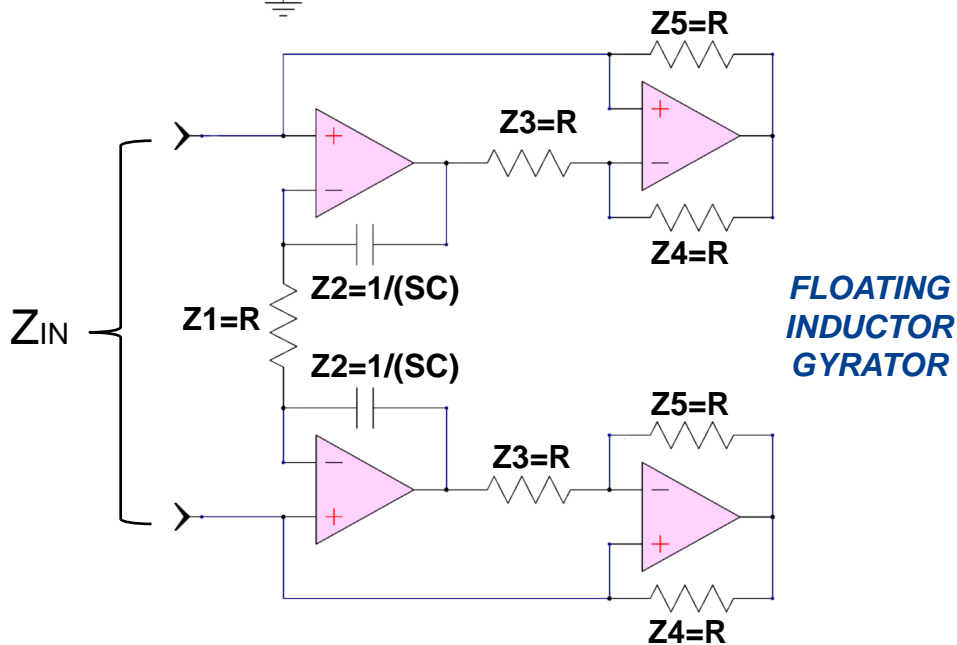

BRUTON'S FDNR

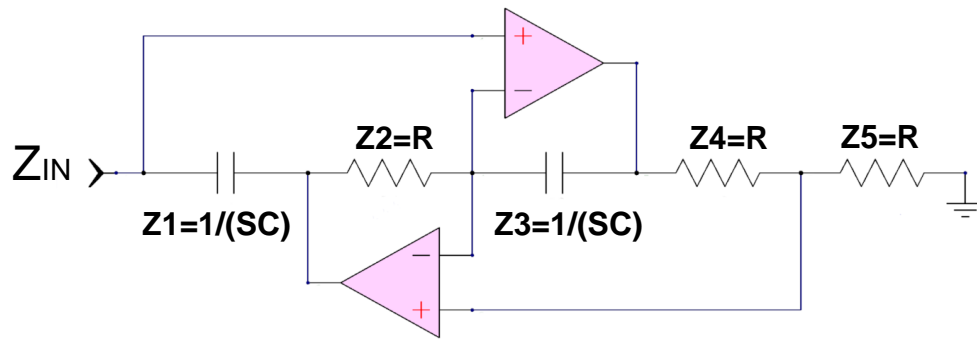


GROUNDING FDNR

$$Z_{IN} = \frac{Z_1 Z_3 Z_5}{Z_2 Z_2}$$

$$Z_1 = Z_3 = (C_D S)^{-1}$$

$$Z_2 = Z_4 = Z_5 = R_D$$
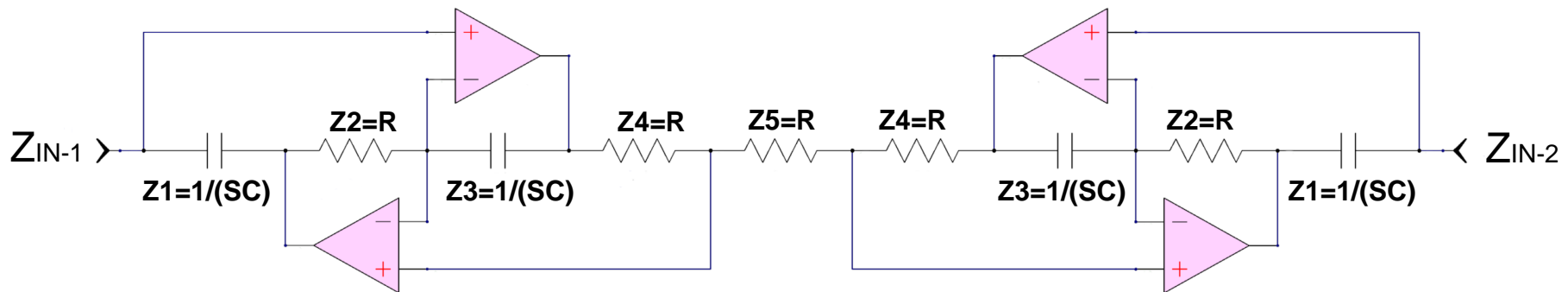
$$Z_{IN} = \frac{1}{S^2 R_D C_D^2} = \frac{1}{S^2 D}$$



FLOATING FDNR

SUMMARY

- SSB (image reject) direct conversion blocks
- Audio band limiting filter is key to setting selectivity
- Phase difference networks are obtained from a pair of allpass delay equalizers
- Audio phase difference networks are realized with Steffen allpass filters
- Wideband RF passive phase difference networks are realized as a pair of 2nd order lattice filters (with balun)
- Active filter sensitivity discussed
- Audio band limiting active filters based on passive ladders are preferred for low sensitivity.