

# RF Power Amplifier Design

Markus Mayer & Holger Arthaber

Department of Electrical Measurements and Circuit Design  
Vienna University of Technology

June 11, 2001



## Contents

- Basic Amplifier Concepts
  - Class A, B, C, F, hHCA
  - Linearity Aspects
  - Amplifier Example
  
- Enhanced Amplifier Concepts
  - Feedback, Feedforward, ...
  - Predistortion
  - LINC, Doherty, EER, ...




TECHNISCHE UNIVERSITÄT WIEN

## Efficiency Definitions

○ Drain Efficiency:  $h_D = \frac{P_{OUT}}{P_{DC}}$


○ Power Added Efficiency:  $h_{PA} = \frac{P_{OUT} - P_{IN}}{P_{DC}} = h_D \cdot \left(1 - \frac{1}{G}\right)$
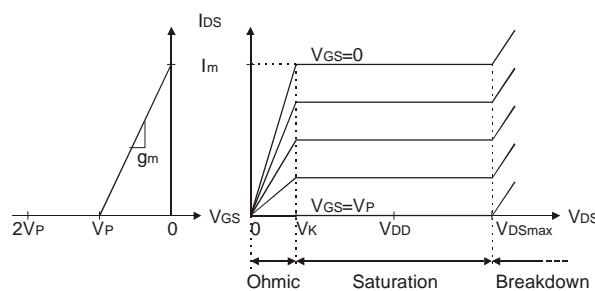
## Ideal FET Input and Output Characteristics




$$k = \frac{V_{DD} - V_K}{V_{DD}}$$

## Maximum Output Power Match

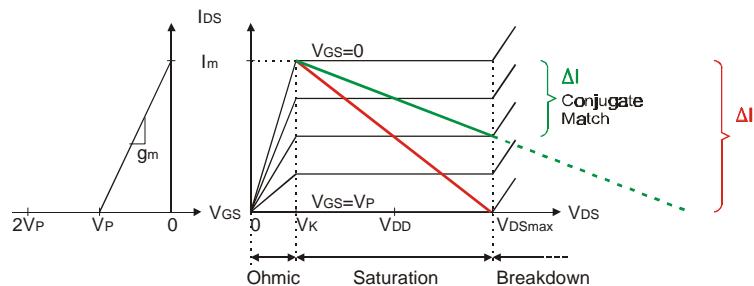


$$R_{OPT} = \frac{V_{DS_{max}} - V_K}{I_m}$$

## Class A

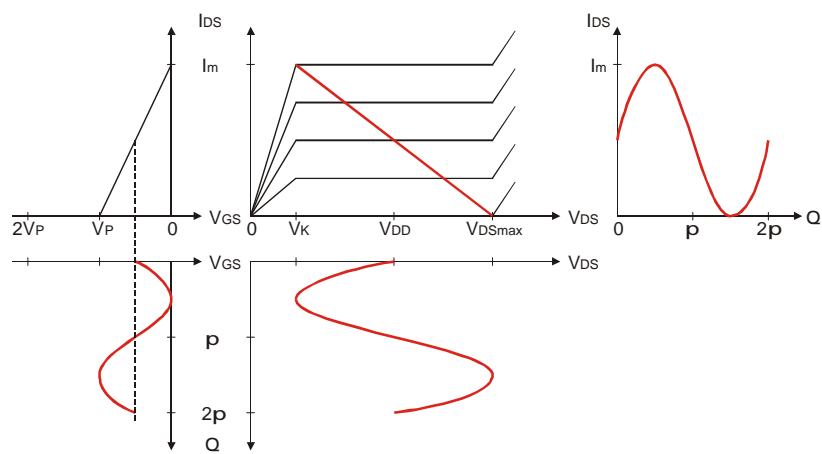

## Class A – Circuit

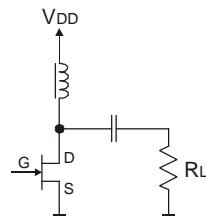


$$h_D = k \cdot 50\%$$


$$G = G_A \quad (\text{e.g. } 14 \text{ dB})$$

$$h_{PA} = k \cdot 48\%$$


## Class B

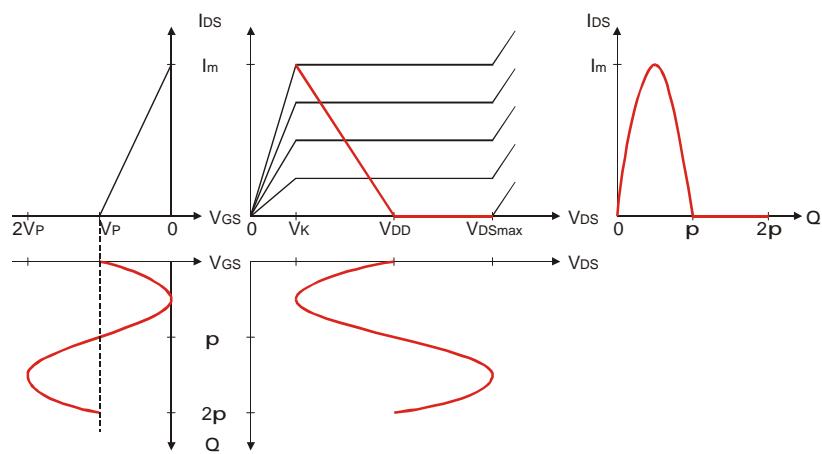

## Class C

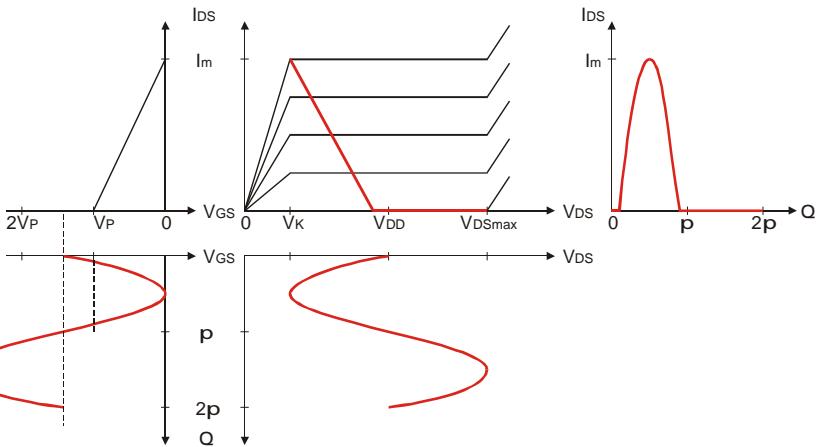

## Class B and C – Circuit

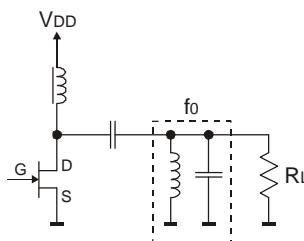

### Class B

$$h_D = k \cdot 78\%$$


$$G = G_A - 6\text{dB} \quad (8\text{ dB})$$

### Class C

$$h_D \rightarrow 100\%$$


$$G \rightarrow 1$$

## Influence of Conduction Angle

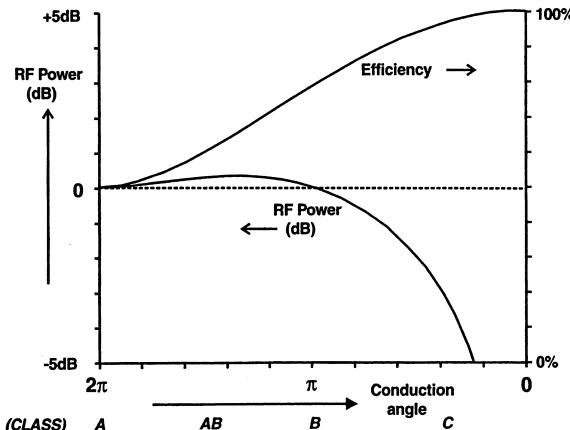


11
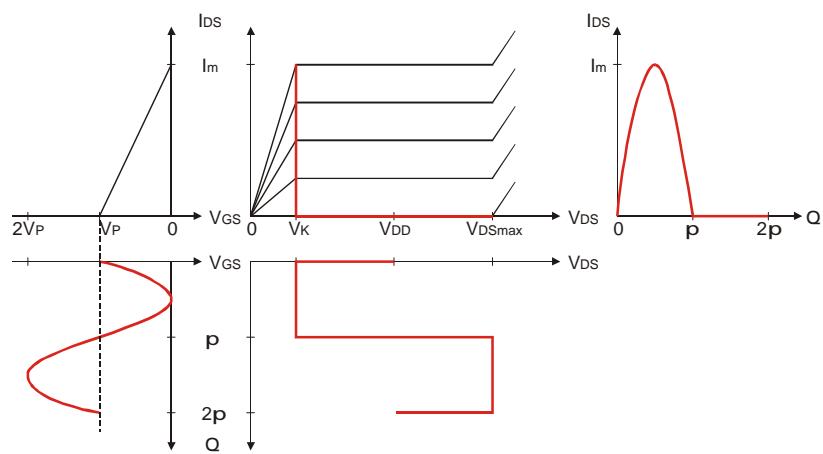
## Class F (HCA ... harmonic controlled amplifier)




12

## hHCA (half sinusoidally driven HCA)

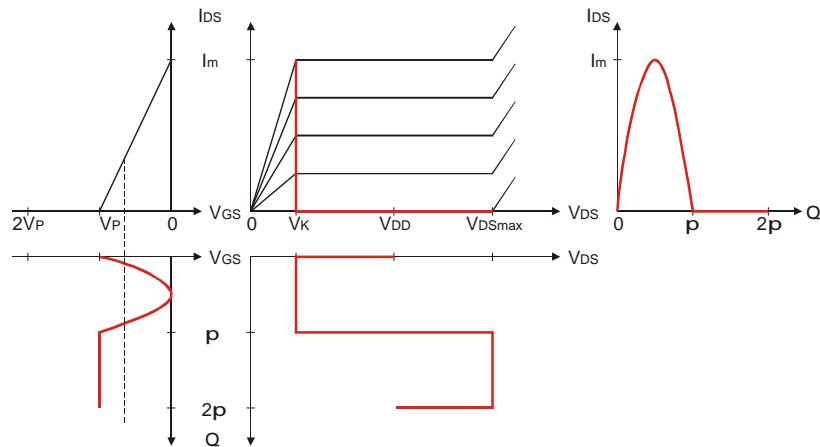

## Class F and hHCA – Circuit

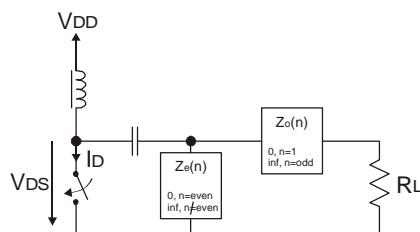

Class F

$$h_D = k \cdot 100\%$$

$$G = G_A - 5 \text{ dB} \quad (9 \text{ dB})$$

hHCA


$$h_D = k \cdot 100\%$$

$$G = G_A + 1 \text{ dB} \quad (15 \text{ dB})$$


$$h_{PA} = k \cdot 87\%$$

$$h_{PA} = k \cdot 96\%$$

## hHCA - Third Harmonic Peaking

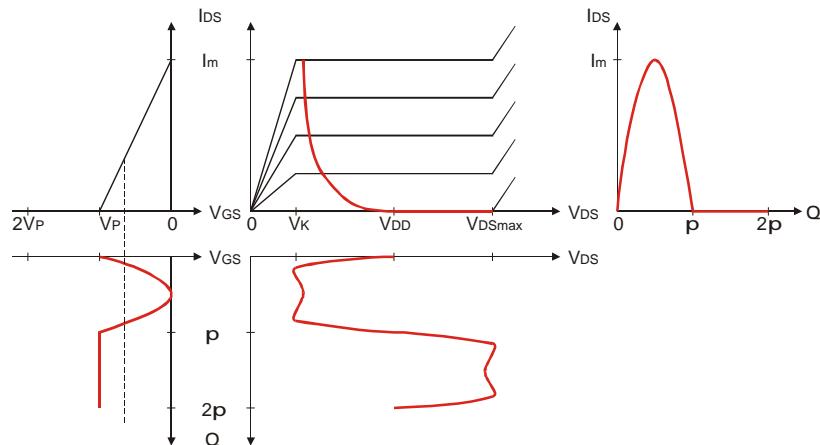

## Third Harmonic Peaking – Circuit

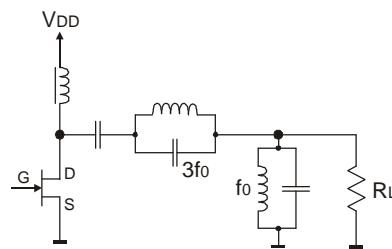


$$h_D = k \cdot 91\%$$


$$G = G_A + 0.6 \text{ dB} \quad (14.6 \text{ dB})$$

$$h_{PA} = k \cdot 87\%$$


## Linearity Aspects

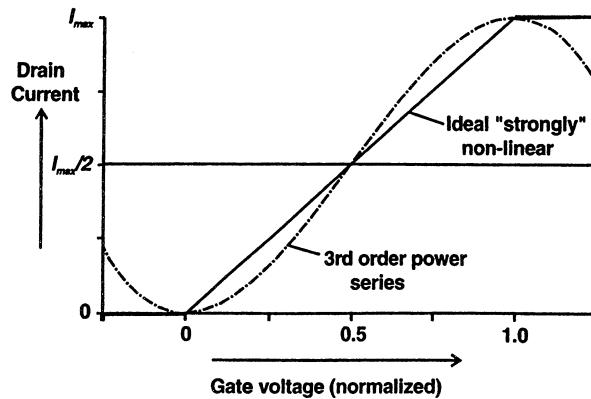

## Linearity Aspects

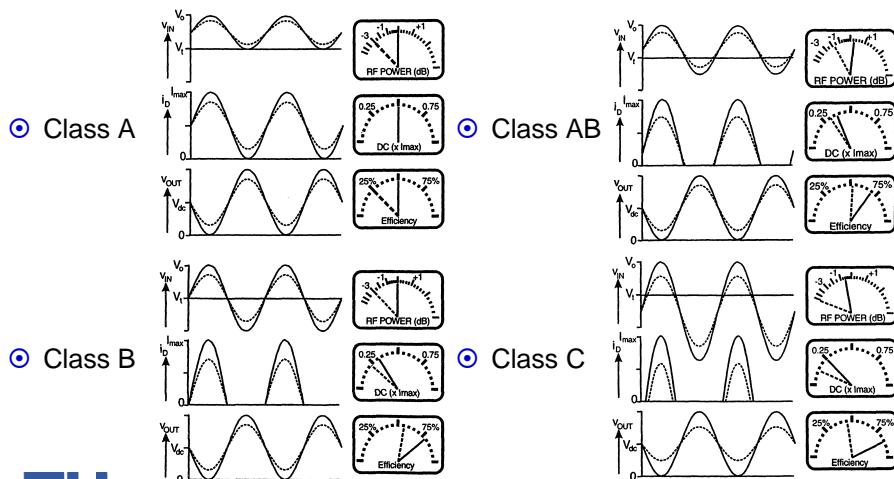


## Linearity Aspects

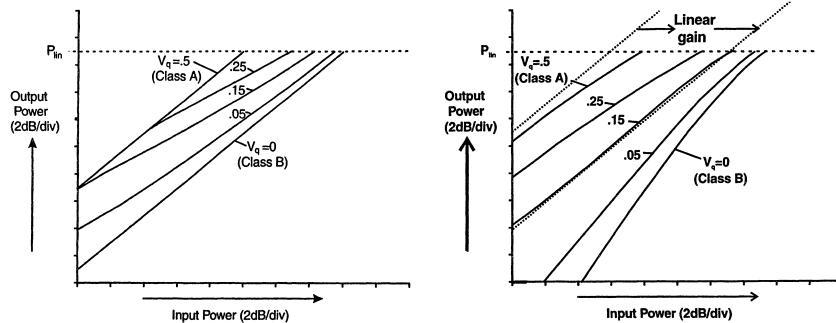

- Ideal strongly nonlinear model
- Strong-weak nonlinear model


## Amplifier Design – An Example

- Balanced Amplifier Configuration

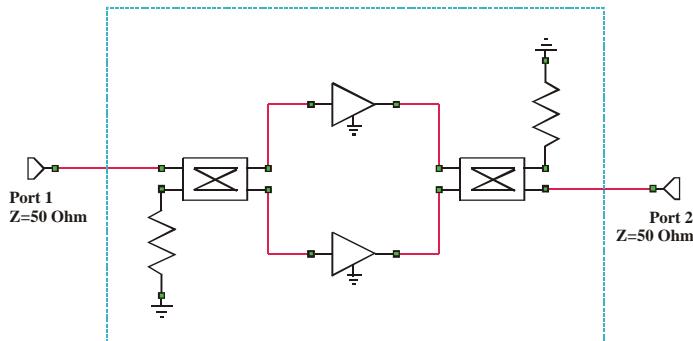


# Amplifier Design - Simulation

## ○ Gate & Drain Waveforms

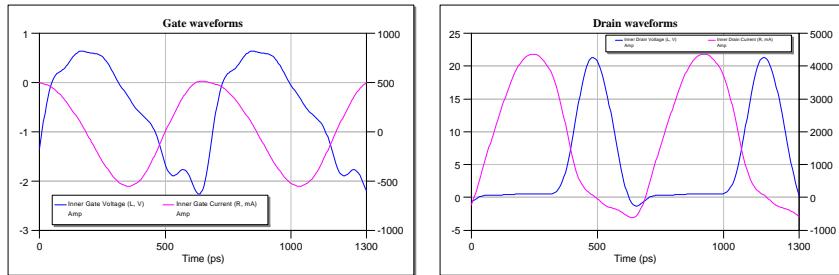


# Amplifier Design - Simulation

## ○ Dynamic Load Line & Power Sweep

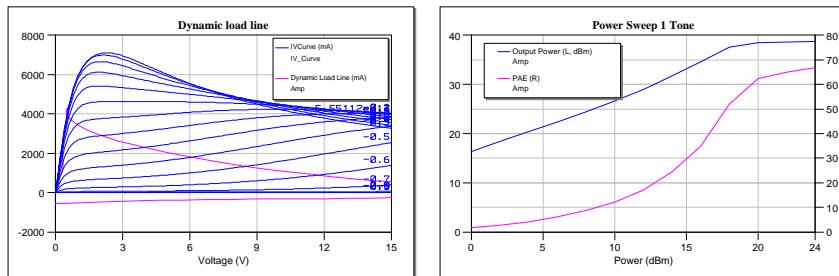


# Amplifier Design – Measurements

- Single Tone & Two Tone

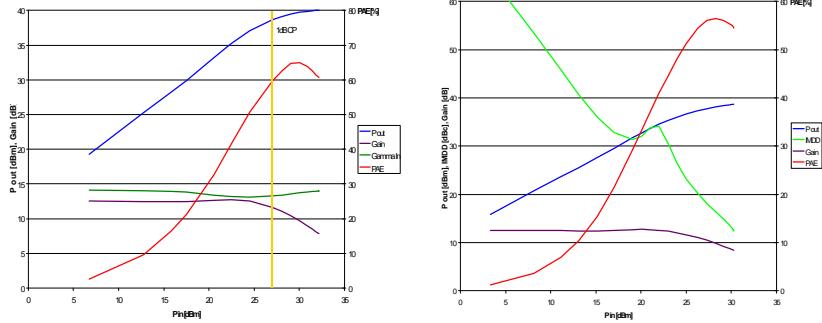

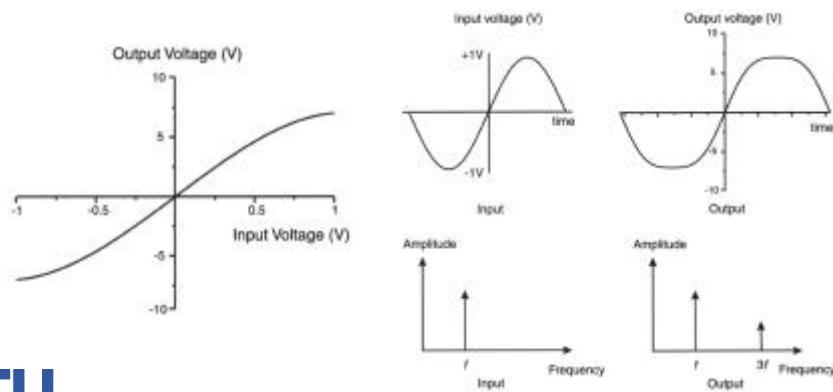
# Amplifier Nonlinearity

- Gain and Phase depends on Input Signal
- 3<sup>rd</sup> Order Gain-Nonlinearities:


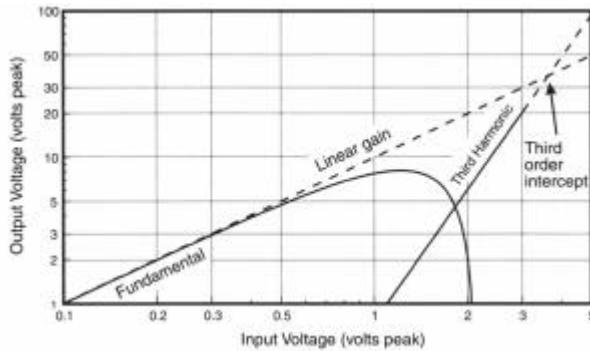
## Amplifier Nonlinearity


- Higher Output Level (close to Saturation) results in more Distortion/Nonlinearity




## Nonlinearity leads to?

- Generation of Harmonics
- Intermodulation Distortion / Spectral Regrowth
- SNR (NPR) Degradation
- Constellation Deformation

## Intermodulation and Harmonics

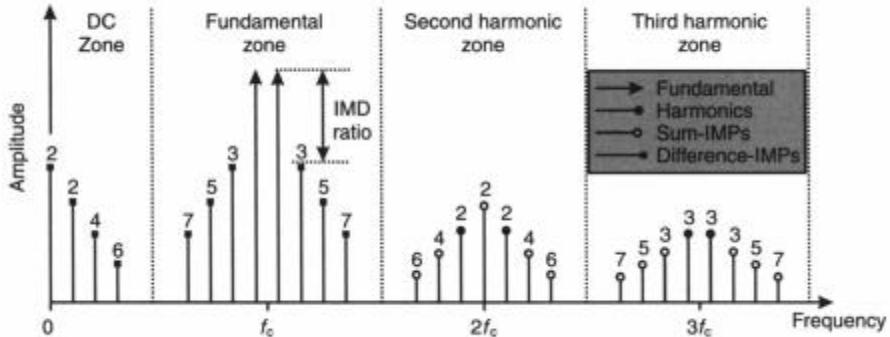


## Spectral Regrowth

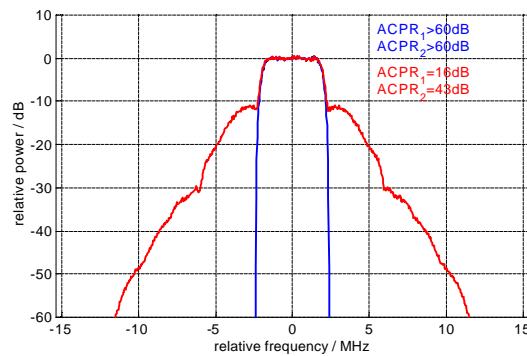


- Energy in adjacent Channels
- ACPR (Adjacent Channel Leakage Power Ratio) increases

## Reduced NPR (Noise Power Ratio)

- Input Signal

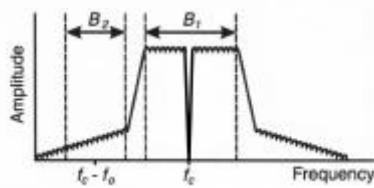


- Output Signal of Nonlinear Amplifier

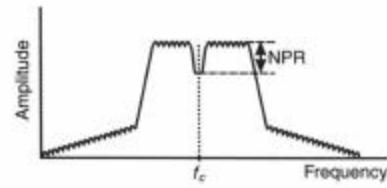


- Degradation of Inband SNR
- „Noisy“ Constellation

## Constellation Deformation

- Input Signal

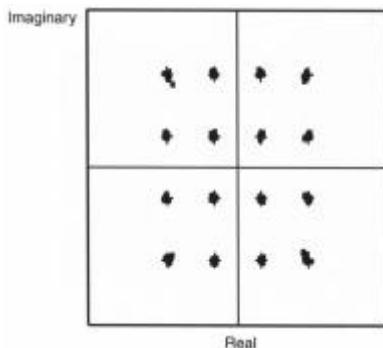

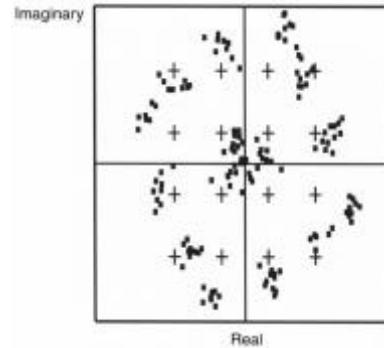- Output Signal of Nonlinear Amplifier (with Gain- and Phase-Distortion)



# Modeling of Nonlinearities

- with Memory-Effects

- Volterra Series (=„Taylor Series with Memory“)




- without Memory-Effects

- Saleh Model  $f(r) = \frac{a_a r}{1 + b_a r^2}$      $g(r) = \frac{a_\Theta r^2}{1 + b_\Theta r^2}$
- Taylor Series
- Blum and Jeruchim Model
- AM/AM- and AM/PM-conversion

 better performance


# AM/AM- and AM/PM-Conversion

- GaAs-PA

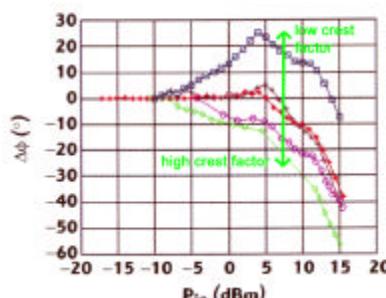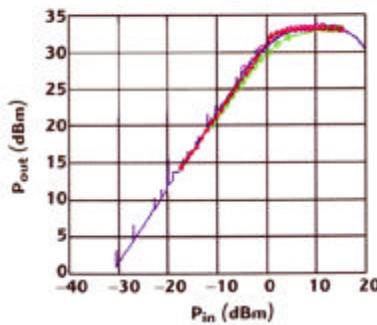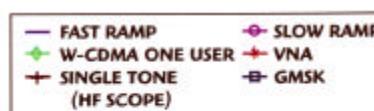

## AM/AM- and AM/PM-Conversion

- LDMOS-PA

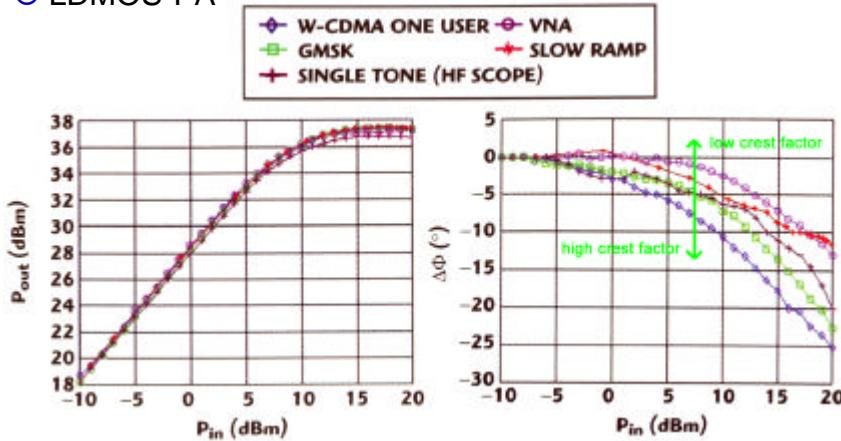

33

## How to preserve Linearity?

- Backed-Off Operation of PA
  - Simplest Way to achieve Linearity
  
- Linearity improving Concepts
  - Predistortion
  - Feedforward
  - ...

34

## How to preserve Efficiency?


- Efficiency improving Concepts

- Doherty
- Envelope Elimination and Restoration
- ...

- Linearity improving Concepts


- Higher Linearity at constant Efficiency  
→ Higher Efficiency at constant Linearity

## Direct (RF) Feedback

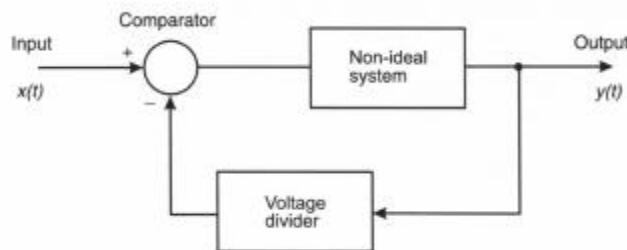


- Classical Method
- Decrease of Gain → Low Efficiency
- Feedback needs more Bandwidth than Signal
- Stability Problems at high Bandwidths

## Distortion Feedback

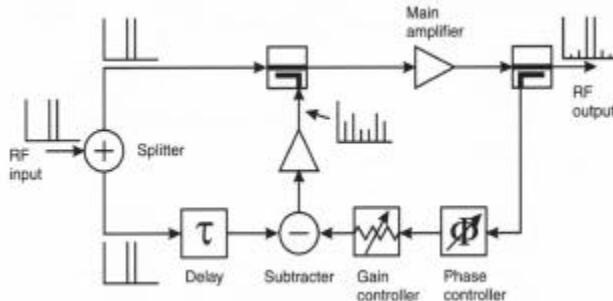



- Feedback of outband Products only
- Higher Gain than RF feedback
- Stability Problems due to Reverse Loop

## Feedforward

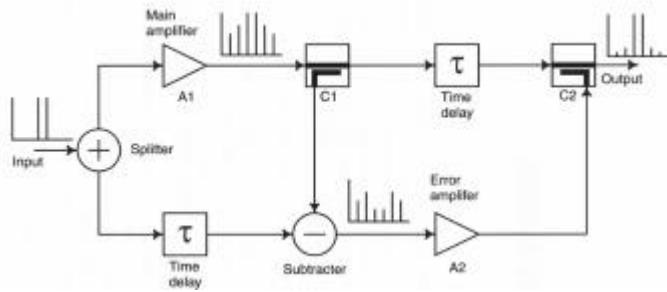

- Overcomes Stability Problem by forward-only Loops
- Critical to Gain/Phase-Imbalances  
0.5dB Gain Error → -31dB Cancellation  
2.5° Phase Error → -27dB Cancellation
- Well suited for narrowband application

## Cartesian Feedback

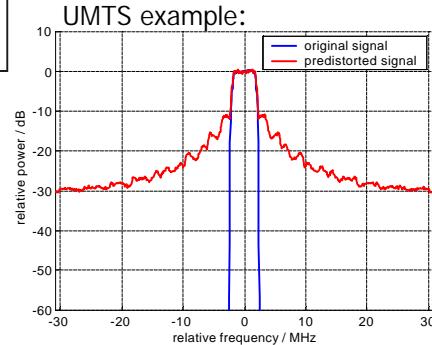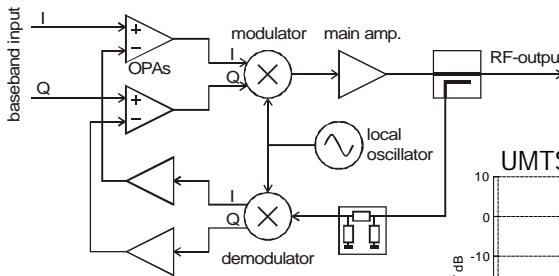

- AM/AM- and AM/PM-correction
- High Feedback-Bandwidth
- Stability Problems




TECHNISCHE UNIVERSITÄT WIEN

39
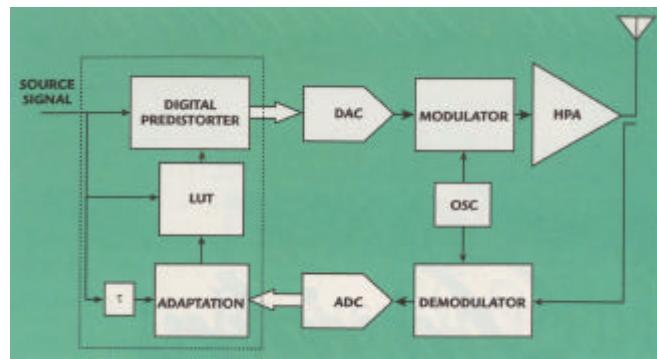
## Digital Predistortion


- Digital Implementation of „Cartesian Feedback“
- Additional ADCs, DSP Power, Oversampling needed
- Loop can be opened → no Stability Problems



TECHNISCHE UNIVERSITÄT WIEN

40


## Analog Predistortion

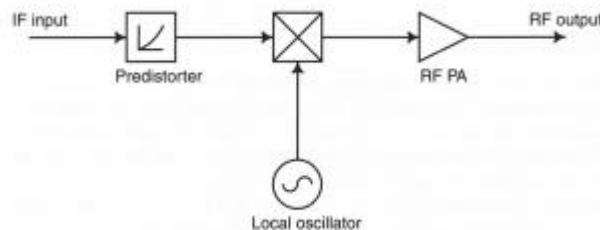


- ◉ Predictorter has inverse Function of Amplifier
- ◉ Leads to infinite Bandwidth (!)
- ◉ Hard to realize (accuracy)

## Analog Predistortion

- ◉ Possible Realizations:

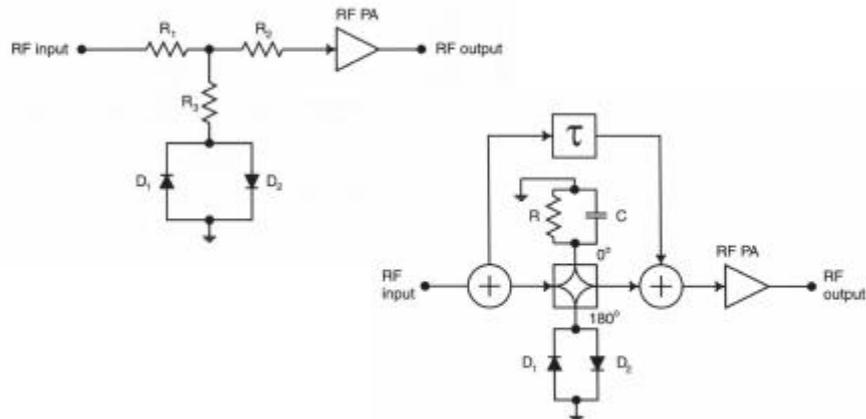

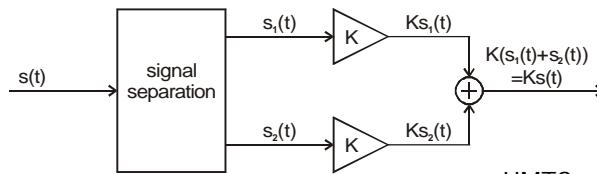
## LINC (Linear Amplification by Nonlinear Components)



- AM/AM- and AM/PM-correction
- Digital separation required (accuracy!)
- High Bandwidth, oversampling necessary
- Stability guaranteed


UMTS example:

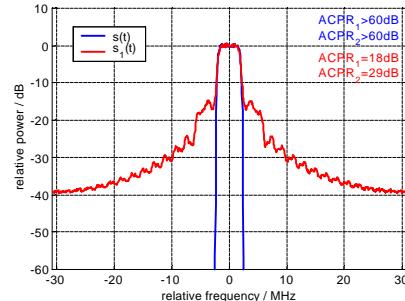

43
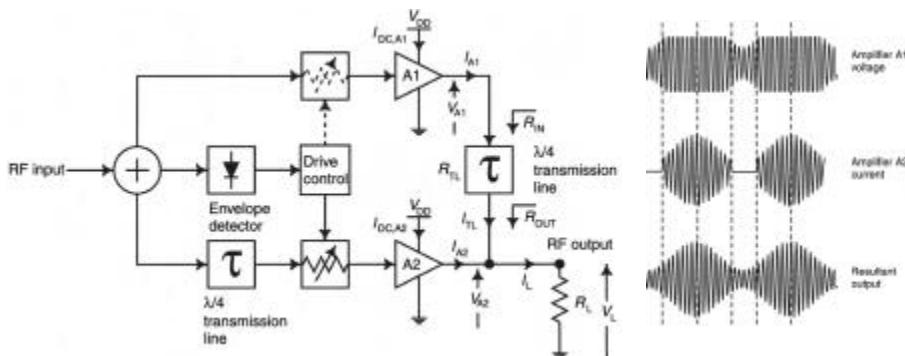
## Doherty Amplifier


- Auxiliary amplifier supports main amplifier during saturation
- PAE can be kept high over a 6dB range




44

## Doherty Amplifier

- Gain vs. Input Power

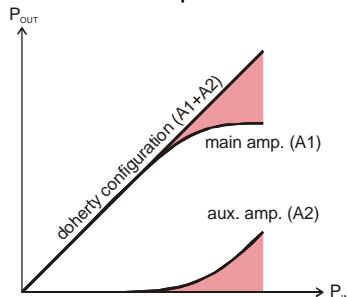


- Efficiency vs. Input Power

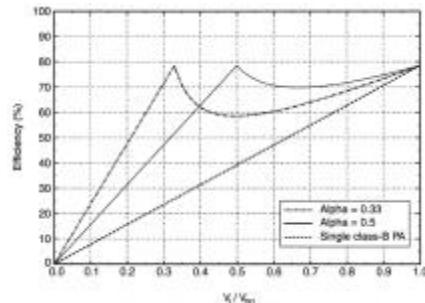

- No improvement of AM/AM- and AM/PM-distortion
- Behavior of auxiliary amplifier very hard (impossible) to realize
- Stability guaranteed
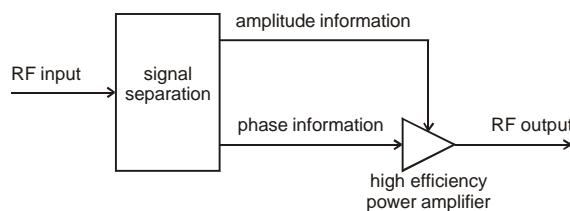
## EER (Envelope Elimination and Restoration)


- Separating phase and magnitude information
- Elimination of AM/AM-distortion
- Application of high-efficient amplifiers (independent of amplitude distortion)
- Stability guaranteed


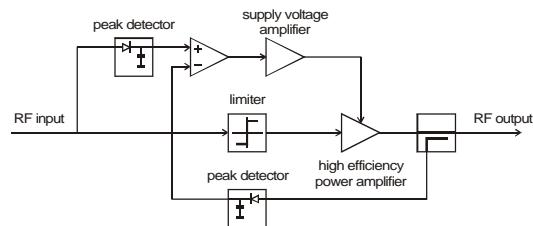
## EER (Envelope Elimination and Restoration)


- Analog realization

- Limiter hard to build
- Accuracy problems
- Feedback necessary




- Digital realization

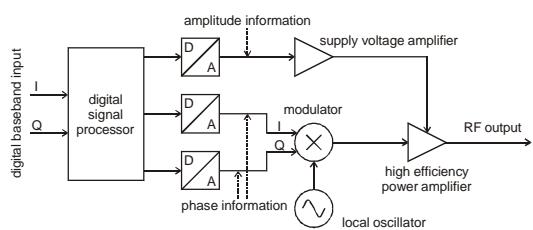- Oversampling + high D/A conversion rates required
- High power consumption of DSP and D/A-converters
- Possible feedback elimination
- Compensation of AM/PM-distortion possible



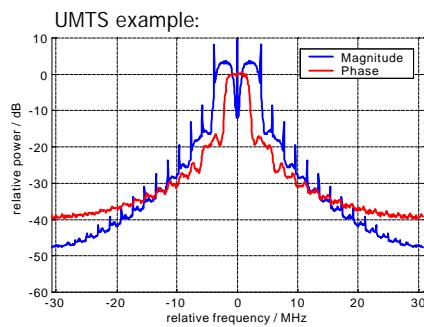
## EER (Envelope Elimination and Restoration)

- Bandwidth of Magnitude- and phase-signal have higher than transmit signal




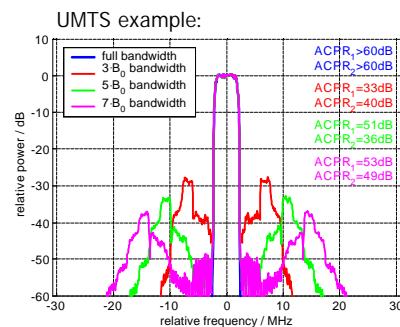- Five times (!) oversampling necessary to achieve standard requirements


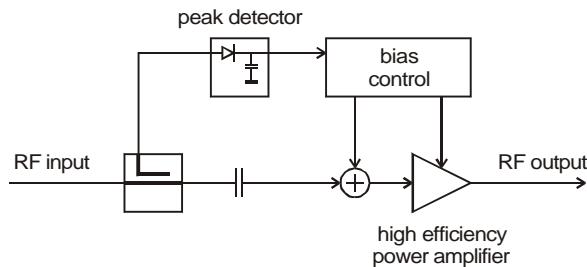
## Adaptive Bias


- Varying/Switching of Bias-Voltage depending on Input Power Level
- Selection of Operating Point with high PAE
- Applicable for nearly each type of Amplifier



49
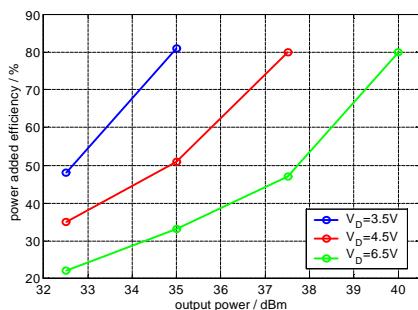
## Adaptive Bias

- Single tone PAE for switched  $V_{DD}$  with  $V_G$  kept constant
- Simply to implement Concept
- Stability guaranteed
- Possible problems:
  - DC-DC converter with high efficiency necessary
  - Possible Linearity Change (can increase and decrease) especially for HCAs



50

## Summary

- Digital Realization required to achieve Accuracy
- Problem of Stability for high Bandwidth Application
- Higher Bandwidths (Oversampling) necessary, depending on Order of IMD cancellation
- Predistortion gives best Results while keeping Efficiency high (valid for high Output Levels > 40dBm)

## Figure References

- F. Zavosh et al,  
“Digital Predistortion Techniques for RF Power Amplifiers with CDMA Applications”,  
Microwave Journal, Oct. 1999
- Peter B. Kenington,  
“High-Linearity RF Amplifier Design”,  
Artech House, 2000
- Steve C. Cripps,  
“RF Power Amplifiers for Wireless Communications”,  
Artech House, 1999

## Contact Information

**DI Markus Mayer**

 +43-1-58801-35425

 markus.mayer@tuwien.ac.at

**DI Holger Arthaber**

 +43-1-58801-35420

 holger.arthaber@tuwien.ac.at



TECHNISCHE UNIVERSITÄT WIEN